 


FIGURES FOR CHAPTER 10


INTRODUCTION TO VHDL

This chapter in the book includes:

- Objectives
- Study Guide
- 10.1 VHDL Description of Combinational Circuits
- 10.2 VHDL Models for Multiplexers
- 10.3 VHDL Modules
- 10.4 Signals and Constants
- 10.5 Arrays
- 10.6 VHDL Operators
- 10.7 Packages and Libraries
- 10.8 IEEE Standard Logic
- 10.9 Compilation and Simulation of VHDL Code
- Problems





 Click the mouse to move to the next page.
Use the ESC key to exit this chapter.




$C \leq A \text{ and } B \text{ after } 5 \text{ ns};$
 $E \leq C \text{ or } D \text{ after } 5 \text{ ns};$

Figure 10-1: Gate Circuit

  

CLK <= not CLK after 10 ns;


Figure 10-2: Inverter with Feedback

 

```
-- when A changes, these concurrent
-- statements all execute at the same time

D <= A and B after 2 ns;
E <= not A after 1 ns;
F <= A or C after 3 ns;
```

Figure 10-3: Three Gates with a Common Input and Different Delays

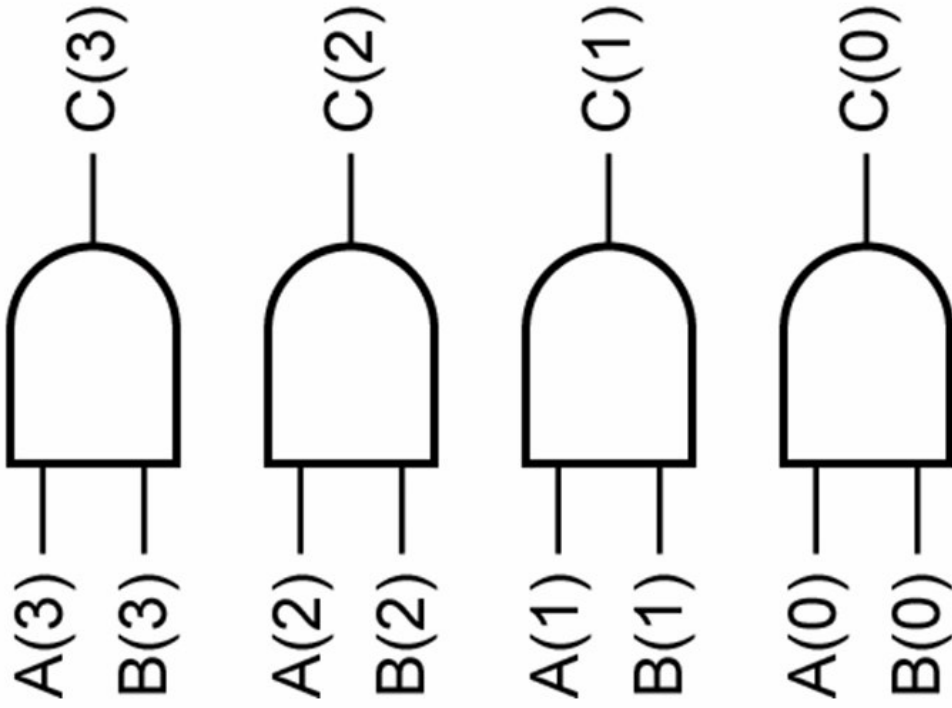


-- the hard way

```
C(3) <= A(3) and B(3);  
C(2) <= A(2) and B(2);  
C(1) <= A(1) and B(1);  
C(0) <= A(0) and B(0);
```

-- the easy way


```
C <= A and B;
```

Figure 10-4: Array of AND Gates

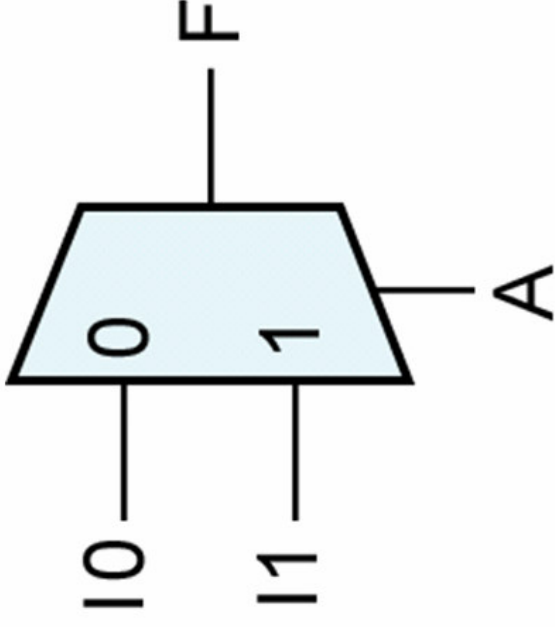


```
-- conditional signal assignment statement  
F <= I0 when A = '0' else I1;
```

Figure 10-5: 2-to-1 Multiplexer

 


```
F <= A when E = '1'  
      else B when D = '1'  
      else C;
```

Figure 10-6: Cascaded 2-to-1 MUXes

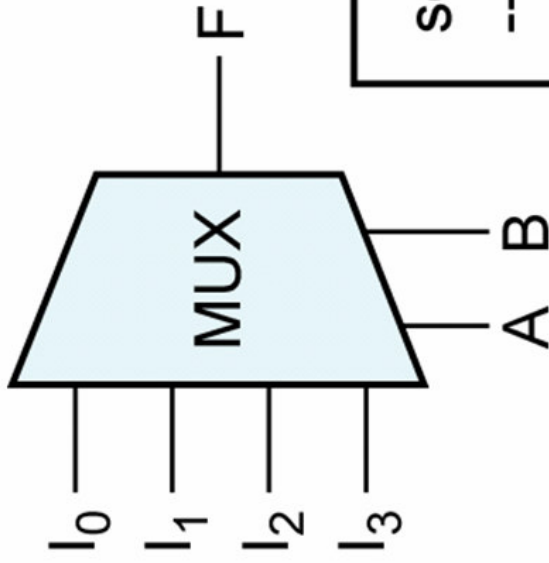

```
sel <= A&B;  
-- selected signal assignment statement  
with sel select  
  F <= I0 when "00",  
    I1 when "01",  
    I2 when "10",  
    I3 when "11";
```

Figure 10-7: 4-to-1 Multiplexer

 

```
entity two_gates is
  port (A,B,D: in bit; E: out bit);
end two_gates;
architecture gates of two_gates is
  signal C: bit;
begin
  C <= A and B; -- concurrent
  E <= C or D; -- statements
end gates;
```

Figure 10-8: VHDL Module with Two Gates


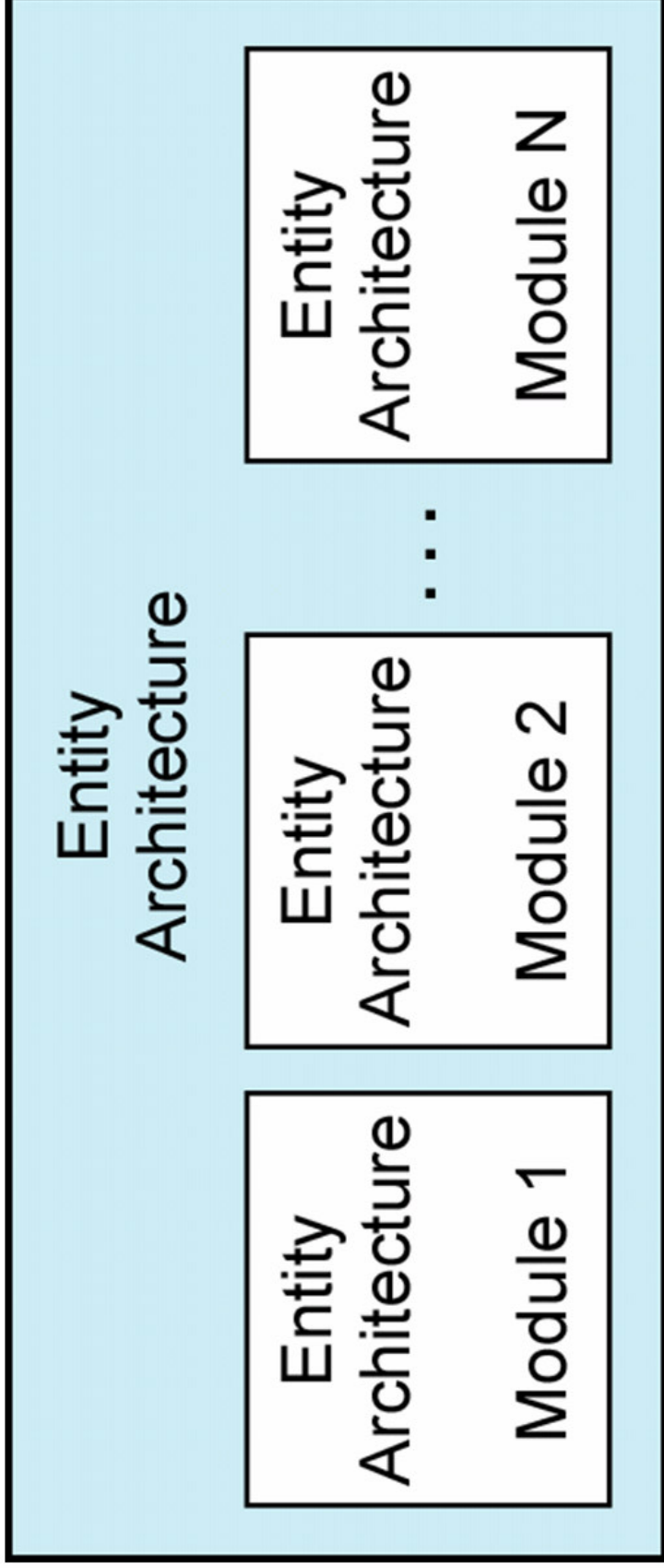


Figure 10-9: VHDL Program Structure

 

```

entity FullAdder is
  port (X,Y,Cin: in bit;          --Inputs
         Cout, Sum: out bit);     --Outputs
end FullAdder;

architecture Equations of FullAdder is
begin
    Sum <= X xor Y xor Cin after 10 ns;
    Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
end Equations ;

```

Figure 10-10: Full Adder Module

 


Figure 10-11: 4-Bit Binary Adder



```




entity Adder4 is
    port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
          S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;

architecture Structure of Adder4 is
component FullAdder
    port (X, Y, Cin: in bit; -- Inputs
          Cout, Sum: out bit); -- Outputs
end component;

signal C: bit_vector(3 downto 1);
begin -- instantiate four copies of the FullAdder
    FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
    FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
    FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
    FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
end Structure;

```

Figure 10-12: Structural Description of a 4-Bit Adder

   

Section 10.3, p. 271

```

1  entity ROM9_17 is
2      port (A, B, C: in bit; F: out bit_vector(0 to 3));
3  end entity;
4  architecture ROM of ROM9_17 is
5      type ROM8X4 is array (0 to 7) of bit_vector(0 to 3);
6      constant ROM1: ROM8X4 := ("1010", "1010",
7          "0111", "0101", "1100", "0001", "1111", "0101");
8      signal index: Integer range 0 to 7;
9      begin
10         Index <= vec2int(A&B&C); -- A&B&C is a 3-bit vector
11         integer
12         F <= ROM1 (index);
13         -- this statement reads the output from the ROM
14     end ROM;

```

Figure 10-13: VHDL Description of a ROM



signal A,B: integer range 0 to 15;
signal C, D, E: Boolean;

C <= A <= B;
D <= A = B;
E <= A > B;


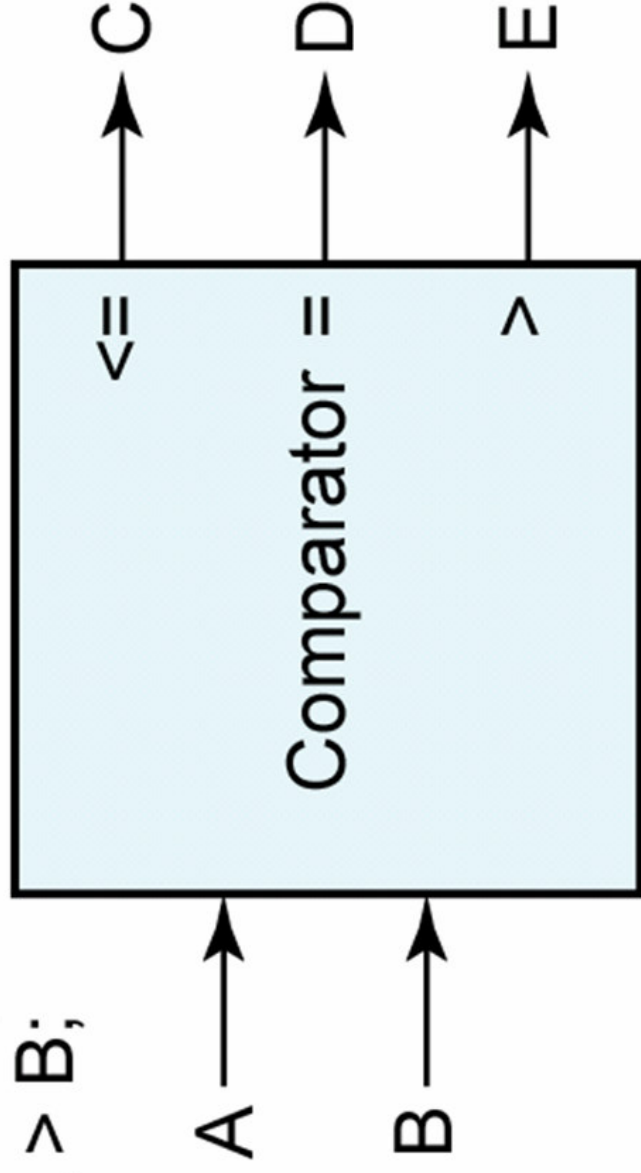


Figure 10-14: Comparator for Integers

 


```

library BITLIB;
use BITLIB.bit_pack.all;
entity nor_nor is
    port (A,B,C,D: in bit; G: out bit);
end nor_nor;
architecture structural of nor_nor is
    signal E,F,BN,CN: bit -- internal signals
begin
    BN <= not B; CN <= not C;
    G1: Nor2 port map (A, BN, E);
    G2: Nor2 port map (CN, D, F);
    G3: Nor2 port map (E, F, G);
end structural;


```

Figure 10-15: NOR-NOR Circuit and Structural VHDL Code Using Library Components

 

```
signal A,B,C: std_logic;  
-----  
C <= A when B = '1' else 'Z';
```

Figure 10-16: Tri-State Buffer

 

```
signal A,C,F: std_logic_vector(3 downto 0);
signal B,D: std_logic;
-----
-- concurrent statements
F <= A when B = '1' else "ZZZZ";
F <= C when D = '1' else "ZZZZ";
```

Figure 10-17: Tri-State Buffers Driving a Bus

		S2				
		U	X	0	1	Z
S1	U	U	U	U	U	U
	X	U	X	X	X	X
	0	U	X	0	X	0
	1	U	X	X	1	1
	Z	U	X	0	1	Z

Figure 10-18: Resolution Function for Two Signals



```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
-----
signal A,B,Sum: std_logic_vector(3 downto 0);
signal Addout: std_logic_vector(4 downto 0);
signal Cin,Cout: std_logic;
-----
Addout <= '0'&A + B + Cin;
Sum <= Addout(3 downto 0);
Cout <= Addout(4);

```

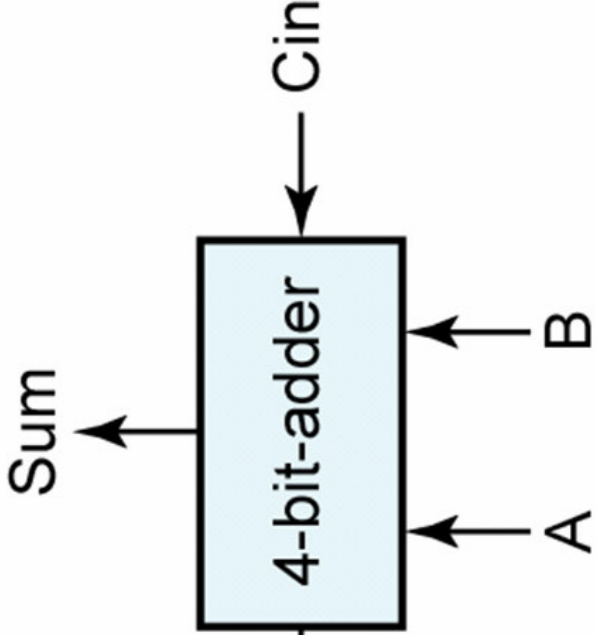


Figure 10-19: VHDL Code for Binary Adder



```
entity IC_pin is  
  port(IO_pin: inout std_logic);  
end entity;  
architecture bi_dir of IC_pin is  
  component IC  
    port(input: in std_logic; output: out std_logic);  
  end component;  
  signal input, output, en: std_logic;  
begin      -- connections to bi-directional I/O pin  
  IO_pin <= output when en = '1' else 'Z';  
  input <= IO_pin;  
  IC1: IC port map (input, output);  
end bi_dir;
```

Figure 10-20: VHDL Code for Bi-Directional I/O Pin


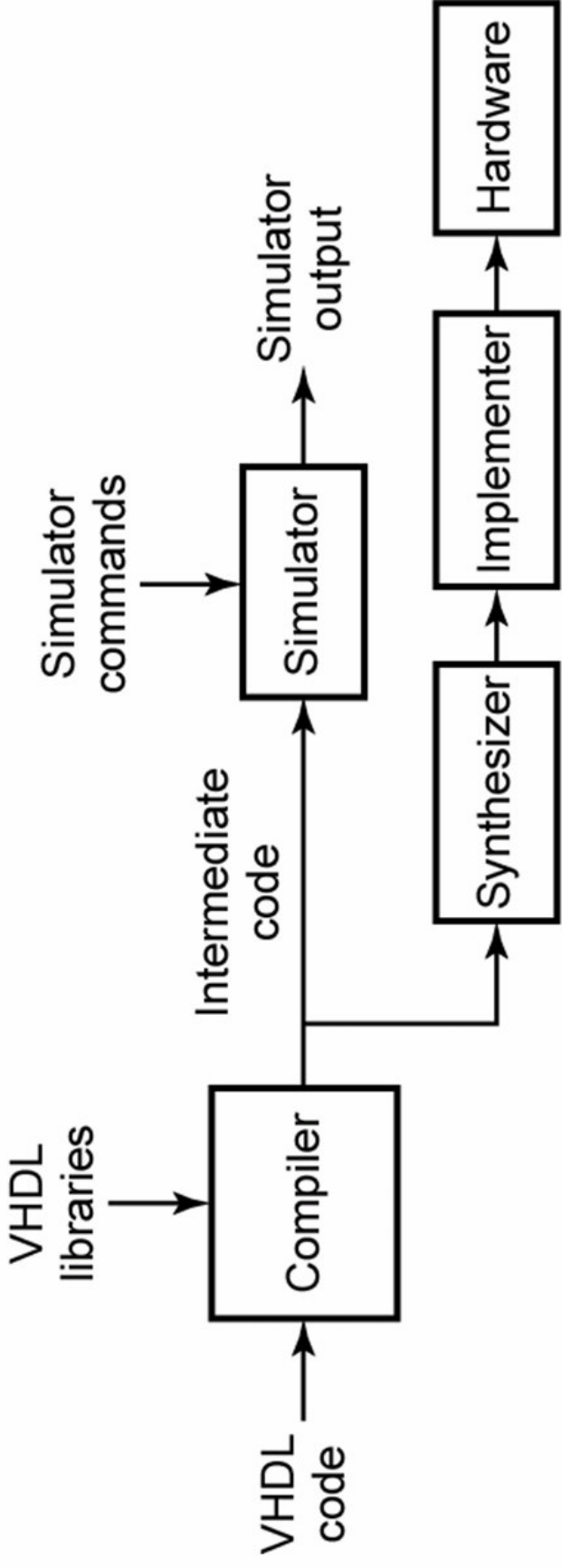


Figure 10-21: Compilation, Simulation, and Synthesis of VHDL Code

 



```

1 B <= not A;
2 C <= not B;
3 D <= not C after 5 ns;
  
```

ns	delta	A	B	C	D
0	+0	0	1	0	1
3	+0	1	1	0	1
3	+1	1	0	0	1
3	+2	1	0	1	1
8	+0	1	0	1	0

Figure 10-22: Simulation of VHDL Code