 


FIGURES FOR CHAPTER 12

REGISTERS AND COUNTERS



This chapter in the book includes:

- Objectives
- Study Guide
- 12.1 Registers and Register Transfers
- 12.2 Shift Registers
- 12.3 Design of Binary Counters
- 12.4 Counters for Other Sequences
- 12.5 Counter Design Using S-R and J-K Flip-Flops
- 12.6 Derivation of Flip-Flop Input Equations--Summary Problems

Click the mouse to move to the next page.
Use the ESC key to exit this chapter.


 


Figure 12-1: 4-Bit D Flip-Flop Registers with Data, Load, Clear, and Clock Inputs

 

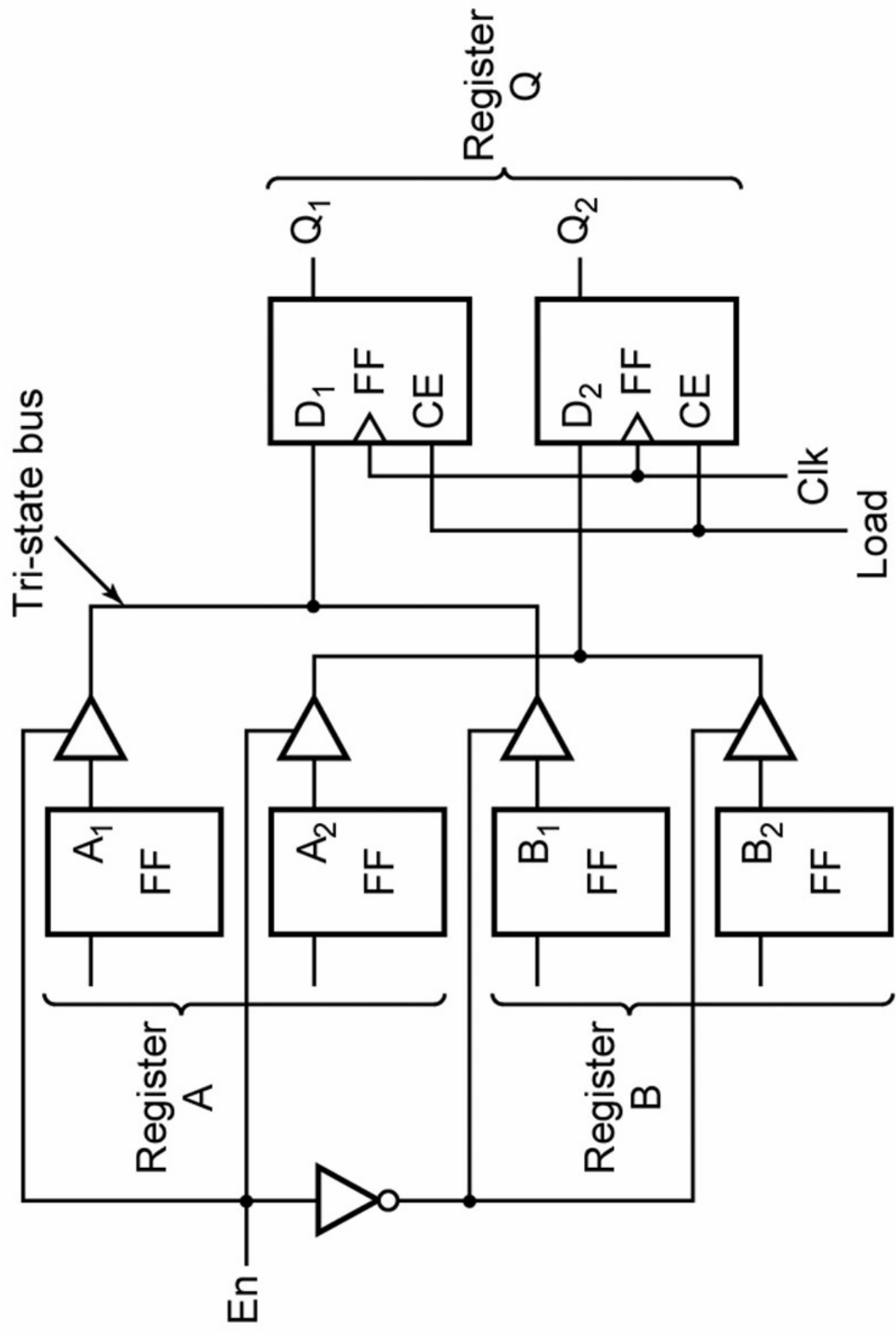


Figure 12-2: Data Transfer Between Registers

©2004 Brooks/Cole

 


Figure 12-3: Logic Diagram for 8-Bit Register with Tri-State Output



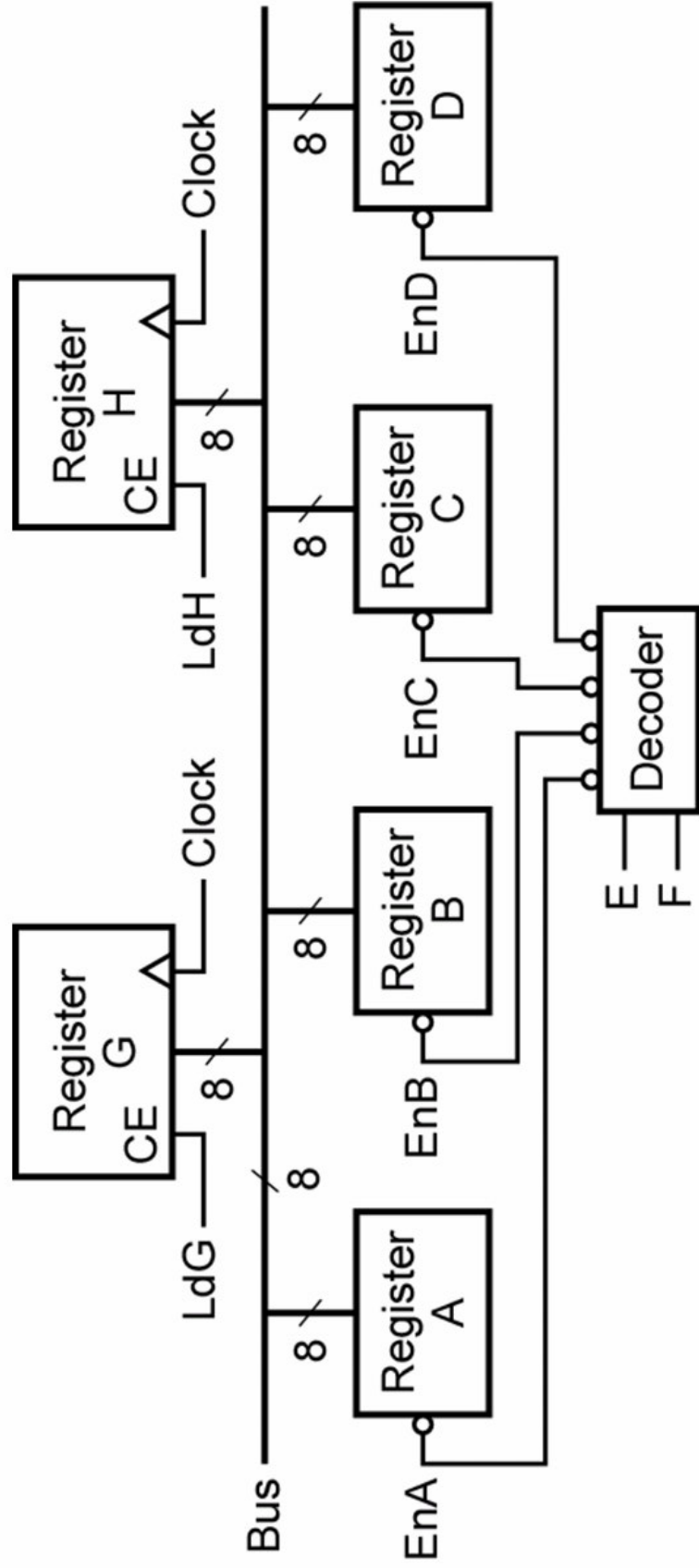


Figure 12-4: Data Transfer Using a Tri-State Bus

 


Figure 12-5: N-Bit Parallel Adder with Accumulator


 



Figure 12-6: Adder Cell with Multiplexer

©2004 Brooks/Cole

 



(a) Flip-flop connections

 

(b) Timing diagram

Figure 12-7: Right-Shift Register

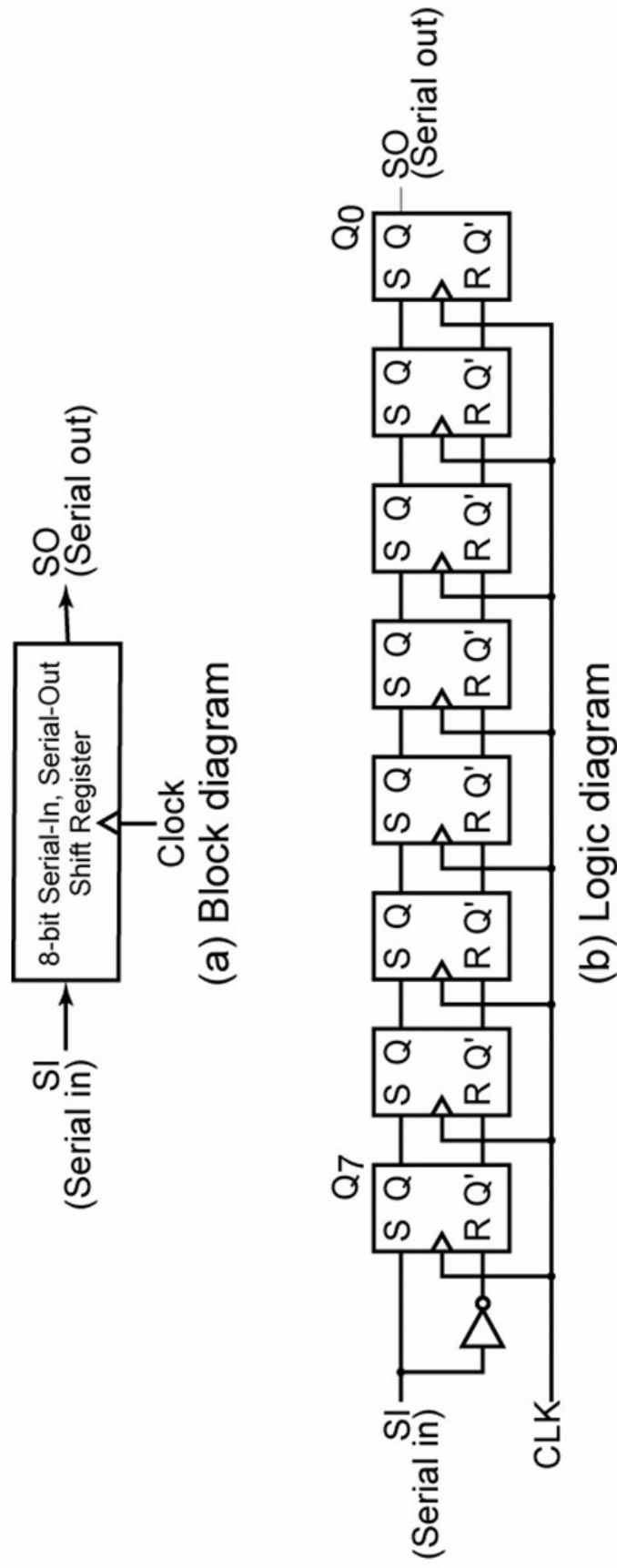


Figure 12-8: 8-Bit Serial-In, Serial-Out Shift Register

 


Figure 12-9: Typical Timing Diagram for Shift Register of Figure 12-8

Figure 12-10:
**Parallel-In,
 Parallel-Out
 Right Shift Register**

 


Table 12-1: Shift Register Operation

Inputs		Next State			Action	
Sh (Shift)	Ld (Load)	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	0	Q_3	Q_2	Q_1	Q_0	no change
0	1	D_3	D_2	D_1	D_0	load
1	X	SI	Q_3	Q_2	Q_1	right shift




 



Figure 12-11: Timing Diagram for Shift Register

©2004 Brooks/Cole

 



(a) Flip-flop connections

 

(b) State graph

Figure 12-12: Shift Register with Inverted Feedback

 


Figure 12-13: Synchronous Binary Counter

Table 12-2 State Table for Binary Counter

Present State			Next State			Flip-Flop Inputs		
C	B	A	C^+	B^+	A^+	T_C	T_B	T_A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1




 


Figure 12-14: Karnaugh Maps for Binary Counter

©2004 Brooks/Cole

 

 


Figure 12-15: Binary Counter with D Flip-Flops

©2004 Brooks/Cole




 


Figure 12-16: Karnaugh Maps for D Flip-Flops

 

CBA	C ⁺ B ⁺ A ⁺	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

Figure 12-17: State Graph and Table for Up-Down Counter




 


Figure 12-18: Binary Up-Down Counter

©2004 Brooks/Cole

 



(a)

ClrN	Ld	Ct	C^+	B^+	A^+
0	X	X	0	0	0
1	1	X	D_C	D_B	D_A
1	0	0	C	B	A
1	0	1	Present state + 1		

(b)

ClrN	Ld	Ct	Output
0	X	X	(load)
1	0	0	(no change)

Figure 12-19ab: Loadable Counter with Count Enable

 


Figure 12-20: Circuit for Figure 12-19

 


Figure 12-21:
State Graph
for Counter

Table 12-3: State
Table for Figure 12-21

C	B	A	C ⁺	B ⁺	A ⁺
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

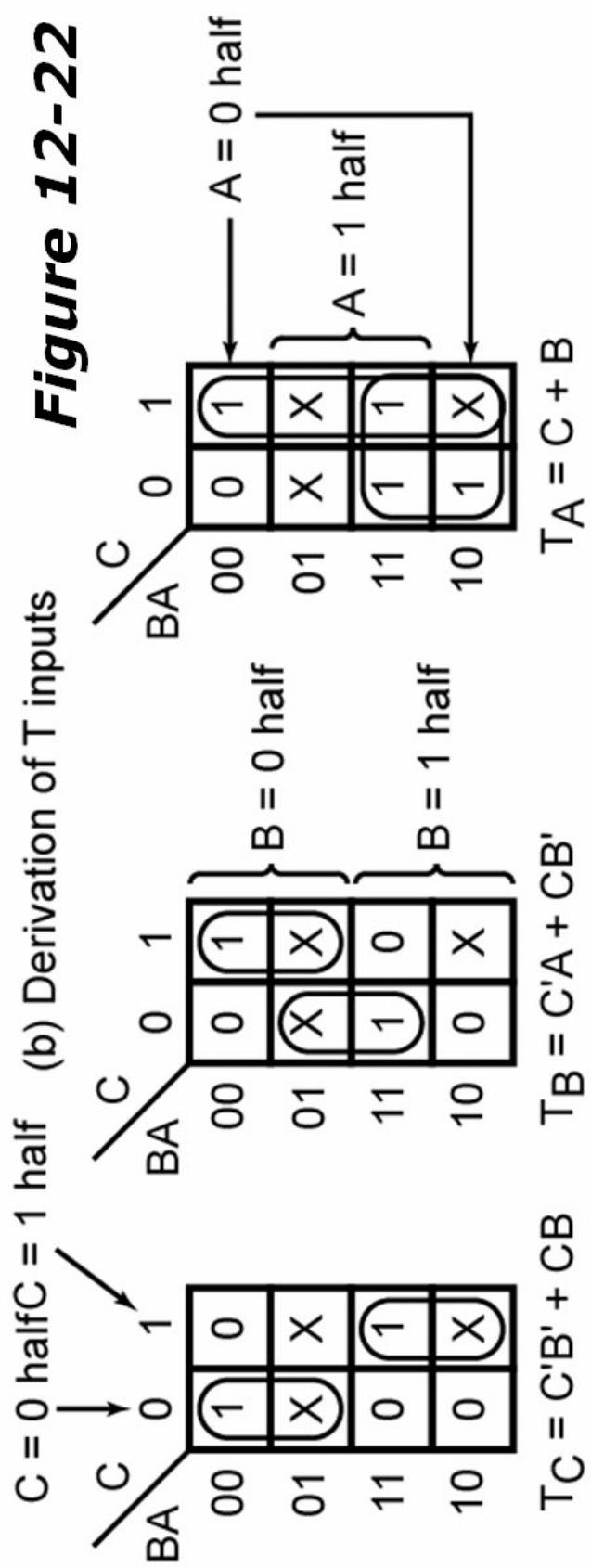
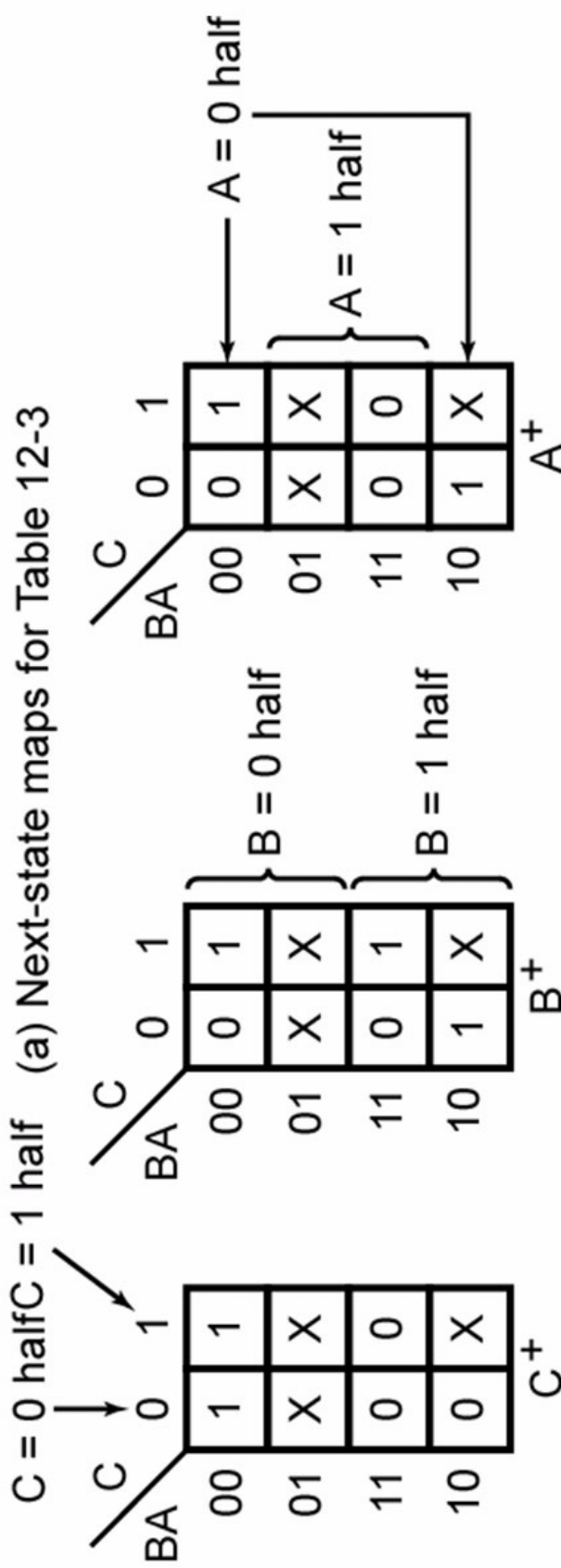


Table 12-4. Input for T Flip-Flop

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

$$T = Q^+ \oplus Q$$

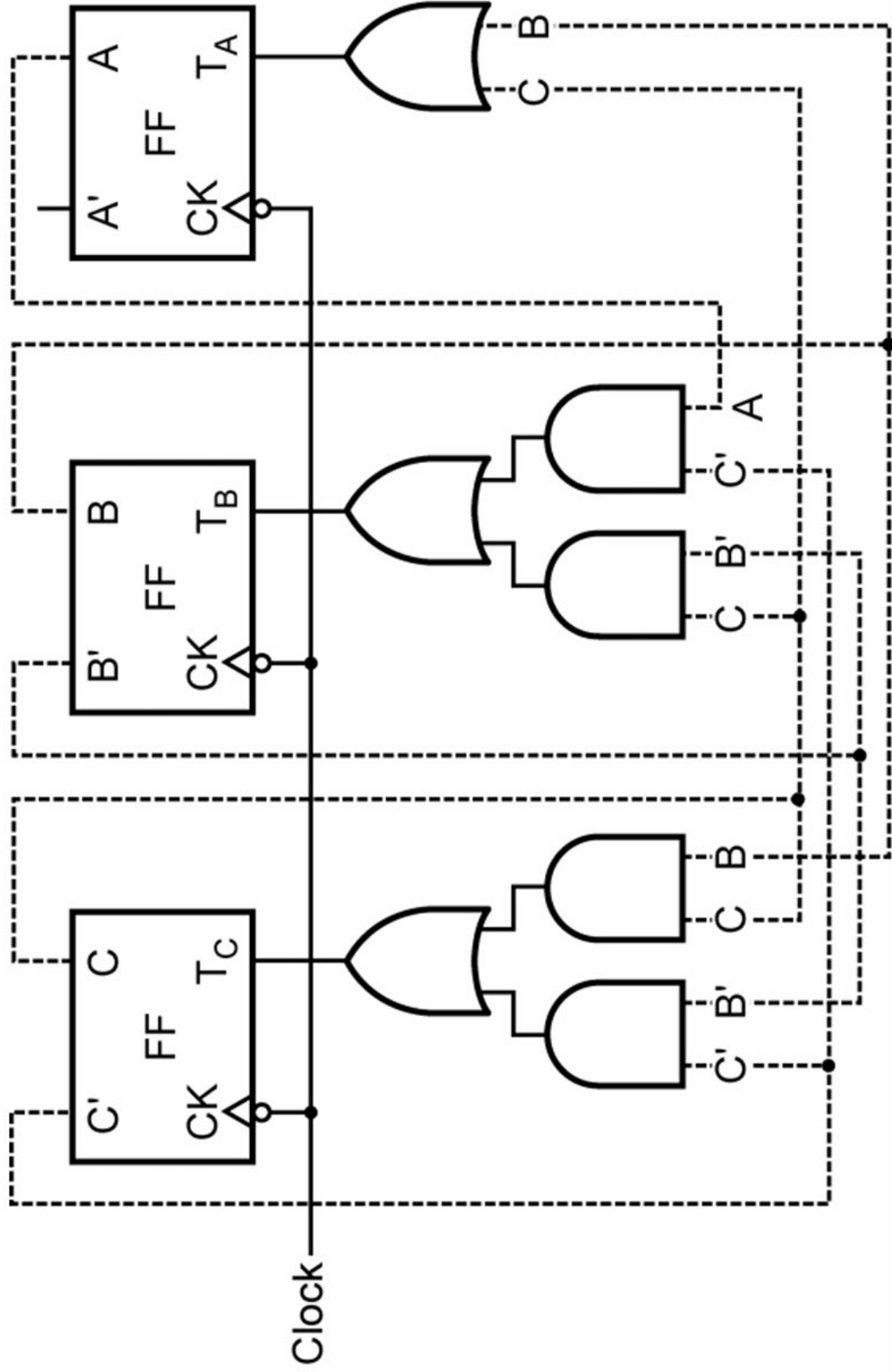


Figure 12-23: Counter Using T Flip-Flops

©2004 Brooks/Cole

 


Figure 12-24: Timing Diagram for Figure 12-23

©2004 Brooks/Cole



 


Figure 12-25: State Graph for Counter

 


Figure 12-26: Counter of Figure 12-21 Using D Flip-Flops

Table 12-5. S-R Flip-Flop Inputs

(a)

S	R	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

(b)

Q	Q^+	S	R
0	0	{0	0
0	1	0	1
1	0	1	0
1	1	0	1
1	1	{0	0
1	1	1	0

(c)

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$Q^+ = S + R'Q$
 $(SR = 0)$

inputs not allowed

Table 12-6.

C	B	A	C ⁺	B ⁺	A ⁺	S _C	R _C	S _B	R _B	S _A	R _A
0	0	0	1	0	0	1	0	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	0	0	0	X	0	1	1	0	1
1	0	0	1	1	1	X	X	X	X	X	X
1	0	1	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	0	1	X	X	0	1





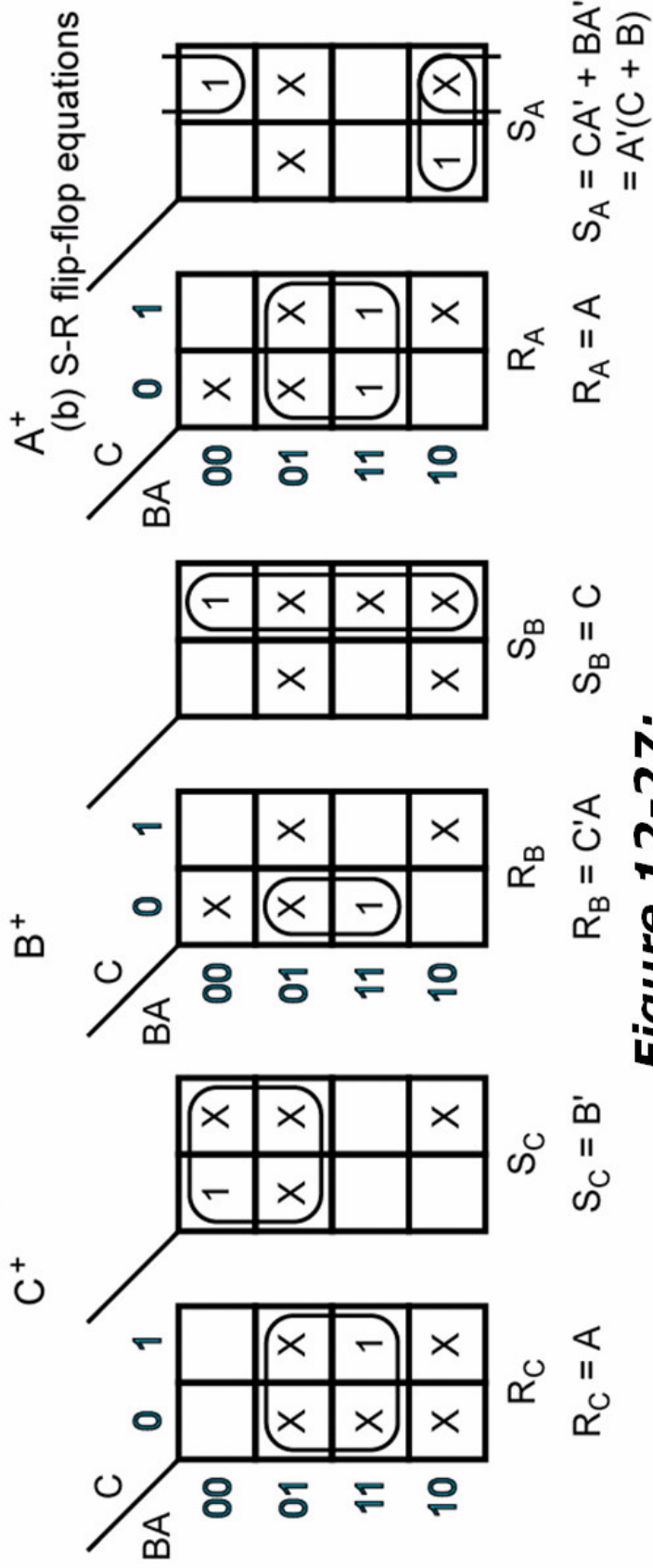


Figure 12-27:
Counter of Figure 12-21 Using S-R Flip-Flops

 

 

(c) Logic circuit

Figure 12-27:
Counter of Figure 12-21
Using S-R Flip-Flops



Table 12-7. J-K Flip-Flop Inputs

J	K	Q	Q^+		Q	Q^+	J	K
0	0	0	0		0	0	0	0
0	0	1	1		0	0	0	1
0	1	0	0		0	1	1	0
0	1	1	0		1	0	1	1
1	0	0	1		1	0	0	1
1	0	1	1		1	1	1	1
1	1	0	1		1	1	0	0
1	1	1	0		1	1	1	0

(a)

J	K	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b)

Q	Q^+	J	K
0	0	{	0 0
0	1	{	0 1
1	0	{	1 0
1	1	{	1 1
1	0	{	0 1
1	1	{	1 1
1	0	{	0 0
1	1	{	1 0

(c)

Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$Q^+ = JQ' + K'Q$



Table 12-8.

C	B	A	C^+	B^+	A^+	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	X	1	X	0	X	1




 


Figure 12-28:
Counter of Figure 12-21 Using J-K Flip-Flops

 

(c) Logic circuit (omitting the feedback lines)

Figure 12-28:
Counter of Figure 12-21
Using J-K Flip-Flops

Table 12-9. Determination of Flip-Flop Input Equations from Next-State Equations Using Karnaugh Maps

Type of Flip-Flop	Input	Rules for Forming Input Map From Next State Map*						
		$Q = 0$		$Q = 1$				
		$Q^+ = 0$	$Q^+ = 1$	$Q^+ = 0$	$Q^+ = 1$			
Delay	D	0	1	0	1	$Q = 0$ Half of Map	$Q = 1$ Half of Map	no change
Trigger	T	0	1	1	0	no change	no change	complement
Set-Reset	S	0	1	0	X	no change	replace 1's with X's**	replace 1's with X's**
	R	X	0	1	0	replace 0's with X's**	complement	complement
J-K	J	0	1	X	X	no change	fill in with X's	fill in with X's
	K	X	X	1	0	fill in with X's	complement	complement



Q \ AB	0	1
00	0	1
01	1	0
11	0	0
10	1	X

Q^+

Next-state map

Q \ AB	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$D = Q'A'B + QB' + AB'$

D input map

Q \ AB	0	1
00	0	0
01	1	1
11	0	1
10	1	X

$T = A'B + AB' + QB$

T input map

Q \ AB	0	1
00	0	X
01	1	0
11	0	0
10	1	X

$S = AB' + Q'A'B$

S-R input maps

Q \ AB	0	1
00	X	0
01	0	1
11	X	1
10	0	X

$R = QB$

Q \ AB	0	1
00	0	X
01	1	X
11	0	X
10	1	X

$J = A'B + AB'$

J-K input maps

Q \ AB	0	1
00	X	0
01	X	1
11	X	1
10	X	X

$K = B$

Example Illustrating the Use of Table 12-9





 
 


Figure 12-29a:
Derivation of Flip-Flop Input Equations
Using 4-Variable Maps

 

Figure 12-29b:
Derivation of Flip-Flop
Input Equations Using
4-Variable Maps

 

S₂

R₂



Figure 12-29c:
Derivation of Flip-Flop
Input Equations Using
4-Variable Maps

