

FIGURES FOR CHAPTER 16


SEQUENTIAL CIRCUIT DESIGN

This chapter in the book includes:

Objectives

Study Guide

 - 16.1 Summary of Design Procedure for Sequential Circuits
 - 16.2 Design Example--Code Converter
 - 16.3 Design of Iterative Circuits
 - 16.4 Design of Sequential Circuits Using ROMs and PLAs
 - 16.5 Sequential Circuit Design Using CPLDs
 - 16.6 Sequential Circuit Design Using FPGAs
 - 16.7 Simulation and Testing of Sequential Circuits
 - 16.8 Overview of Computer-Aided Design
- Design Problems
- Additional Problems



Click the mouse to move to the next page.
Use the ESC key to exit this chapter.

Table 16-1.

X Input (BCD)				Z Output (excess-3)			
t_3	t_2	t_1	t_0	t_3	t_2	t_1	t_0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0



Table 16-2. State Table for Code Converter

Time	Input Sequence Received (Least Significant Bit First)	Present State	Next State $X=0$ 1	Present Output (Z) $X=0$ 1
t_0	reset	A	B C	1 0
t_1	0 1	B C	D F E G	1 0 0 1
t_2	00 01 10 11	D E F G	H L I M J N K P	0 1 1 0 1 0 1 0
t_3	000 001 010 011 100 101 110 111	H I J K L M N P	A A A A A - A - A - A - A - A -	0 1 0 1 0 - 0 - 0 - 1 - 1 - 1 -



Table 16-3. Reduced State Table for Code Converter

Time	Present State	Next State $X = 0$	Next State $X = 1$	Present Output (Z) $X = 0$	Present Output (Z) $X = 1$
t_0	A	B	C	1	0
t_1	B	D	E	1	0
	C	E	E	0	1
t_2	D	H	H	0	1
	E	H	M	1	0
t_3	H	A	A	0	1
	M	A	-	1	-

 


Figure 16-1: State Graph for Code Converter


		Q_1	
		0	1
Q_2Q_3	00	A	B
	01		C
	11	H	D
	10	M	E

(a) Assignment map


$Q_1Q_2Q_3$	$Q_1^+Q_2^+Q_3^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
A 000	100	101	1	0
B 100	111	110	1	0
C 101	110	110	0	1
D 111	011	011	0	1
E 110	011	010	1	0
H 011	000	000	0	1
M 010	000	xxx	1	x
- 001	xxx	xxx	x	x

(b) Transition table


Figure 16-2: Assignment Map for Flip Flops

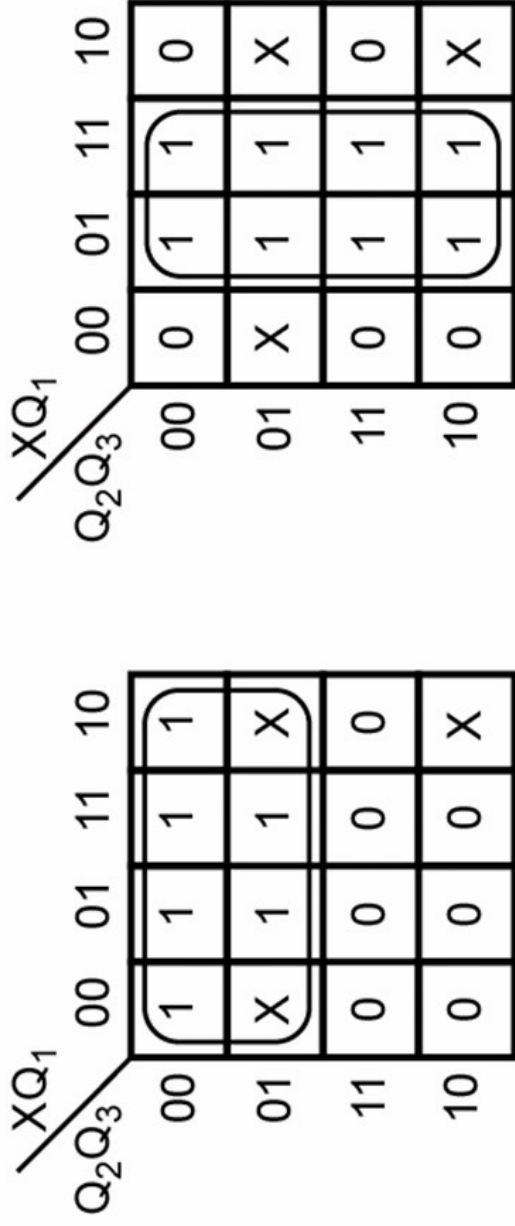

$$D_1 = Q_1^* = Q_2'$$

 

$$D_2 = Q_2^* = Q_1$$

 

$$D_3 = Q_3^* = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$$

$$Z = X'Q_1' + XQ_3$$

Figure 16-3: Karnaugh Maps for Code Converter Design

©2004 Brooks/Cole



 


Figure 16-4: Code Converter Circuit



 


Figure 16-5: Unilateral Iterative Circuit

 


Figure 16-6: Form of Iterative Circuit for Comparing Binary Numbers



Table 16-4 State Table for Comparator

		S_{i+1}				$Z_1 Z_2 Z_3$
		$x_i y_i = 00$	01	11	10	
$X = Y$ $X > Y$ $X < Y$	S_i					
	S_0	S_0	S_2	S_0	S_1	0 1 0
	S_1	S_1	S_1	S_1	S_1	0 0 1
S_2	S_2	S_2	S_2	S_2	1 0 0	

Table 16-5 Transition Table for Comparator

$a_i b_i$	$a_{i+1} b_{i+1}$			$Z_1 Z_2 Z_3$	
	$x_i y_i = 00$	01	11		10
00	00	10	00	01	0 1 0
01	01	01	01	01	0 0 1
10	10	10	10	10	1 0 0

	$x_i y_i$ 00	01	11	10
$a_j b_j$	00	0	0	0
	01	0	0	0
	11	X	X	X
	10	1	1	1

$$a_j + 1 = a_j + x_i y_i b_j$$

	$x_i y_i$ 00	01	11	10
$a_j b_j$	00	0	0	0
	01	1	1	1
	11	X	X	X
	10	0	0	0

$$b_j + 1 = b_j + x_i y_i a_j$$

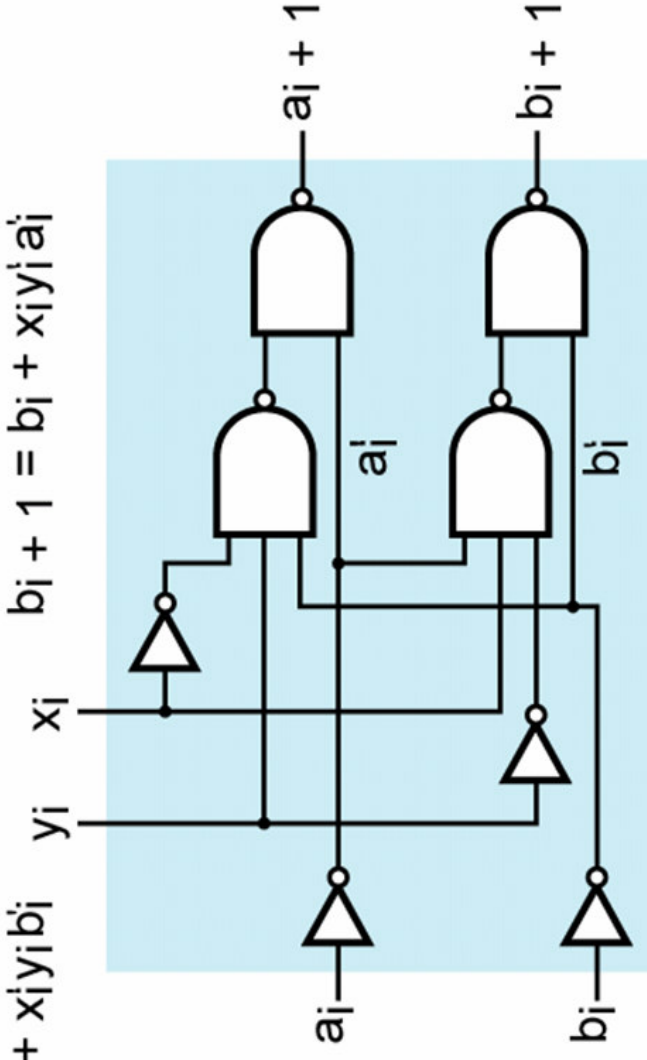


Figure 16-7:
Typical Cell for
Comparator



 
 


Figure 16-8: Output Circuit for Comparator

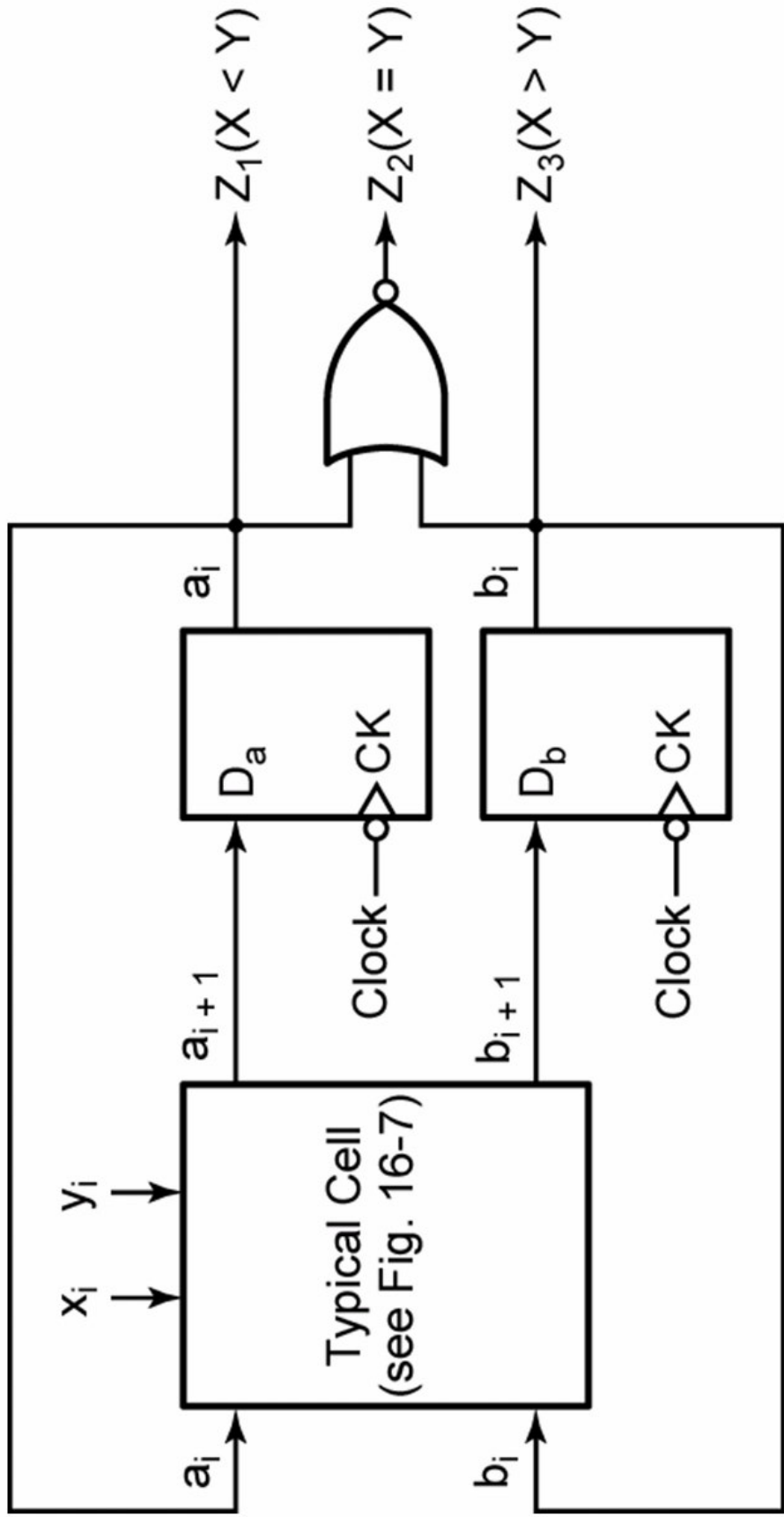


Figure 16-9: Sequential Comparators for Binary Numbers



Table 16-6a

(a) state table

Present State	Next State		Present Output (Z)
	X = 0	X = 1	
A	B	C	1
B	D	E	0
C	E	E	1
D	H	H	0
E	H	M	1
H	A	A	0
M	A	-	1

Table 16-6b

(b) transition table

	$Q_1 Q_2 Q_3$	$Q_1^+ Q_2^+ Q_3^+$		Z	
		$X = 0$	$X = 1$	$X = 0$	$X = 1$
A	000	001	010	1	0
B	001	011	100	1	0
C	010	100	100	0	1
D	011	101	101	0	1
E	100	101	110	1	0
H	101	000	000	0	1
M	110	000	-	1	-



Table 16-6c Truth Table

X	Q_1	Q_2	Q_3	Z	D_1	D_2	D_3
0	0	0	0	1	0	0	1
0	0	0	1	1	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	1
0	1	0	0	1	1	0	1
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	0
0	1	1	1	X	X	X	X
1	0	0	0	0	0	1	0
1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	0	1	1	0
1	1	0	1	1	0	0	0
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X



 


Figure 16-10:
Realization of
Table 16.6(a)
Using a ROM



Table 16-7

X	Q ₁	Q ₂	Q ₃	Z	D ₁	D ₂	D ₃
-	-	0	-	0	1	0	0
-	1	-	-	0	0	1	0
-	1	1	1	0	0	0	1
0	1	-	0	0	0	0	1
1	0	0	-	0	0	0	1
0	-	-	0	1	0	0	0
1	-	-	1	1	0	0	0

 


Figure 16-11: Segment of Sequential PAL

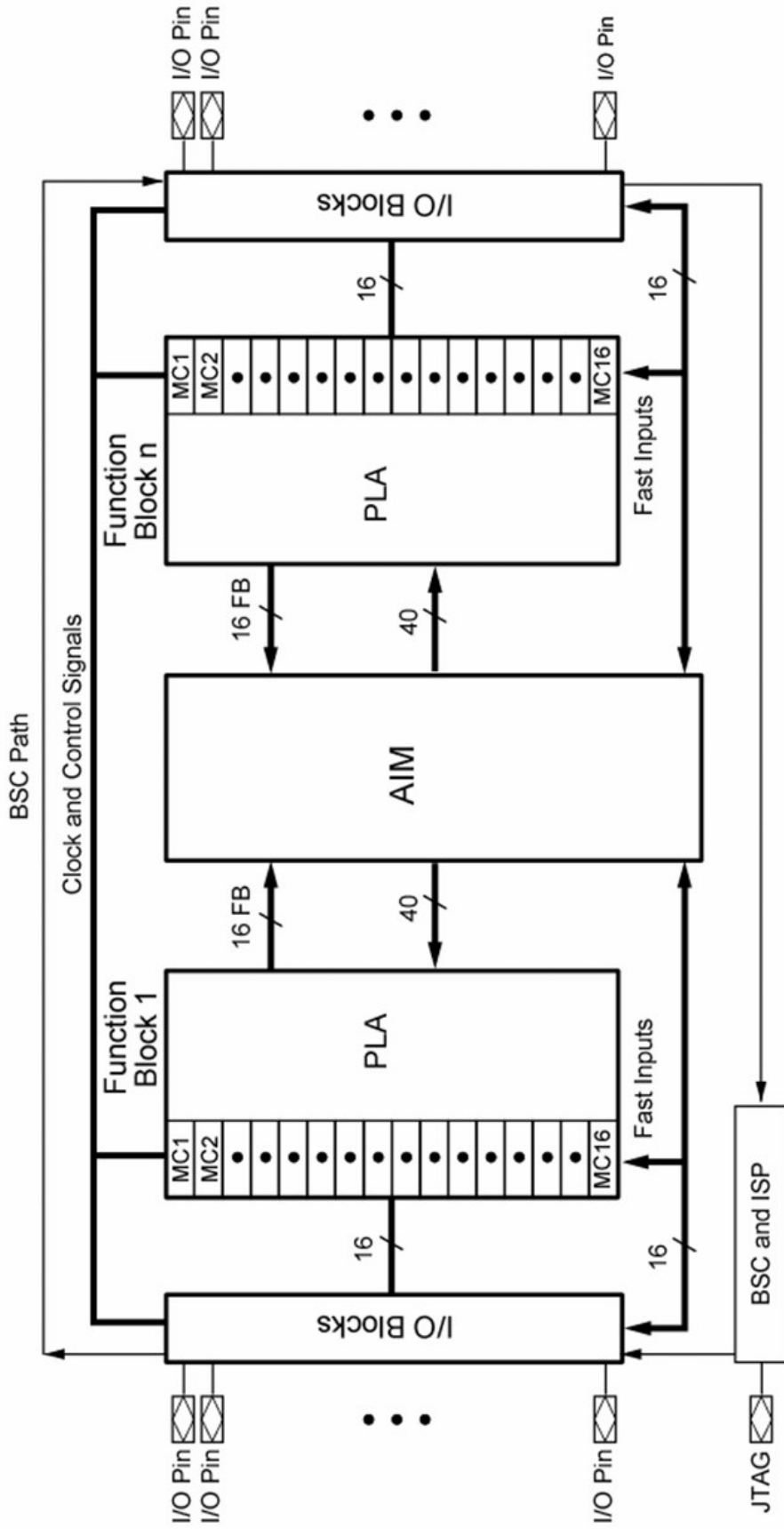


Figure 16-12: CoolRunner-II Architecture
 (Figure based on figures and text owned by Xilinx, Inc., Courtesy of Xilinx, Inc. © Xilinx, Inc. 1999-2003. All rights reserved.)



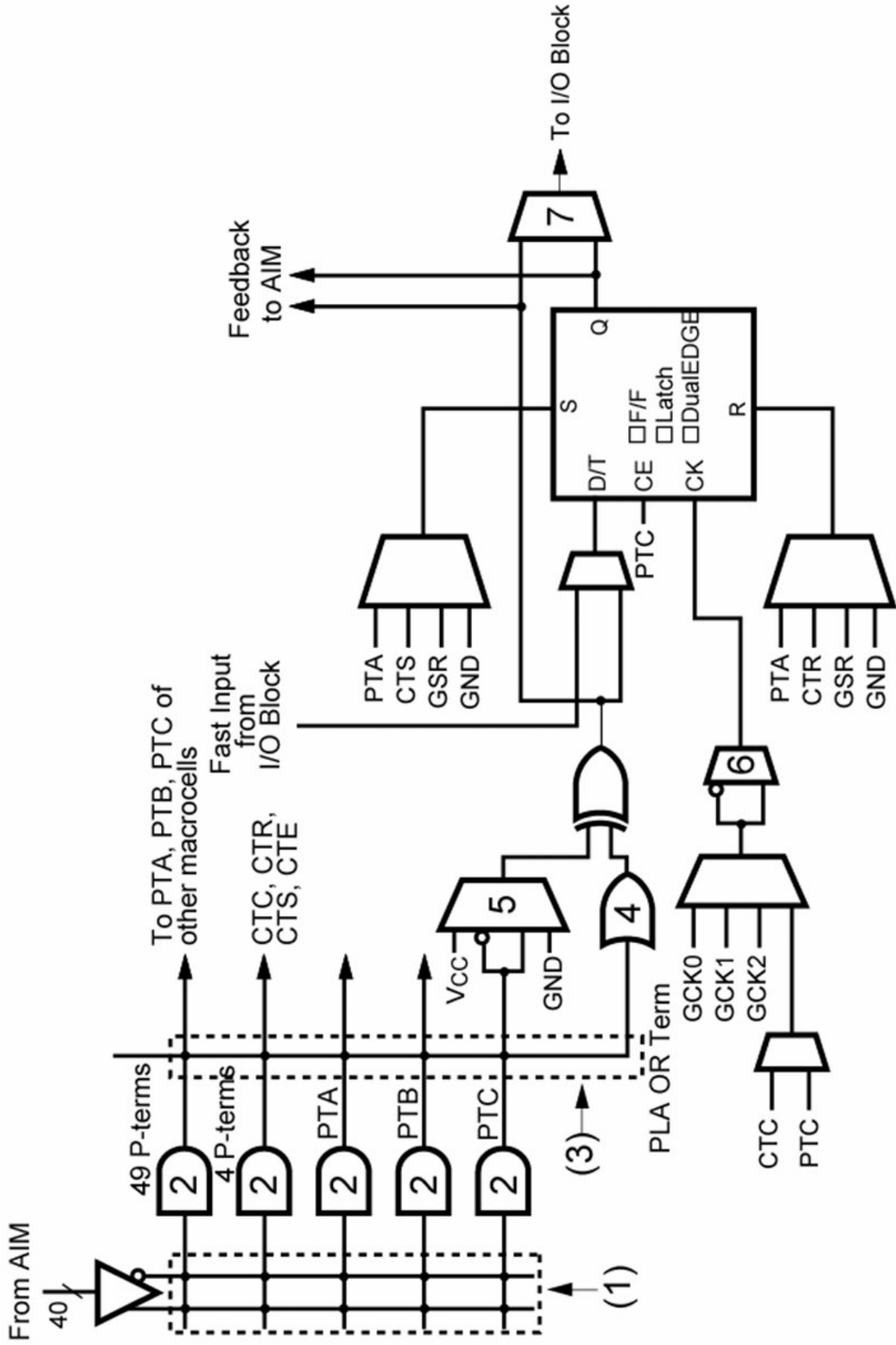


Figure 16-13: CoolRunner-II Macrocell

(Figure based on figures and text owned by Xilinx, Inc., Courtesy of Xilinx, Inc. © Xilinx, Inc. 1999-2003. All rights reserved.)



 


Figure 16-14: CPLD Implementation of a Mealy Machine



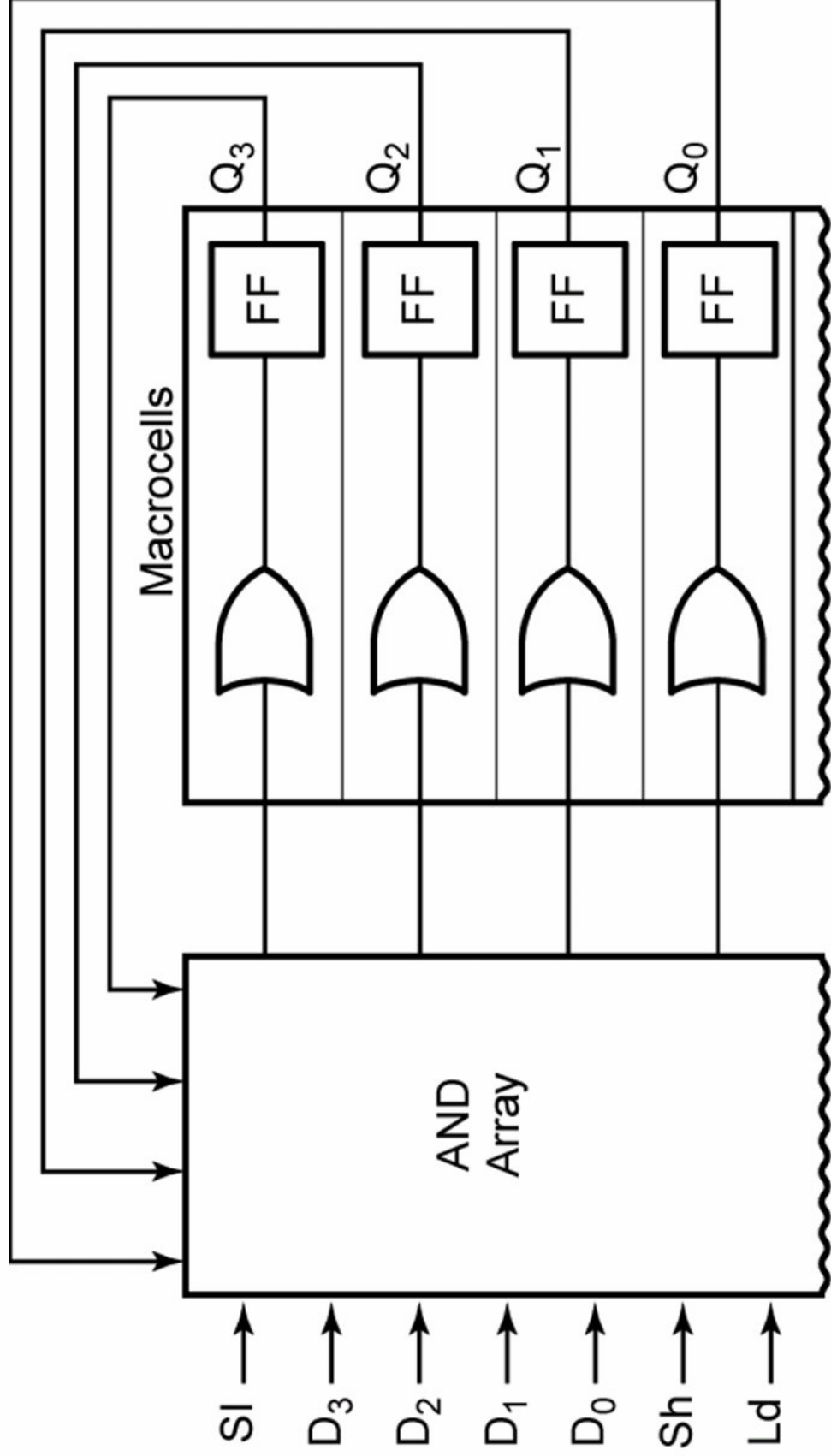


Figure 16-15: CPLD Implementation of a Shift Register

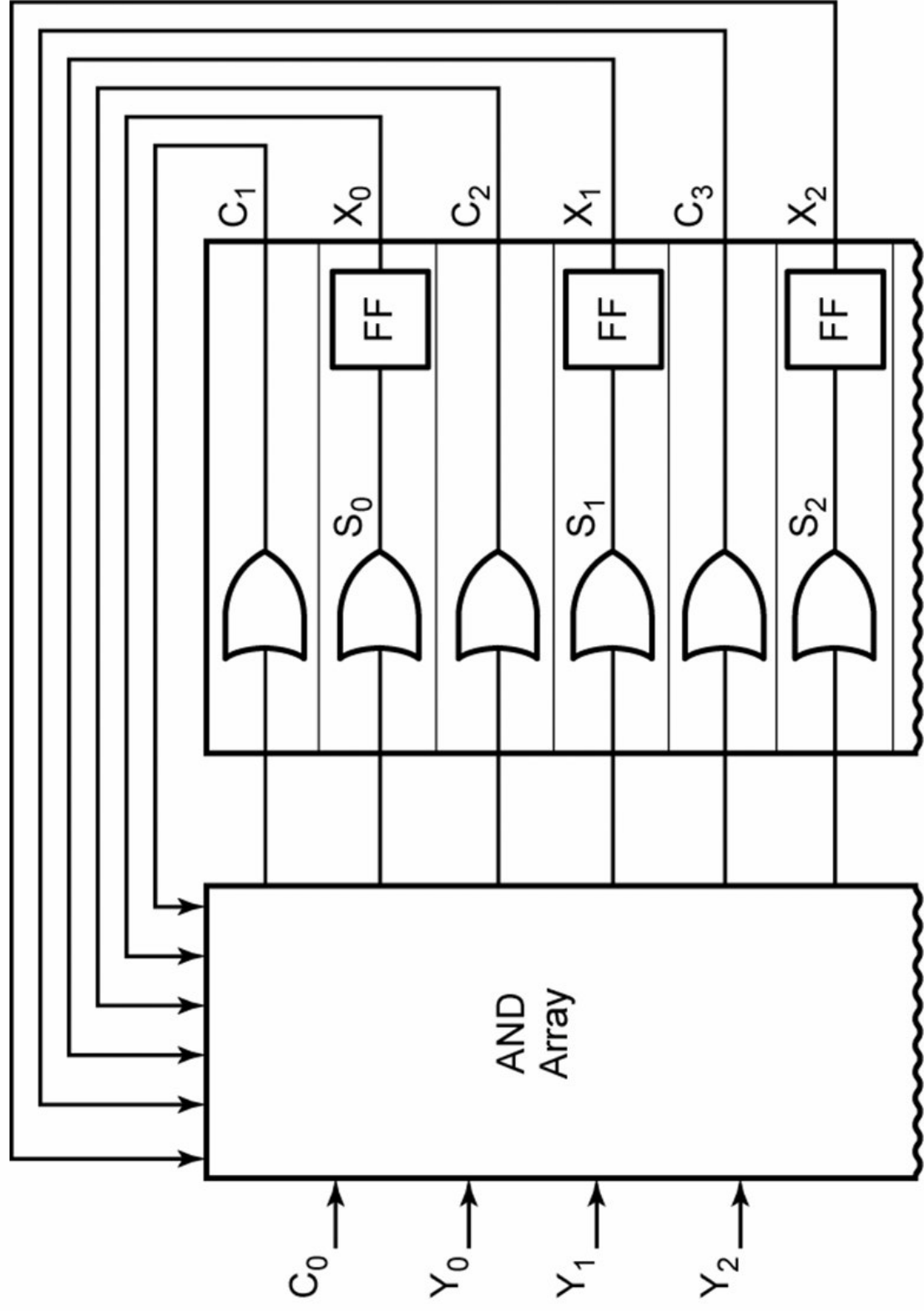


Figure 16-16: CPLD Implementation of a Parallel Adder with Accumulator



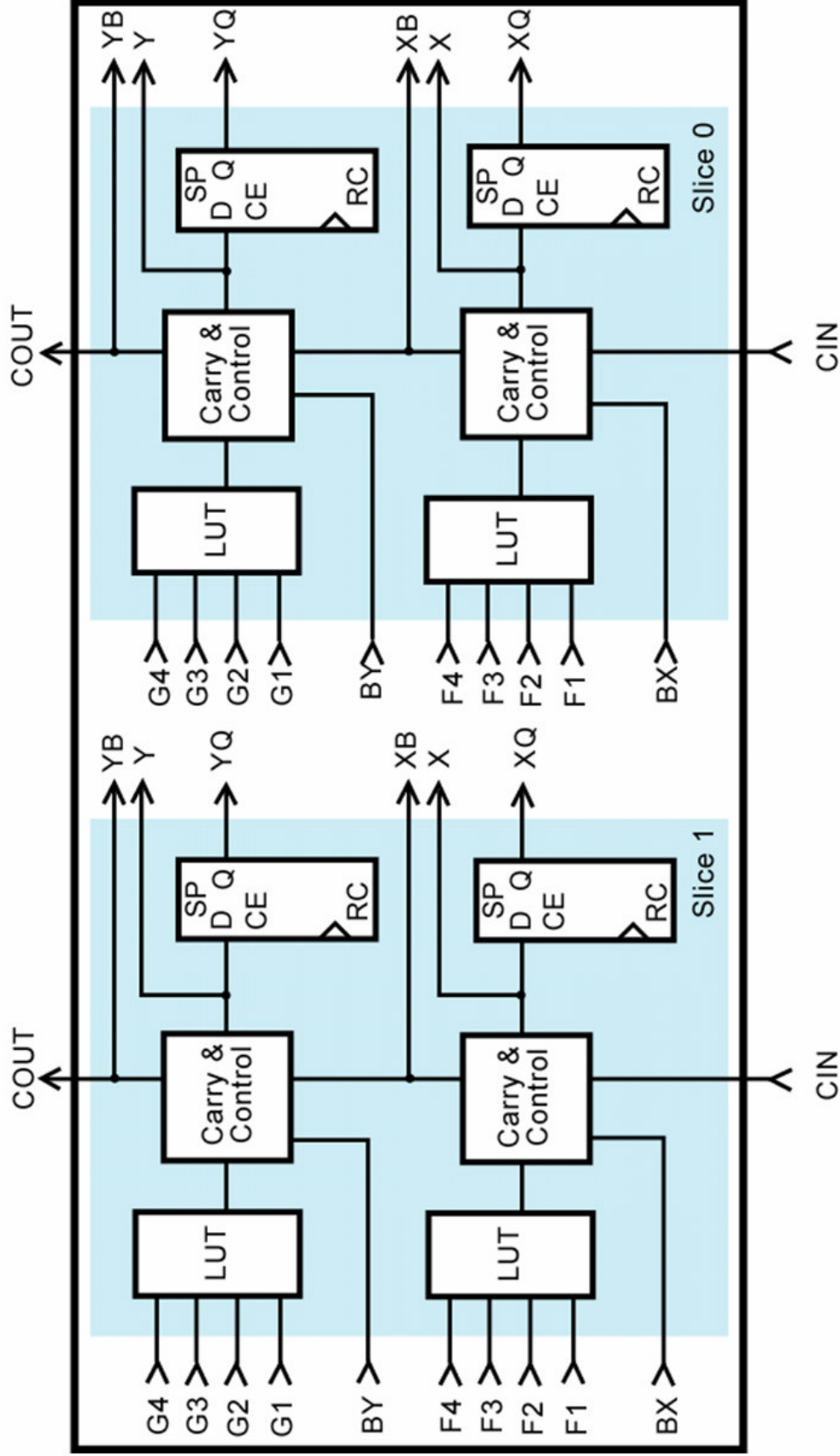


Figure 16-17: Xilinx Virtex/Spartan II CLB (Figure based on figures and text owned by Xilinx, Inc., Courtesy of Xilinx, Inc. © Xilinx, Inc. 1999-2003. All rights reserved.)

 


Figure 16-18:
FPGA
Implementation
of a
Mealy Machine



 


Figure 16-19: FPGA Implementation of a Shift Register

 


Figure 16-20: FPGA Implementation of a Parallel Adder with Accumulator

 


Figure 16-21: Simulator Output for an Inverter


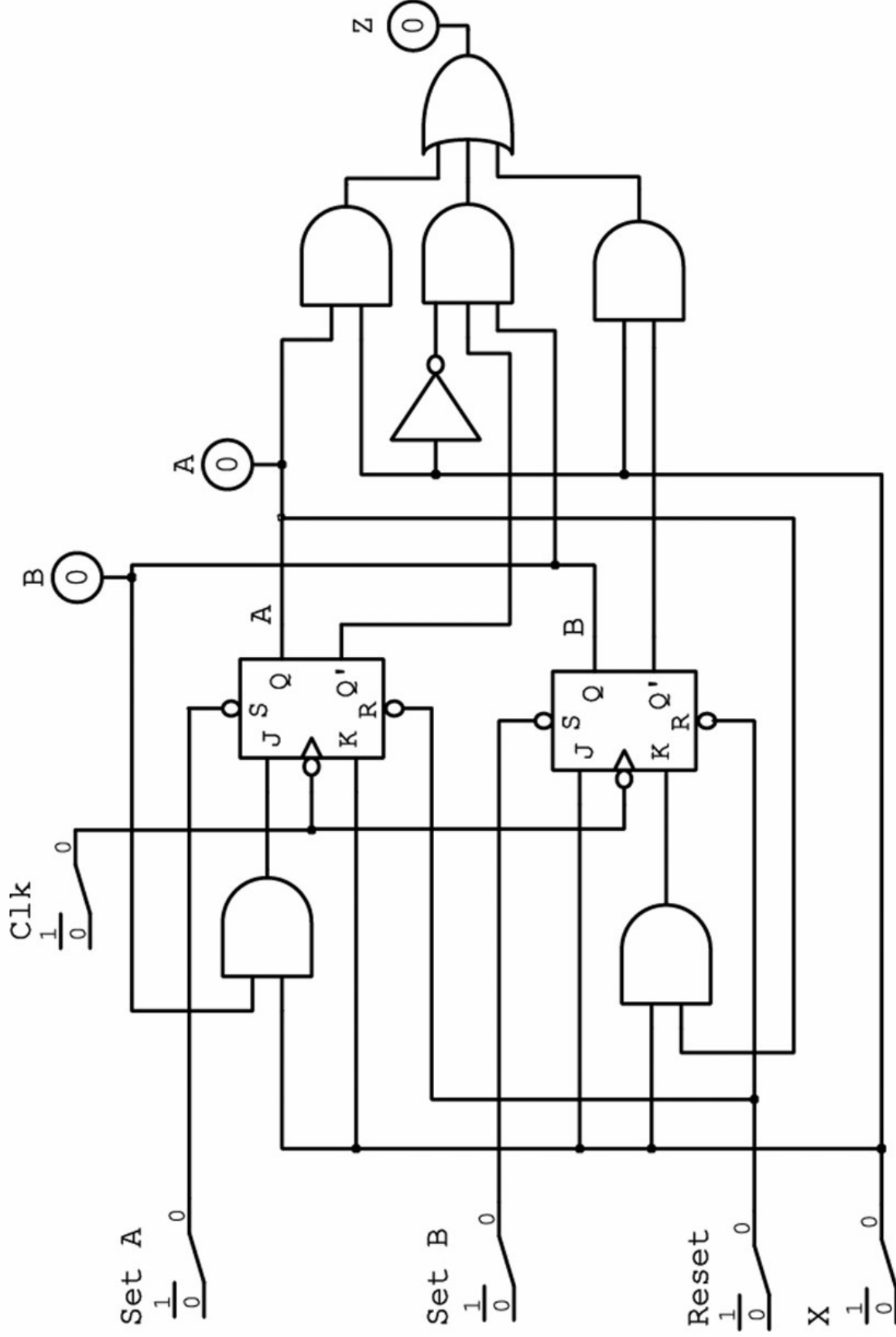



Figure 16-22: Simulation Screen for Figure 13-7

©2004 Brooks/Cole

 



 (a) Simulator output with a unit delay model



(b) Simulator output with a nominal delay of 10 ns

Figure 16-23



 


Figure 16-24: Using a Shift Register to Generate Synchronized Inputs

 

(b) Synchronizer inputs and outputs

 

(a) Synchronizer circuit

Figure 16-25



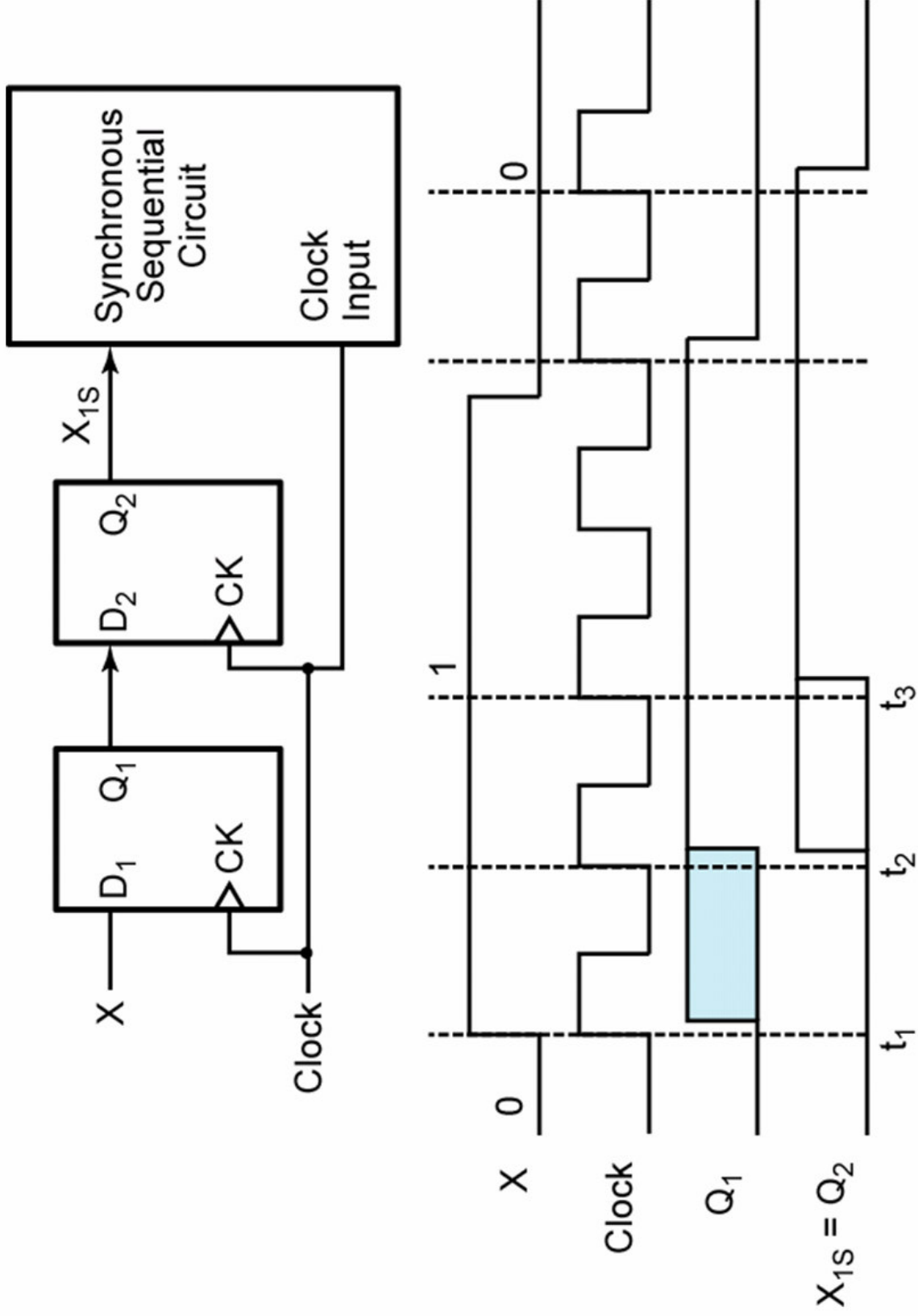


Figure 16-26: Synchronizer with Two D Flip-Flops

©2004 Brooks/Cole



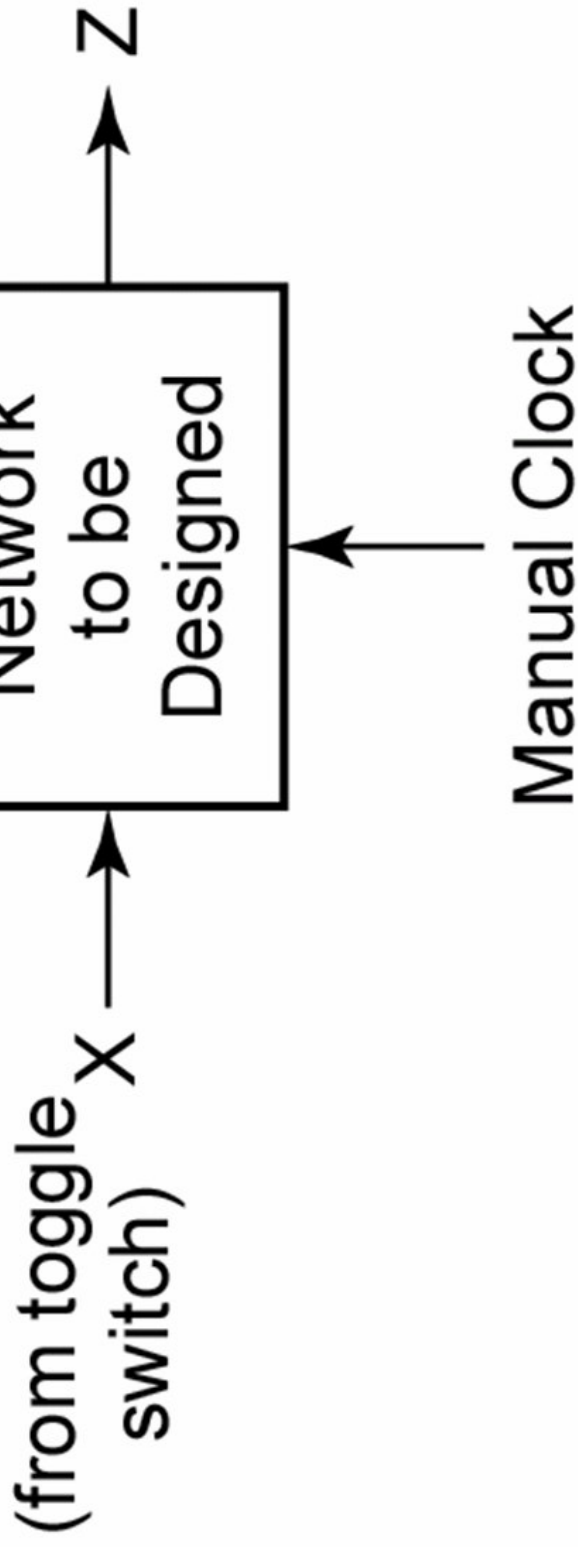


Figure 16-27