 


# FIGURES FOR CHAPTER 17


## VHDL FOR SEQUENTIAL LOGIC



 ***This chapter in the book includes:***

- Objectives
- Study Guide
- 17.1 Modeling Flip-Flops Using VHDL Processes
- 17.2 Modeling Registers and Counters Using VHDL Processes
- 17.3 Modeling Combinational Logic Using VHDL Processes
- 17.4 Modeling a Sequential Machine
- 17.5 Synthesis of VHDL Code
- 17.6 More About Processes and Sequential Statements
- Problems
- Simulation Problems

**Click the mouse to move to the next page.  
Use the ESC key to exit this chapter.**




```
process (CLK)
begin
  if CLK'event and CLK = '1' -- rising edge of CLK
    then Q <= D;
  end if;
end process;
```

**Figure 17-1: VHDL Code for a Simple D Flip-Flop**

©2004 Brooks/Cole




 

```
process (G,D)  
begin  
    if G = '1' then Q <= D; end if;  
end process;
```

**Figure 17-2: VHDL Code for a Transparent Latch**




 

```
process (CLK, ClrN)
begin
  if ClrN = '0' then Q <= '0';
  else if CLK'event and CLK = '1'
    then Q <= D;
    end if;
  end if;
end process;
```


**Figure 17-3: VHDL Code for a D Flip-Flop with Asynchronous Clear**



 

**Figure 17-4: Equivalent Representations of a Flow Chart Using Nested Ifs and Elsifs**



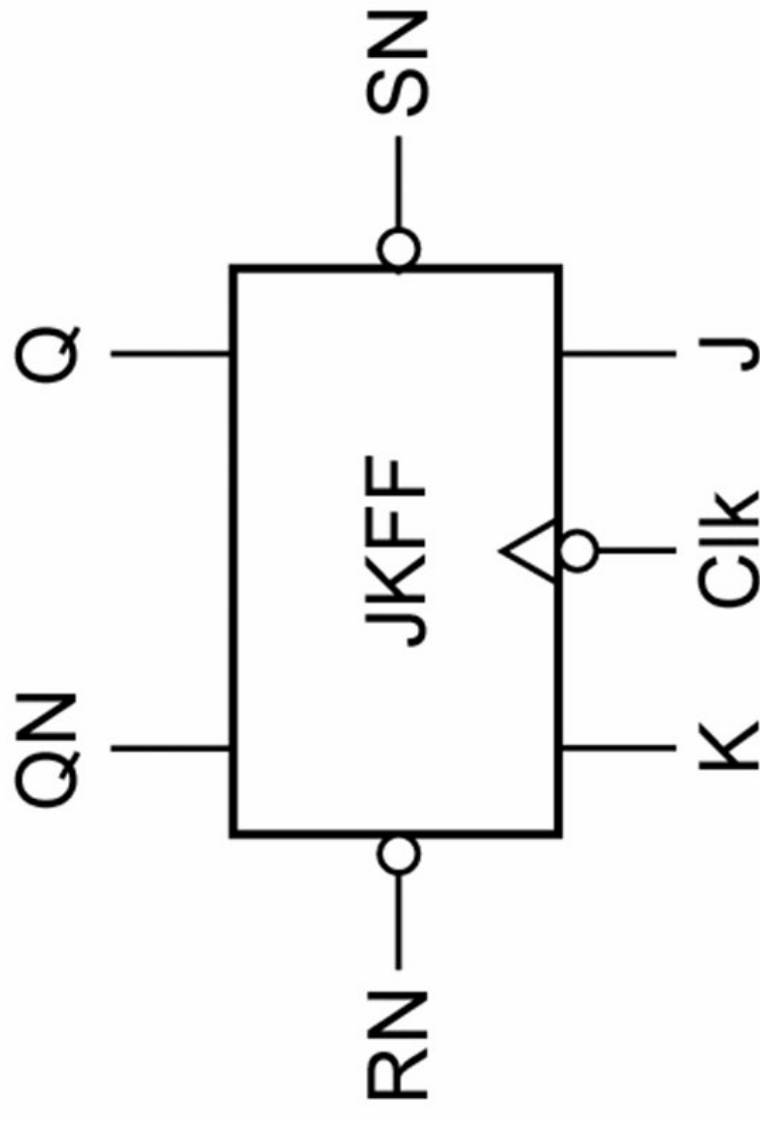

**Figure 17-5: J-K Flip-Flop**



```


1 entity JKFF is
2 port (SN, RN, J, K, CLK: in bit;
3       Q, QN: out bit);
4 end JKFF;

5 architecture JKFF1 of JKFF is
6 signal Qint: bit;
7 begin
8   Q <= Qint; -- output Q and QN to port
9   QN <= not Qint;
10  process (SN, RN, CLK)
11  begin
12    if RN = '0' then Qint <= '0' after 8 ns;
13    elsif SN = '0' then Qint <= '1' after 8 ns;
14    elsif CLK'event and CLK = '0' then
15      Qint <= (J and not Qint) or (not K and Qint) after 10 ns;
16    end if;
17  end process;
18 end JKFF1;

```

**Figure 17-6. J-K Flip-Flop Model**



 


```
process (CLK)
begin
  if CLK'event and CLK = '1' then
    Q1 <= Q3 after 5 ns;
    Q2 <= Q1 after 5 ns;
    Q3 <= Q2 after 5 ns;
  end if;
end process;
```

**Figure 17-7: Cyclic Shift Register**





 


```

process (CLK)
begin
    if CLK'event and CLK = '1' then
        if CLR = '1' then Q <= "0000";
            elsif Ld = '1' then Q <= D;
        end if;
    end if;
end process;

```

**Figure 17-8: Register with Synchronous Clear and Load**



 


```

process (CLK)
begin
  if CLK'event and CLK = '1' then
    if CLR = '1' then Q <= "0000";
    elsif Ld = '1' then Q <= D;
    elsif LS = '1' then Q <= Q(2 downto 0) & Rin;
    end if;
  end if;
end process;

```

**Figure 17-9: Left-Shift Register with Synchronous Clear and Load**

 


```

signal Q: std_logic_vector(3 downto 0);
-----
process (CLK)
begin
  if CLK'event and CLK = '1' then
    if ClrN = '0' then Q <= "0000";
      elsif En = '1' then Q <= Q + 1;
    end if;
  end if;
end process;

```

**Figure 17-10: VHDL Code for a Simple Synchronous Counter**

 

**Figure 17-11: Two 74163 Counters Cascaded to Form an 8-Bit Counter**



**Table 17-1 74163 Counter Operation**

Control Signals		Next State				
ClrN	LdN	PT	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$
0	X	X	0	0	0	0
1	0	X	$D_3$	$D_2$	$D_1$	$D_0$
1	1	0	$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	1	1	present state + 1			

(clear)

(parallel load)

(no change)

(increment count)

```
-- 74163 FULLY SYNCHRONOUS COUNTER

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;
5 entity c74163 is
6   port(LdN, ClrN, P, T, Clk: in std_logic;
7         D: in std_logic_vector(3 downto 0);
8         Cout: out std_logic; Qout: out std_logic_vector(3 downto 0) );
9 end c74163;
```

**Figure 17-12a. 74163 Counter Model**



```

10 architecture b74163 of c74163 is
11   signal Q: std_logic_vector(3 downto 0);    -- Q is the counter register
12 begin
13   Qout <= Q;
14   Cout <= Q(3) and Q(2) and Q(1) and Q(0) and T;
15   process (Clk)
16   begin
17     if Clk'event and Clk = '1' then
18       if ClrN = '0' then Q <= "0000";
19         elsif LdN = '0' then Q <= D;
20         elsif (P and T) = '1' then Q <= Q+1;
21       end if;
22     end if;
23   end process;
24 end b74163;

```

**Figure 17-12b. 74163 Counter Model**



```
--Test module for 74163 counter

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;

5 entity c74163test is
6   port(ClrN,LdN,P,T1,Clk: in std_logic;
7     Din1, Din2: in std_logic_vector(3 downto 0);
8     Count: out integer range 0 to 255;
9     Carry2: out std_logic);
10 end c74163test;
```

**Figure 17-13a. VHDL for 8-Bit Counter**




```

11 architecture tester of c74163test is
12 component c74163
13   port(LdN, ClrN, P, T, Clk: in std_logic;
14     D: in std_logic_vector(3 downto 0);
15     Cout: out std_logic; Qout: out std_logic_vector(3 downto 0) );
16 end component;
17 signal Carry1: std_logic;
18 signal Qout1, Qout2: std_logic_vector(3 downto 0);
19 begin
20   ct1: c74163 port map (LdN, ClrN, P, T1, Clk, Din1, Carry1, Qout1);
21   ct2: c74163 port map (LdN, ClrN, P, Carry1, Clk, Din2, Carry2, Qout2);
22   Count <= Conv_integer(Qout2 & Qout1);
23 end tester;

```

**Figure 17-13b. VHDL for 8-Bit Counter**

 

```
process (A, B, C, D)
begin
    C <= A and B after 5 ns;
    E <= C or D after 5 ns;
end process;
```


**Figure 17-14: VHDL Code for Gate Circuit**

```
signal sel: bit_vector(0 to 1);
-----
sel <= A&B; -- a concurrent statement, outside of the process
process (sel, I0, I1, I2, I3)
begin
  case sel is -- a sequential statement in the process
    when "00" => F <= I0;
    when "01" => F <= I1;
    when "10" => F <= I2;
    when "11" => F <= I3;
    when others => null; -- required if sel is a std_logic_vector;
                        -- omit if sel is a bit_vector
  end case;
end process;
```

## The Case Statement for Figure 10-7

**Table 17-2. State Table for Code Converter**

<b>PS</b>	<b>NS</b>		<b>Z</b>	
	<b>X = 0</b>	<b>X = 1</b>	<b>X = 0</b>	<b>X = 1</b>
<b>S0</b>	<b>S1</b>	<b>S2</b>	<b>1</b>	<b>0</b>
<b>S1</b>	<b>S3</b>	<b>S4</b>	<b>1</b>	<b>0</b>
<b>S2</b>	<b>S4</b>	<b>S4</b>	<b>0</b>	<b>1</b>
<b>S3</b>	<b>S5</b>	<b>S5</b>	<b>0</b>	<b>1</b>
<b>S4</b>	<b>S5</b>	<b>S6</b>	<b>1</b>	<b>0</b>
<b>S5</b>	<b>S0</b>	<b>S0</b>	<b>0</b>	<b>1</b>
<b>S6</b>	<b>S0</b>	<b>-</b>	<b>1</b>	<b>-</b>

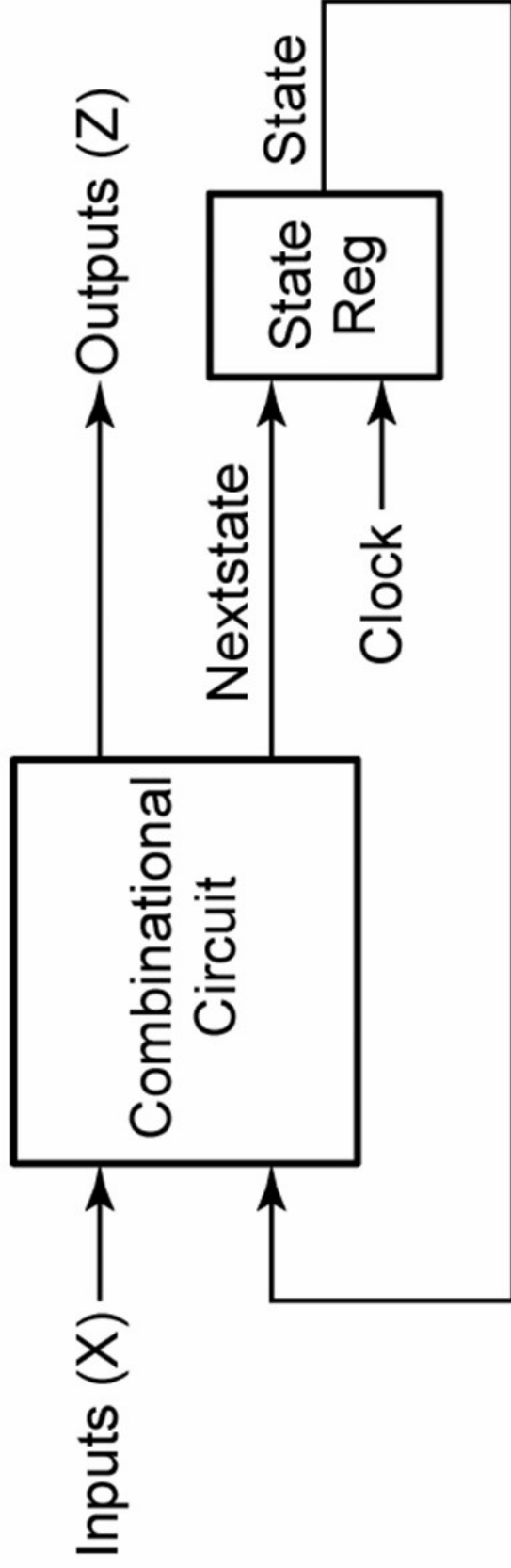

**Figure 17-15: General Model of Mealy Sequential Machine**

```

1 entity SM17_2 is
2   port(X, CLK: in bit;
3         Z: out bit);
4 end SM17_2;

5 architecture Table of SM17_2 is
6   signal State, Nextstate: integer range 0 to 6 := 0;
7 begin
8   process(State,X)                                --Combinational Circuit
9   begin
10    case State is
11    when 0 =>
12      if X='0' then Z<='1'; Nextstate<=1;
13      else Z<='0'; Nextstate<=2; end if;
14    when 1 =>
15      if X='0' then Z<='1'; Nextstate<=3;
16      else Z<='0'; Nextstate<=4; end if;
17    when 2 =>
18      if X='0' then Z<='0'; Nextstate<=4;
19      else Z<='1'; Nextstate<=4; end if;

```

**Figure 17-16a: Behavioral Model for Table 17-2**

©2004 Brooks/Cole



```

20  when 3 =>
21  if X='0' then Z<='0'; Nextstate<=5;
22  else Z<='1'; Nextstate<=5; end if;
23  when 4 =>
24  if X='0' then Z<='1'; Nextstate<=5;
25  else Z<='0'; Nextstate<=6; end if;
26  when 5 =>
27  if X='0' then Z<='0'; Nextstate<=0;
28  else Z<='1'; Nextstate<=0; end if;
29  when 6 =>
30  Z<='1'; Nextstate<=0;
31  end case;
32  end process;


33  process(CLK)           -- State Register
34  begin
35  if CLK'event and CLK='1' then  -- rising edge of clock
36  State <= Nextstate;
37  end if;
38  end process;
39  end Table;

```

**Figure 17-16b: Behavioral Model for Table 17-2**

©2004 Brooks/Cole



 

**Figure 17-17: Waveforms for Figure 17-16**



```

1 entity SM1_2 is
2   port(X,CLK: in bit;
3     Z: out bit);
4 end SM1_2;

5 architecture Equations1_4 of SM1_2 is
6   signal Q1,Q2,Q3: bit;
7 begin
8   process(CLK)
9   begin
10    if CLK'event and CLK='1' then -- rising edge of clock
11      Q1<=not Q2 after 10 ns;
12      Q2<=Q1 after 10 ns;
13      Q3<=(Q1 and Q2 and Q3) or (not X and Q1 and not Q3) or
14        (X and not Q1 and not Q2) after 10 ns;
15    end if;
16  end process;
17  Z<=(not X and not Q3) or (X and Q3) after 20 ns;
18 end Equations1_4;

```

**Figure 17-18. Sequential Machine Model Using Equations**



---

-- The following is a STRUCTURAL VHDL description  
-- of the circuit of Figure 16-4.

```
1 library BITLIB;  
2 use BITLIB.bit_pack.all;  
  
3 entity SM17_1 is  
4   port(X,CLK: in bit;  
5         Z: out bit);  
6 end SM17_1;
```


## ***Figure 17-19a: Structural Model of Sequential Machine***

```

7 architecture Structure of SM17_1 is
8   signal A1,A2,A3,A5,A6,D3: bit:= '0';
9   signal Q1,Q2,Q3: bit:= '0';
10  signal Q1N,Q2N,Q3N, XN: bit:= '1';
11 begin
12   I1: Inverter port map (X,XN);
13   G1: Nand3 port map (Q1,Q2,Q3,A1);
14   G2: Nand3 port map (Q1,Q3N,XN,A2);
15   G3: Nand3 port map (X,Q1N,Q2N,A3);
16   G4: Nand3 port map (A1,A2,A3,D3);
17   FF1: DFF port map (Q2N,CLK,Q1,Q1N);
18   FF2: DFF port map (Q1,CLK,Q2,Q2N);
19   FF3: DFF port map (D3,CLK,Q3,Q3N);
20   G5: Nand2 port map (X,Q3,A5);
21   G6: Nand2 port map (XN,Q3N,A6);
22   G7: Nand2 port map (A5,A6,Z);
23 end Structure;

```

**Figure 17-19b: Structural Model of Sequential Machine**

 

**Figure 17-20: Waveforms for Figure 16-4**



```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;

5 entity SM16_5 is
6   Port ( X : in std_logic;
7         CLK : in std_logic;
8         Z : out std_logic);
9 end SM16_5;
```

**Figure 17-21a: Sequential Machine Using a ROM**

```

10 architecture ROM of SM16_5 is
11 type ROM16X4 is array (0 to 15) of std_logic_vector(0 to 3);
12 constant ROM1: ROM16X4 := ("1001", "1011", "0100", "0101",
13     "1101", "0000", "1000", "0000",
14     "0010", "0100", "1100", "1101",
15     "0110", "1000", "0000", "0000");
16 signal Q, D: std_logic_vector (1 to 3) := "000";
17 signal Index, Romout: std_logic_vector (0 to 3);
18 begin
19 Index <= X&Q; -- X&Q is a 4-bit vector: X Q1 Q2 Q3
20 Romout <= ROM1 (conv_integer(Index));
    -- this statement reads the output from the ROM
    -- conv_integer converts Index to an Integer
21 Z <= Romout(0);
22 D <= Romout(1 to 3);

23 process (CLK)
24 begin
25     if CLK'event and CLK = '1' then Q <= D; end if;
26 end process;
27 end ROM;

```

**Figure 17-21b: Sequential Machine Using a ROM**


```

1 entity Table_13_4 is
2   port(X1, X2, CLK: in bit; Z1, Z2: out bit);
3 end Table_13_4;

4 architecture T1 of Table_13_4 is
5   signal State, Nextstate: integer range 0 to 3:= 0;
6   signal X12: bit_vector(0 to 1);
7 begin
8   X12 <= X1&X2;
9   process(State, X12)
10  begin
11    case State is
12    when 0 =>
13      case X12 is
14      when "00" => Nextstate <= 3; Z1 <= '0'; Z2 <= '0';
15      when "01" => Nextstate <= 2; Z1 <= '1'; Z2 <= '0';
16      when "10" => Nextstate <= 1; Z1 <= '1'; Z2 <= '1';
17      when "11" => Nextstate <= 0; Z1 <= '0'; Z2 <= '1';
18      when others => null -- not required since X is a bit_vector
19    end case;
20    when 1 =>    -- code for state 1 goes here, etc.

```

**Figure 17-22 Partial VHDL Code for the Table of Figure 13-4**

 

**Figure 17-23: Synthesis of VHDL Code from Figure 17-9**



```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_UNSIGNED.ALL;


4 entity adder is
5   Port (B : in std_logic_vector(3 downto 0);
6        Ld, Ad, Cin, CLK : in std_logic;
7        Aout : out std_logic_vector(3 downto 0);
8        Cout : out std_logic);
9 end adder;
```

*Figure 17-24a:*  
**VHDL Code for 4-Bit Adder  
with Accumulator**

```
10 architecture Behavioral of adder is
11 signal A : std_logic_vector(3 downto 0);
12 signal Addout : std_logic_vector(4 downto 0);
13 begin
14   Addout <= ('0' & A) + B + Cin;
15   Cout <= Addout(4);
16   Aout <= A;
17 process(CLK)
18 begin
19   if CLK'event and CLK = '1' then
20     if Ld = '1' then A <= B;
21     elsif Ad = '1'
22       then A <= Addout(3 downto 0);
23     end if;
24   end if;
25 end process;
26 end Behavioral;
```

*Figure 17-24b:*  
**VHDL Code for 4-Bit Adder  
with Accumulator**



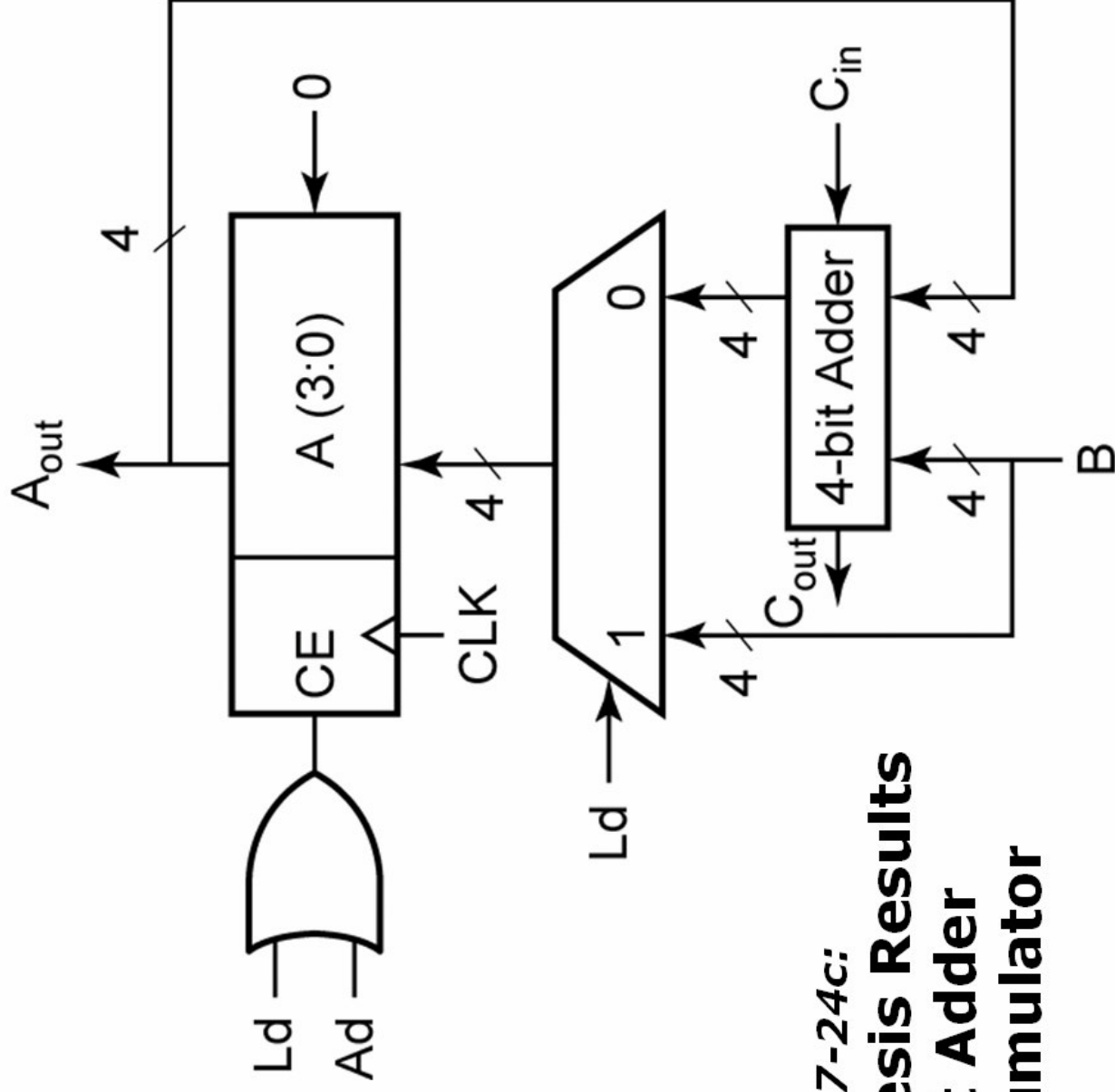

**Figure 17-24c:**  
**VHDL Synthesis Results**  
**for 4-Bit Adder**  
**with Accumulator**