 


FIGURES FOR CHAPTER 18

CIRCUITS FOR ARITHMETIC OPERATIONS



This chapter in the book includes:

- Objectives
- Study Guide
- 18.1 Serial Adder with Accumulator
- 18.2 Design of a Parallel Multiplier
- 18.3 Design of a Binary Divider
- Programmed Exercises
- Problems

Click the mouse to move to the next page.
Use the ESC key to exit this chapter.

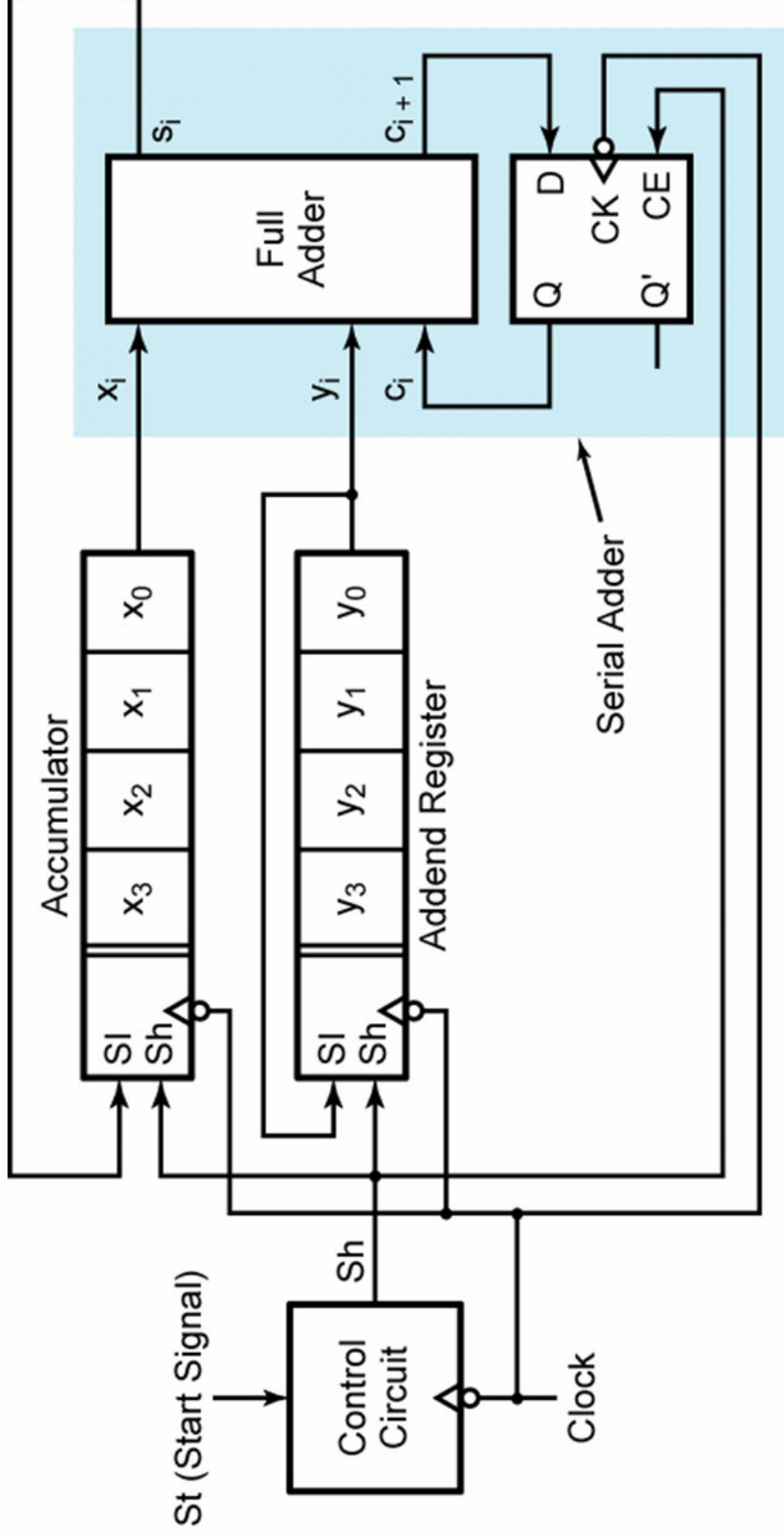


Figure 18-1: Block Diagram for Serial Adder with Accumulator

Figure 18-2ab:
Operation of
Serial Adder



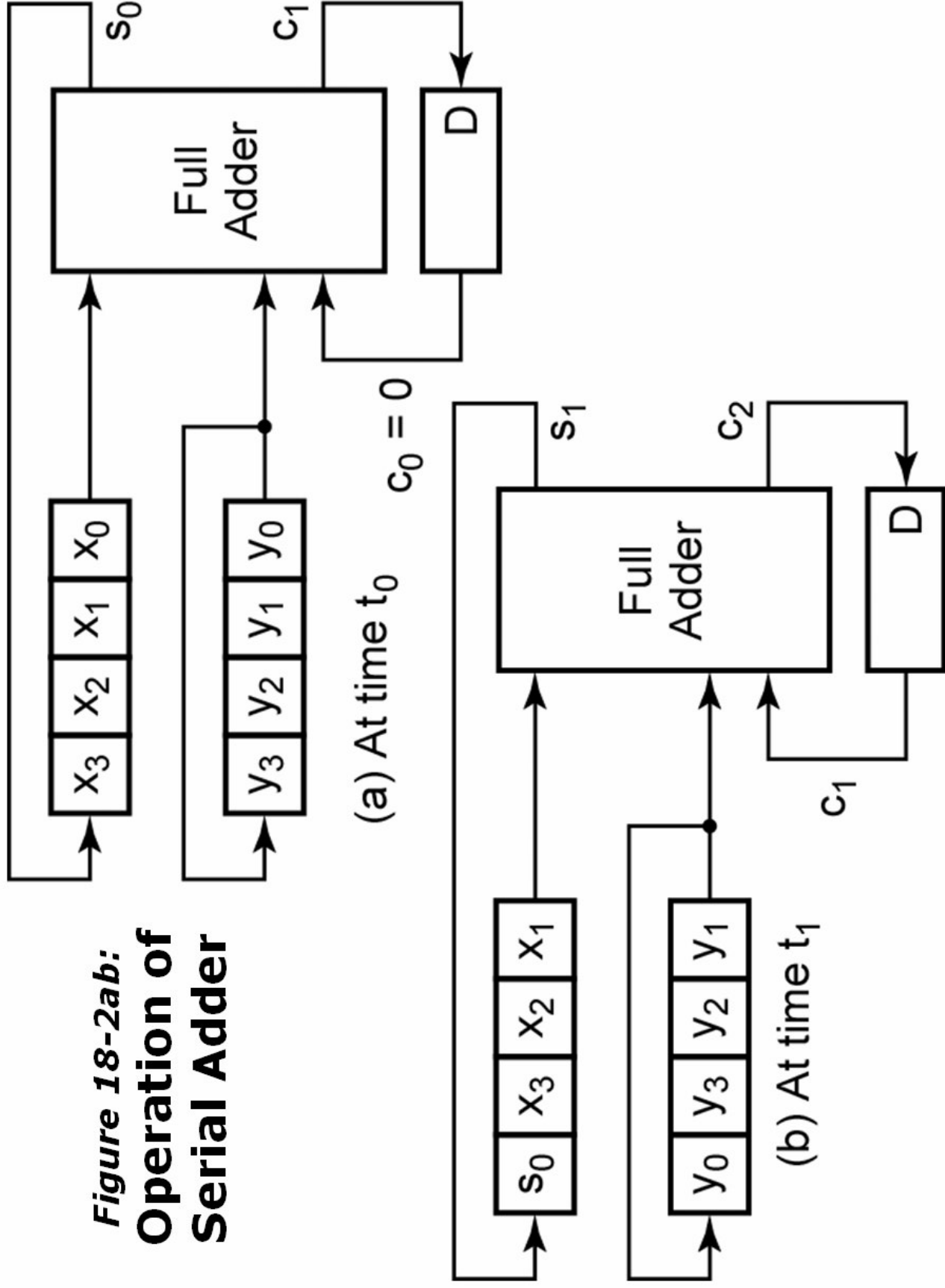


Figure 18-2cd:
Operation of
Serial Adder

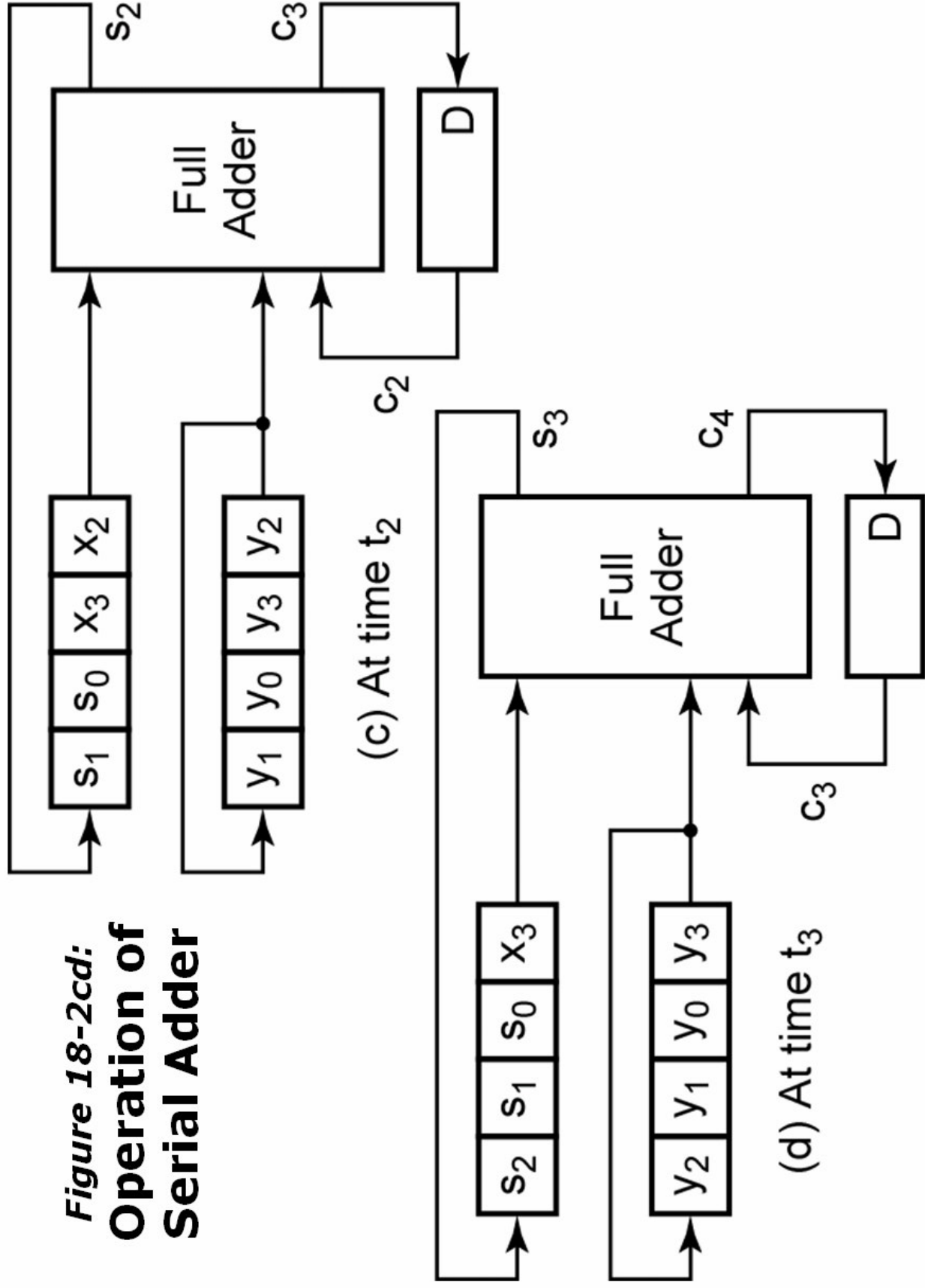

 


(e) At time t_4

Figure 18-2c:
Operation of
Serial Adder

Table 18-1 Operation of Serial Adder

	X	Y	c_i	s_i	c_i^+
t_0	0101	0111	0	0	1
t_1	0010	1011	1	0	1
t_2	0001	1101	1	1	1
t_3	1000	1110	1	1	0
t_4	1100	0111	0	(1)	(0)

 


Next State		Sh
St = 0	1	0 1
S ₀	S ₁	0 1
S ₁	S ₂	1 1
S ₂	S ₃	1 1
S ₃	S ₀	1 1

Figure 18-3: State Graph for Serial Adder Control




	AB	A⁺B⁺
	0	1
S₀	00	01
S₁	01	10
S₂	10	11
S₃	11	00

Figure 18-4a: Derivation of Control Circuit Equations

 


$$D_A = A'B + AB'$$

$$= A \oplus B$$

 

$$D_B = St B' + AB'$$

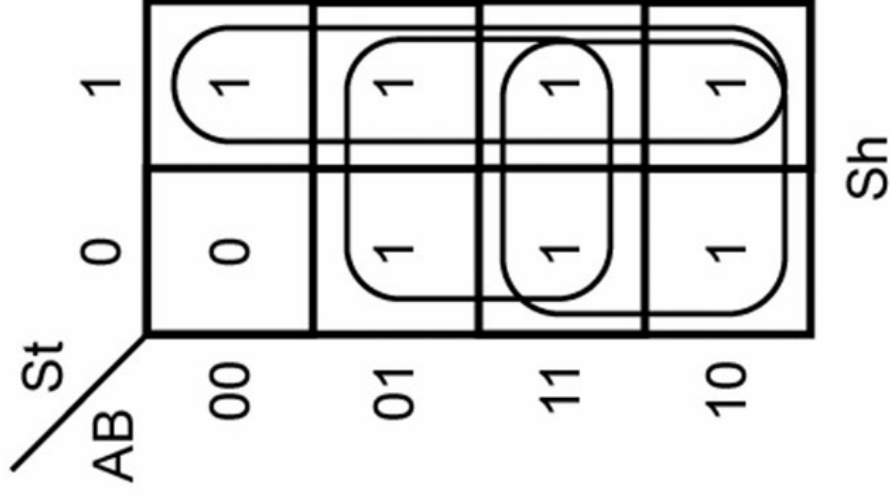

$$Sh = St + A + B$$

Figure 18-4b: Derivation of Control Circuit Equations




 


Figure 18-5: Typical Serial Processing Unit

 

(a)

(b)

Figure 18-6: State Graphs for Serial Processing Unit

 


Figure 18-7: Block Diagram for Parallel Binary Multiplier

Parallel Binary Multiplication

initial contents of product register	0 0 0 0 0 1 0 1 1 ← M	(11)
(add multiplicand since $M = 1$)	$\begin{array}{r} 0 0 0 0 0 1 0 1 1 \\ 1 1 0 1 \\ \hline 0 1 1 0 1 1 0 1 1 \end{array}$	(13)
after addition		
after shift	$\begin{array}{r} 0 0 1 1 0 1 1 0 1 1 \\ 0 0 1 1 0 1 1 0 1 \\ \hline 0 1 0 0 1 1 1 0 1 \end{array}$	← M
(add multiplicand since $M = 1$)	$\begin{array}{r} 0 1 0 0 1 1 1 0 1 \\ 1 1 0 1 \\ \hline 1 0 0 1 1 1 1 0 1 \end{array}$	
after addition		
after shift	$\begin{array}{r} 0 1 0 0 1 1 1 0 1 \\ 0 1 0 0 1 1 1 1 0 \\ \hline 0 0 1 0 0 1 1 1 1 0 \end{array}$	← M
(skip addition since $M = 0$)		
after shift	$\begin{array}{r} 0 0 1 0 0 1 1 1 1 0 \\ 0 0 1 0 0 1 1 1 1 \\ \hline 0 0 1 0 0 1 1 1 1 1 \end{array}$	← M
(add multiplicand since $M = 1$)	$\begin{array}{r} 0 0 1 0 0 1 1 1 1 1 \\ 1 1 0 1 \\ \hline 1 0 0 0 1 1 1 1 1 \end{array}$	
after addition		
after shift (final answer)	$\begin{array}{r} 1 0 0 0 1 1 1 1 1 \\ 0 1 0 0 0 1 1 1 1 \\ \hline 0 1 0 0 0 1 1 1 1 \end{array}$	(143)

dividing line between product and multiplier


 



Figure 18-8: State Graph for Multiplier Control

 



(a) Multiplier control

Figure 18-9

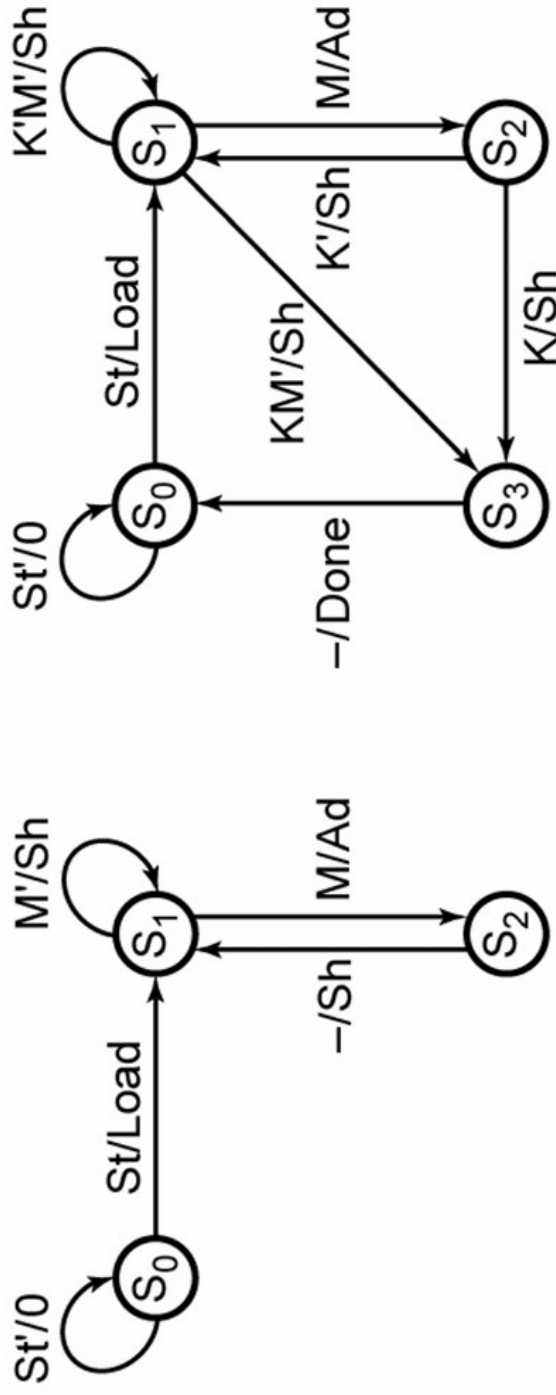

(b) State graph for add-shift control

(c) Final state graph for add-shift control

Table 18.2 Operation of a Multiplier Using a Counter

Time	State	Counter	Product Register	St	M	K	Load	Ad	Sh	Done
t_0	S_0	00	00000000	0	0	0	0	0	0	0
t_1	S_0	00	00000000	1	0	0	1	0	0	0
t_2	S_1	00	000001011	0	1	0	0	1	0	0
t_3	S_2	00	011011011	0	1	0	0	0	1	0
t_4	S_1	01	001101101	0	1	0	0	1	0	0
t_5	S_2	01	100111101	0	1	0	0	0	1	0
t_6	S_1	10	010011110	0	0	0	0	0	1	0
t_7	S_1	11	001001111	0	1	1	0	1	0	0
t_8	S_2	11	100011111	0	1	1	0	0	1	0
t_9	S_3	00	010001111	0	1	0	0	0	0	1

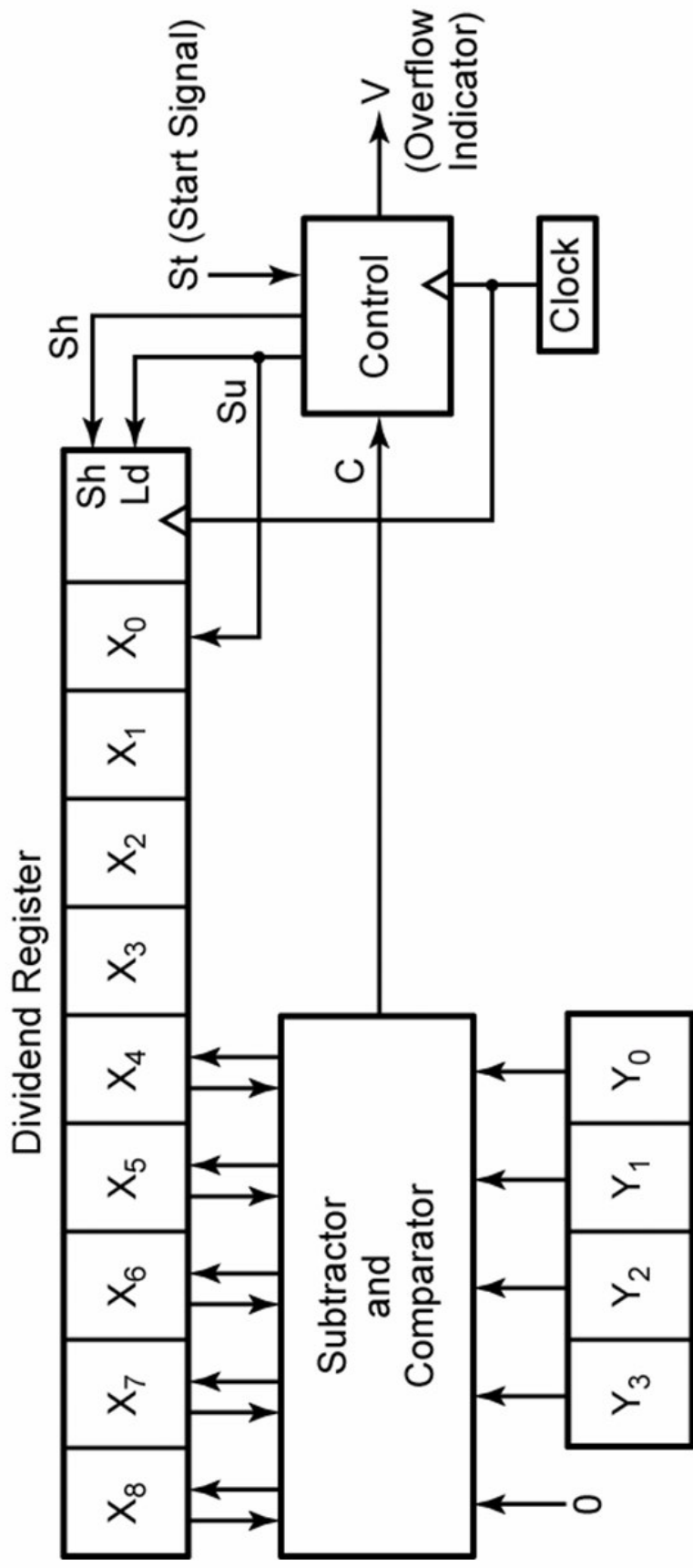


Figure 18-10: Block Diagram for Parallel Binary Divider

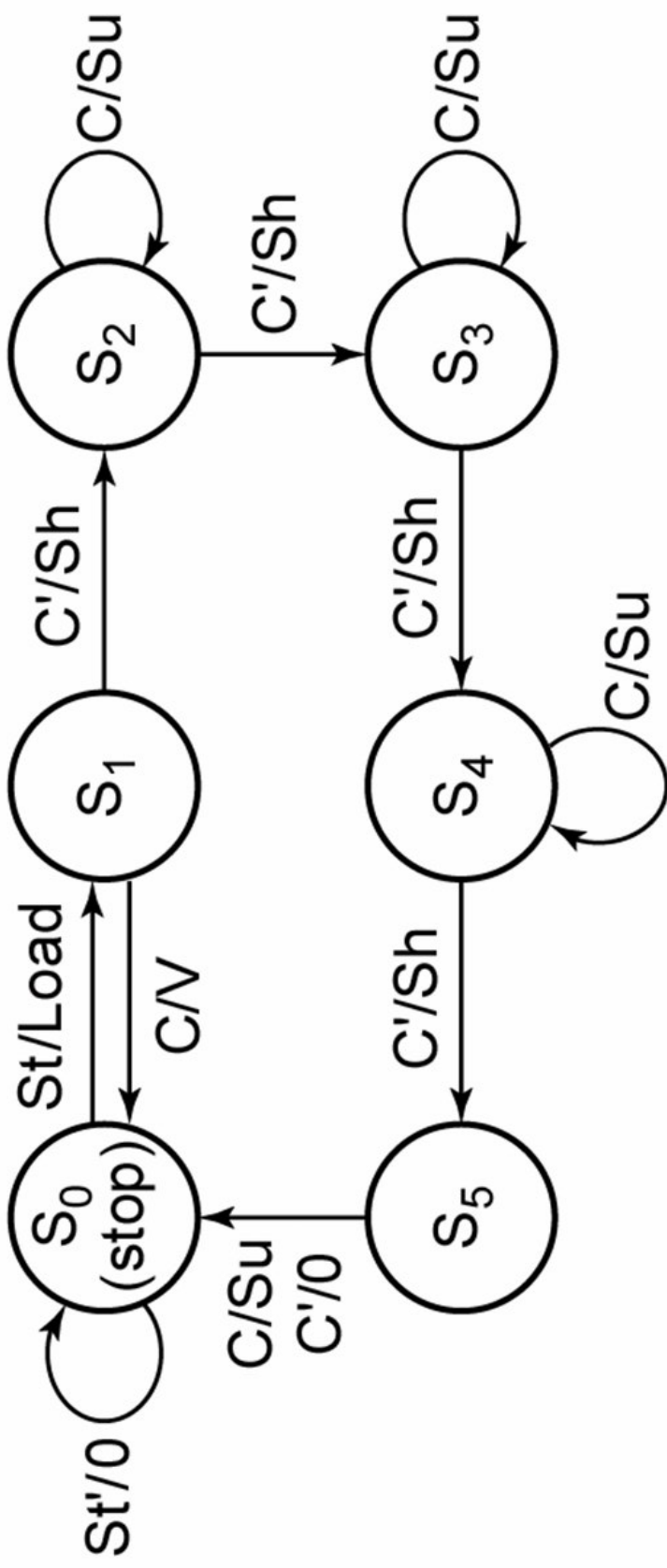


Figure 18-11: State Graph for Divider Control Circuit


 
 


Figure 18-12: Logic Diagram for 5-Bit Subtracter

 

Bus Merger

Bus Splitter

Section 18.3, p. 550



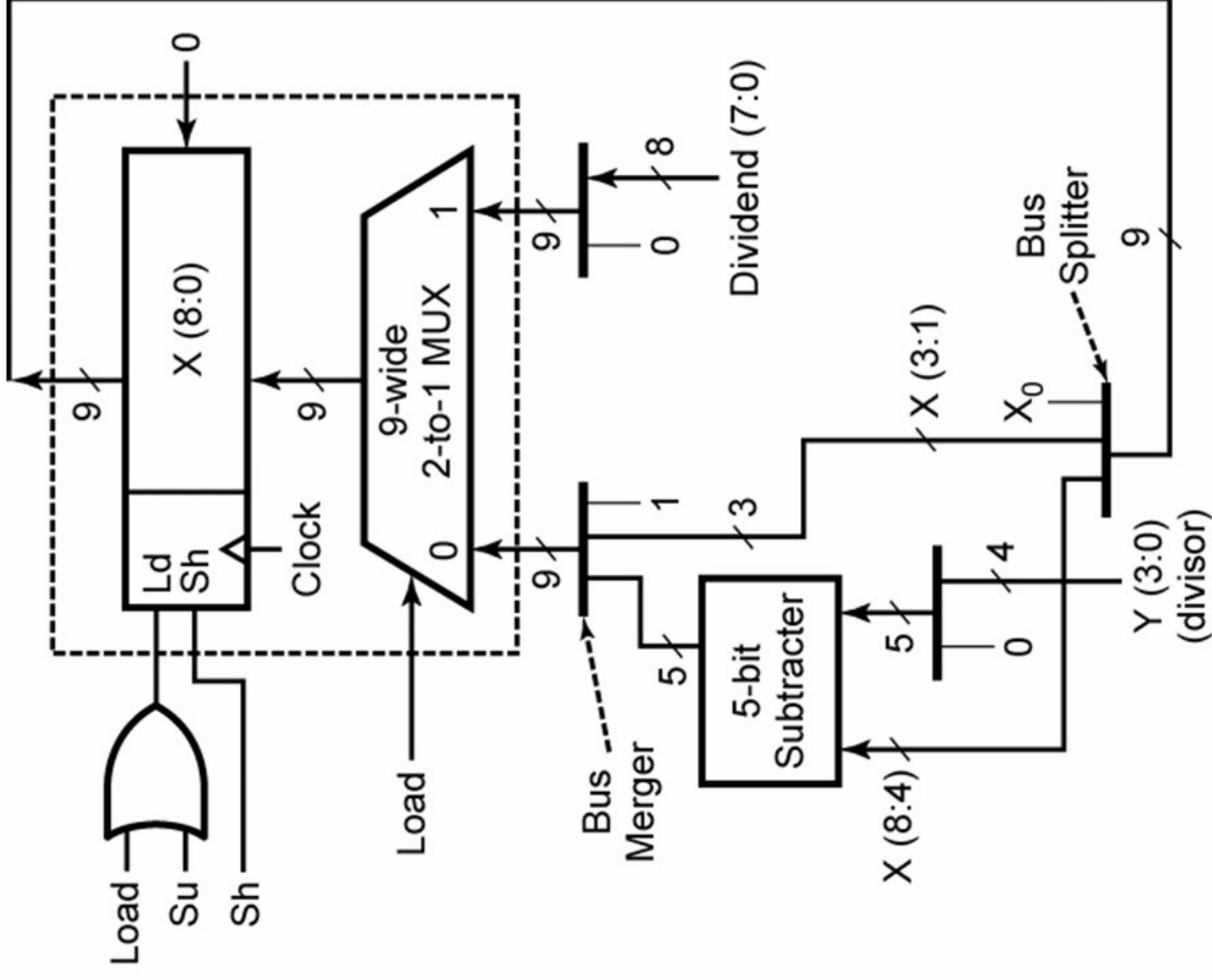


Figure 18-13:
Block Diagram for
Divider Using Bus
Notation