 


FIGURES FOR CHAPTER 20

VHDL FOR DIGITAL SYSTEM DESIGN



This chapter in the book includes:

- Objectives
- Study Guide
- 20.1 VHDL Code for a Serial Adder
- 20.2 VHDL Code for a Binary Multiplier
- 20.3 VHDL Code for a Binary Divider
- 20.4 VHDL Code for a Dice Game Simulator
- 20.5 Concluding Remarks
- Problems
- Lab Design Problems

Click the mouse to move to the next page.
Use the ESC key to exit this chapter.

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;

3 entity serial is
4   Port ( St : in std_logic;
5         Clk : in std_logic;
6         Xout: out std_logic_vector(3 downto 0));
7 end serial;

8 architecture Behavioral of serial is
9   signal X, Y: std_logic_vector(3 downto 0);
10  signal Sh: std_logic;
11  signal Ci, Ciplus : std_logic;
12  signal Sumi: std_logic;
13  signal State, NextState : integer range 0 to 3;    -- 4 states
```

Figure 20-1a. VHDL Code for Figure 18-1

```

14 begin
15     Sumi <= X(0) xor Y(0) xor Ci;           -- full adder
16     Ciplus <= (Ci and X(0)) or (Ci and Y(0)) or (X(0) and Y(0));
17     Xout <= X;
18 process (State, St)
19 begin
20     case State is
21         when 0 =>
22             if St = '1' then Sh <= '1'; Nextstate <= 1;
23             else Sh <= '0'; NextState <= 0; end if;
24             when 1 => Sh <= '1'; NextState <= 2;
25             when 2 => Sh <= '1'; NextState <= 3;
26             when 3 => Sh <= '1'; NextState <= 0;
27         end case;
28     end process;

```

Figure 20-1b. VHDL Code for Figure 18-1

```

29 process (clk)
30 begin
31   if clk'event and clk = '0' then
32     State <= Nextstate;    -- update state register
33     if Sh = '1' then
34       X <= Sumi & X(3 downto 1);    -- shift Sumi into X register
35       Y <= Y (0) & Y(3 downto 1);  -- rotate right Y register
36       Ci <= Ciplus; end if;      -- store next carry
37     end if;
38   end process;
39 end Behavioral;

```

Figure 20-1c. VHDL Code for Figure 18-1

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;

5 entity mult4X4 is
6   port (Clk, St: in std_logic;
7         Mplier, Mcand : in std_logic_vector(3 downto 0);
8         Done: out std_logic;
9         Product: out std_logic_vector (7 downto 0));
10 end mult4X4;
```

Figure 20-2a.
Behavioral VHDL Code for Multiplier of Figure 18-6

```

11 architecture behave1 of mult4X4 is
12   signal State: integer range 0 to 9;
13   signal ACC: std_logic_vector(8 downto 0); --accumulator
14   alias M: std_logic is ACC(0); --M is bit 0 of ACC
15 begin
16   Product <= ACC (7 downto 0);
17   process (Clk)
18   begin
19     if Clk'event and Clk = '1' then --executes on rising edge of clock
20       case State is
21       when 0=> --initial State
22         if St='1' then
23           ACC(8 downto 4) <= "00000"; --clear upper ACC
24           ACC(3 downto 0) <= Mplier; --load the multiplier
25           State <= 1;
26         end if;

```

Figure 20-2b.
Behavioral VHDL Code for Multiplier of Figure 18-6

```

27  when 1 | 3 | 5 | 7 =>      --"add/shift" State
28  if M = '1' then          --Add multiplicand to ACC
29  ACC(8 downto 4) <= ('0' & ACC(7 downto 4)) + Mcand;
30  State <= State+1;
31  else ACC <= '0' & ACC(8 downto 1); --Shift accumulator right
32  State <= State + 2;
33  end if;
34  when 2 | 4 | 6 | 8 =>      --"shift" State
35  ACC <= '0' & ACC(8 downto 1); --Right shift
36  State <= State + 1;
37  when 9 =>                --end of cycle
38  State <= 0;
39  end case;
40  end if;
41  end process;
42  Done <= '1' when State = 9 else '0';
43  end behave1;

```

Figure 20-2c.

Behavioral VHDL Code for Multiplier of Figure 18-6



```
-- command file to test multiplier
view list
add list CLK St State ACC done product
force st 1 2, 0 22
force clk 1 0, 0 10 -repeat 20
force Mcand 1101
force Mplier 1011
run 200
```

Figure 20-3a.
Command File for (13 by 11)

ns	delta	clk	st	state	ACC	done	product
0	+1	1	U	0	UUUUUUUU	0	UUUUUUUU
2	+0	1	1	0	UUUUUUUUU	0	UUUUUUUUU
10	+0	0	1	0	UUUUUUUUU	0	UUUUUUUUU
20	+2	1	1	1	000001011	0	00001011
22	+0	1	0	1	000001011	0	00001011
30	+0	0	0	1	000001011	0	00001011
40	+2	1	0	2	011011011	0	11011011
50	+0	0	0	2	011011011	0	11011011
60	+2	1	0	3	001101101	0	01101101
70	+0	0	0	3	001101101	0	01101101
80	+2	1	0	4	100111101	0	00111101
90	+0	0	0	4	100111101	0	00111101
100	+2	1	0	5	010011110	0	10011110
110	+0	0	0	5	010011110	0	10011110
120	+2	1	0	7	001001111	0	01001111
130	+0	0	0	7	001001111	0	01001111
140	+2	1	0	8	100011111	0	00011111
150	+0	0	0	8	100011111	0	00011111
160	+2	1	0	9	010001111	1	10001111
170	+0	0	0	9	010001111	1	10001111
180	+0	1	0	0	010001111	0	10001111
190	+0	0	0	0	010001111	0	10001111
200	+0	1	0	0	010001111	0	10001111

Figure 20-3b.
Simulation Results for (13 by 11)

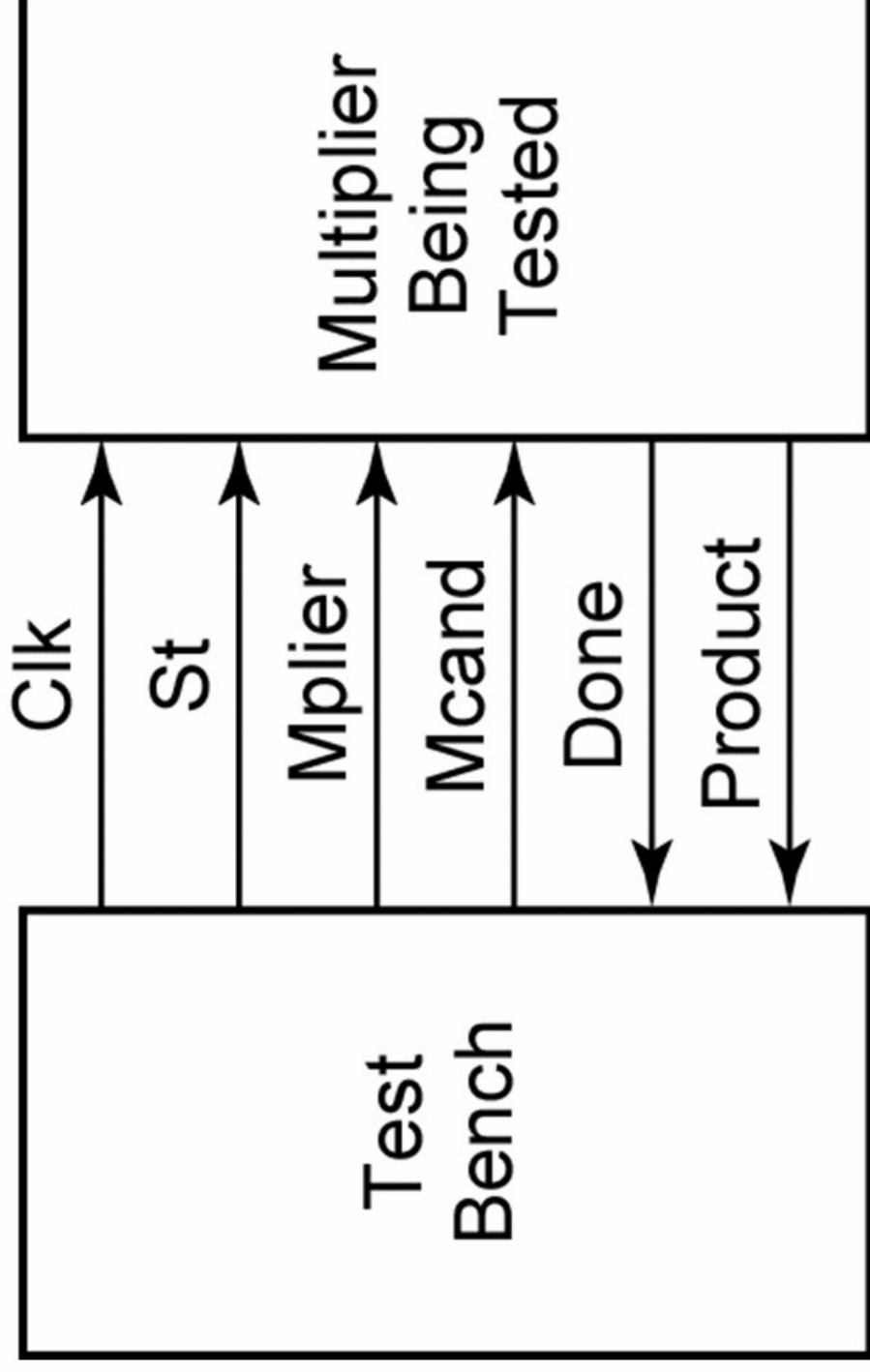


Figure 20-4: Test Bench for Multiplier

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;
5 entity testmult is
6 end testmult;
7 architecture test1 of testmult is
8 component mult4X4
9 port (Clk: in std_logic;
10      St: in std_logic;
11      Mplier,Mcand : in std_logic_vector(3 downto 0);
12      Product: out std_logic_vector (7 downto 0);
13      Done: out std_logic);
14 end component;
15 constant N: integer := 6;
16 type arr is array(1 to N) of std_logic_vector(3 downto 0);
17 constant Mcandarr: arr :=
           ("1011", "1101", "0001", "1000", "1111", "1101");
18 constant Mplierarr: arr :=
           ("1101", "1011", "0001", "1000", "1111", "0000");
```

Figure 20-5a. Testbench for Multiplier



```

19 signal CLK: std_logic :='0';
20 signal St, Done: std_logic;
21 signal Mplier, Mcand: std_logic_vector(3 downto 0);
22 signal Product: std_logic_vector(7 downto 0);
23 begin
24   mult1: mult4X4 port map(CLK, St, Mplier, Mcand, Product, Done);
25   CLK <= not CLK after 10 ns; -- clock has 20 ns period
26 process
27 begin
28   for i in 1 to N loop
29     Mcand <= Mcandarr(i);
30     Mplier <= Mplierarr(i);
31     St <= '1';
32     wait until CLK = '1' and CLK'event;
33     St <= '0';
34     wait until done = '1';
35     wait until CLK = '1' and CLK'event;
36   end loop;
37 end process;
38 end test1;

```

Figure 20-5b.
Testbench for Multiplier

```
-- Command file to test multiplier
view list
add list -NOtrigger Mplier Mcand product -Trigger done
run 1320 ns
```

Figure 20-6a. Command File and Simulation of Multiplier

ns	+delta	mcand	mplier	product	done
0	+0	UUUU	UUUU	UUUUUUUU	U
0	+1	1011	1101	UUUUUUUU	0
150	+2	1011	1101	10001111	1
170	+2	1011	1101	10001111	0
330	+2	1101	1011	10001111	1
350	+2	1101	1011	10001111	0
470	+2	0001	0001	00000001	1
490	+2	0001	0001	00000001	0
610	+2	1000	1000	01000000	1
630	+2	1000	1000	01000000	0
810	+2	1111	1111	11100001	1
830	+2	1111	1111	11100001	0
930	+2	1101	0000	00000000	1

11 x 13 = 143
 13 x 11 = 143
 1 x 1 = 1
 8 x 8 = 64
 15 x 15 = 225
 13 x 0 = 0

Figure 20-6b. Command File and Simulation of Multiplier



```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3 use IEEE.STD_LOGIC_ARITH.all;
4 use IEEE.STD_LOGIC_UNSIGNED.all;
5 entity mult4X4 is
6   port (Clk, St: in std_logic;
7         Mplier, Mcand : in std_logic_vector(3 downto 0);
8         Product: out std_logic_vector (7 downto 0);
9         Done: out std_logic);
10 end mult4X4;

11 architecture control_signals of mult4X4 is
12   signal State, Nextstate: integer range 0 to 9;
13   signal ACC: std_logic_vector(8 downto 0);
14   alias M: std_logic is ACC(0);
15   signal addout: std_logic_vector(4 downto 0);
16   signal Load, Ad, Sh: std_logic;

```

Figure 20-7a. Two-process VHDL Model for Multiplier

```

17 Begin
18   Product <= ACC (7 downto 0);
19   addout <= ('0' & ACC(7 downto 4)) + Mcand;
    -- uses "+" operator from the ieee_std_logic_unsigned package
20 process(State, St, M)
21 begin
22   Load <='0'; Ad<='0'; Sh <='0'; Done <='0';
23   case State is
24     when 0 =>
25       if St='1' then Load <='1'; Nextstate <= 1;
26       else Nextstate <= 0; end if;
27     when 1 | 3 | 5 | 7 =>      --"add/shift" State
28       if M = '1' then Ad <='1'; --Add multiplicand
29       Nextstate <= State + 1;
30       else Sh <='1'; Nextstate <= State + 2; end if;

```

Figure 20-7b. Two-process VHDL Model for Multiplier


```

31  when 2 | 4 | 6 | 8 =>    --"shift" State
32      Sh <='1'; Nextstate <= State + 1;
33  when 9 => Done <= '1'; Nextstate <= 0;
34  end case;
35  end process;

36  process (CLK)          --Register update process
37  begin
38  if Clk'event and Clk = '1' then --executes on rising edge of clock
39  if Load = '1' then ACC(8 downto 4) <= "00000";
40      ACC(3 downto 0) <= Mplier; end if; --load the multiplier
41  if Ad = '1' then ACC(8 downto 4) <= addout; end if;
42  if Sh = '1' then ACC <= '0' & ACC(8 downto 1); end if;
43      -- Shift accumulator right
44  State <= Nextstate;
45  end if;
46  end process;
end control_signals;

```

Figure 20-7c. Two-process VHDL Model for Multiplier



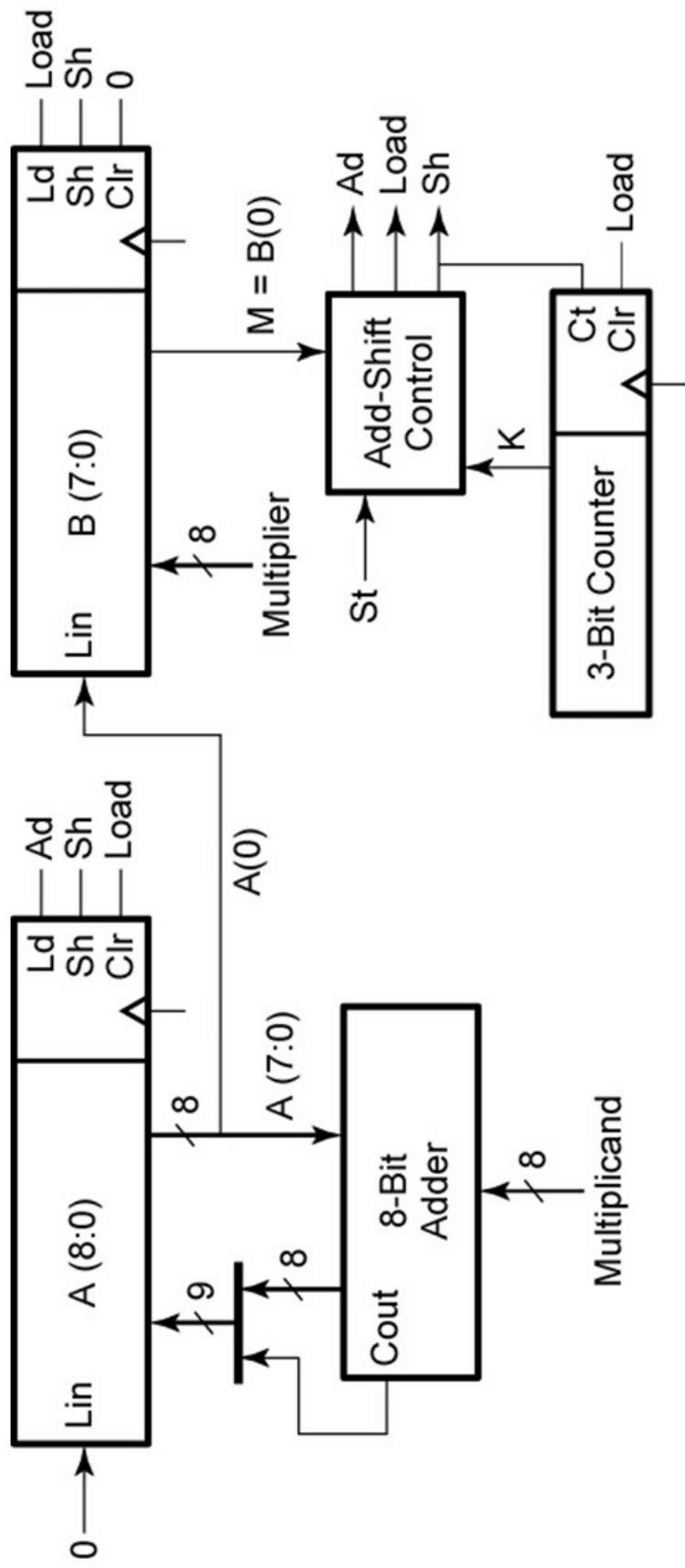


Figure 20-8: Block Diagram for 8 x 8 Binary Multiplier

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3 use IEEE.STD_LOGIC_ARITH.all;
4 use IEEE.STD_LOGIC_UNSIGNED.all;

5 entity mult8X8 is
6   Port (CLK, St: in std_logic;
7         Mplier, Mcand : in std_logic_vector(7 downto 0);
8         Done : out std_logic;
9         Product: out std_logic_vector(15 downto 0));
10 end mult8X8;
```

Figure 20-9a. VHDL Code for Multiplier with Shift Counter

```

11 architecture Behavioral of mult8X8 is
12   signal State, NextState: integer range 0 to 3;
13   signal count: std_logic_vector (2 downto 0):="000"; -- 3-bit counter
14   signal A: std_logic_vector (8 downto 0);      -- accumulator
15   signal B: std_logic_vector (7 downto 0);
16   alias M: std_logic is B(0);      -- M is bit 0 of B
17   signal addout: std_logic_vector (8 downto 0);
18   signal K, Load, Ad, Sh: std_logic;
19   begin
20     Product <= A(7 downto 0) & B; -- 16-bit product is in A and B
21     addout <= '0' & A(7 downto 0) + Mcand; -- adder output is 9 bits
                                           -- including carry
22     K <= '1' when count = 7 else '0';
23     process (St, State, K, M)
24     begin

```

Figure 20-9b. VHDL Code for Multiplier with Shift Counter

```

25 Load <= '0'; Sh <='0'; Ad <='0'; Done <='0';
    -- control signals are '0' by default
26 case State is
27 when 0 =>
28     if St = '1' then Load <= '1'; NextState <= 1;
29     else NextState <= 0; end if;
30 when 1 =>
31     if M = '1' then Ad <= '1'; NextState <= 2;
32     else if K = '0' then Sh <= '1'; NextState <= 1;
33         else Sh <= '1'; NextState <= 3; end if;
34     end if;
35 when 2 =>
36     if K = '0' then Sh <= '1'; NextState <= 1;
37     else Sh <= '1'; NextState <= 3; end if;
38 when 3 =>
39     Done <='1'; NextState <= 0;
40 end case;
41 end process;

```

Figure 20-9c. VHDL Code for Multiplier with Shift Counter



```

42 process (clk)
43 begin
44   if clk'event and clk = '1' then
45     if load = '1' then
46       A <= "0000000000"; Count <= "000"; -- clear A and counter
47       B <= Mplier;
48     end if; -- load multiplier
49     if Ad = '1' then A <= addout; end if;
50     if Sh = '1' then
51       A <= '0' & A(8 downto 1); B <= A(0) & B(7 downto 1);
52       -- right shift A and B
53       count <= count +1; -- increment counter
54       -- uses "+" operator from ieee_std_logic_unsigned package
55     end if;
56     State <= NextState;
57   end if;
58 end process;
end Behavioral;

```

Figure 20-9d. VHDL Code for Multiplier with Shift Counter



```

add wave clk st state count a b done product
force st 1 2, 0 22
force clk 1 0, 0 10 --repeat 20
force mcand 00001011
force mplier 00001101
run 280

```

 


Figure 20-10: Command File and Simulation of 8 x 8 Multiplier



```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3 use IEEE.STD_LOGIC_ARITH.all;
4 use IEEE.STD_LOGIC_UNSIGNED.all;

5 entity Divider is
6 Port (Dividend_in: in std_logic_vector(7 downto 0);
7       Divisor: in std_logic_vector(3 downto 0);
8       St, Clk: in std_logic;
9       Quotient: out std_logic_vector(3 downto 0);
10      Remainder: out std_logic_vector(3 downto 0);
11      Overflow : out std_logic);
12 end Divider;

13 architecture Behavioral of Divider is
14 signal State, NextState: integer range 0 to 5;
15 signal C, Load, Su, Sh: std_logic;
16 signal Subout : std_logic_vector (4 downto 0);
17 signal Dividend: std_logic_vector (8 downto 0);

```

Figure 20-11a. VHDL Code for Divider




```

18 begin
19   Subout <= Dividend(8 downto 4) - ('0' & divisor);
20   C <= not Subout (4);
21   Remainder <= Dividend (7 downto 4);
22   Quotient <= Dividend (3 downto 0);

23 State_Graph: process (State, St, C)
24 begin
25   Load <= '0'; Overflow <='0'; Sh <= '0'; Su <= '0';
26   case State is
27     when 0 =>
28       if (St = '1') then Load <='1'; NextState <= 1;
29       else Nextstate <= 0; end if;
30     when 1 =>
31       if (C = '1') then Overflow <='1'; NextState <= 0;
32       else Sh <= '1'; NextState <= 2; end if;
33     when 2 | 3 | 4 =>
34       if (C = '1') then Su <= '1'; NextState <= State;
35       else Sh <= '1'; NextState <= State + 1; end if;

```

Figure 20-11b. VHDL Code for Divider



```

36  when 5 =>
37  if (C = '1') then Su <= '1'; end if;
38  NextState <= 0;
39  end case;
40  end process State_Graph;
41  Update: process (CLK)
42  begin
43  if CLK'event and CLK = '1' then           -- rising edge of CLK
44  State <= NextState;
45  if Load = '1' then Dividend <= '0' & Dividend_in; end if;
46  if Su = '1' then Dividend(8 downto 4) <= Subout; Dividend(0) <= '1';
      end if;
47  if Sh = '1' then Dividend <= Dividend (7 downto 0) & '0'; end if;
48  end if;
49  end process update;
50  end Behavioral;

```

Figure 20-11c. VHDL Code for Divider



```
1 entity DiceGame is
2   port (Rb, Reset, CLK: in bit;
3     Sum: in integer range 2 to 12;
4     Roll, Win, Lose: out bit);
5 end DiceGame;

6 architecture DiceBehave of DiceGame is
7   signal State, Nextstate: integer range 0 to 5;
8   signal Point: integer range 2 to 12;
9   signal Sp: bit;
10  begin
11    process(Rb, Reset, Sum, State)
12  begin
13    Sp <= '0'; Roll <= '0'; Win <= '0'; Lose <= '0';
```

Figure 20-12a VHDL Code for Dice Game Controller



```

14 case State is
15   when 0 =>
16     if Rb = '1' then Nextstate <= 1; else nextstate <= 0; end if;
17     when 1 =>
18       if Rb = '1' then Roll <= '1'; Nextstate <= 1;
19       elsif Sum = 7 or Sum = 11 then Nextstate <= 2;
20       elsif Sum = 2 or Sum = 3 or Sum = 12 then Nextstate <= 3;
21       else Sp <= '1'; Nextstate <= 4;
22     end if;
23   when 2 => Win <= '1';
24   if Reset = '1' then Nextstate <= 0; else nextstate <= 2; end if;
25   when 3 => Lose <= '1';
26   if Reset = '1' then Nextstate <= 0; else nextstate <= 3; end if;
   when 4 => if Rb = '1' then Nextstate <= 5; else nextstate <= 4;
           end if;

```

Figure 20-12b VHDL Code for Dice Game Controller

```

27  when 5 =>
28  if Rb = '1' then Roll <= '1'; Nextstate <= 5;
29  elsif Sum = Point then Nextstate <= 2;
30  elsif Sum = 7 then Nextstate <= 3;
31  else Nextstate <= 4;
32  end if;
33  end case;
34  end process;
35  process(CLK)
36  begin
37  if CLK'event and CLK = '1' then
38  State <= Nextstate;
39  if Sp = '1' then Point <= Sum; end if;
40  end if;
41  end process;
42  end DiceBehave;

```

Figure 20-12c VHDL Code for Dice Game Controller



```

1 entity Counter is
2 port(Clk, Roll: in bit;
3   Sum: out integer range 2 to 12);
4 end Counter;

5 architecture Count of Counter is
6 signal Cnt1, Cnt2: integer range 1 to 6 := 1;
7 begin
8   process (Clk)
9   begin
10    if Clk'event and Clk='1' then
11    if Roll='1' then
12    if Cnt1=6 then Cnt1 <= 1; else Cnt1 <= Cnt1+1; end if;
13    if Cnt1=6 then
14    if Cnt2=6 then Cnt2 <= 1; else Cnt2 <= Cnt2+1; end if;
15    end if;
16    end if;
17    end if;
18  end process;
19  Sum <= Cnt1 + Cnt2;
20 end Count;

```

**Figure 20-13 Counter
Module for Dice Game**

```
1 entity Game is
2   port (Rb, Reset, Clk: in bit;
3     Win, Lose: out bit);
4 end Game;

5 architecture Play1 of Game is
6   component Counter
7     port(Clk, Roll: in bit;
8       Sum: out integer range 2 to 12);
9   end component;
10  component DiceGame
11    port (Rb, Reset, CLK: in bit;
12      Sum: in integer range 2 to 12;
13      Roll, Win, Lose: out bit);
14  end component;
15  signal roll1: bit;
16  signal sum1: integer range 2 to 12;
17  begin
18    Dice: Dicegame port map(Rb,Reset,Clk,sum1,roll1,Win,Lose);
19    Count: Counter port map(Clk,roll1,sum1);
20  end Play1;
```

**Figure 20-14 Main
Module for Dice Game**

Table 20-1 Synthesis Results (optimized for area)

Device	Multiplier Fig. 20-2	Multiplier Fig. 20-7	Multiplier Fig. 20-9	Divider Fig. 20-11	Dice Game Fig. 20-12 +
	13	13	22	12	13
Coolrunner CPLD	18 63	19 61	32 108	18 70	24 72
Spartan FPGA	38 20	32 18	36 19	23 14	31 16
Spartan II FPGA	30 16	30 15	35 19	30 16	30 19

