 


FIGURES FOR CHAPTER 9

MULTIPLExERS, DECODERS, AND PROGRAMMABLE LOGIC DEVICES



This chapter in the book includes:

- Objectives
- Study Guide
- 9.1 Introduction
- 9.2 Multiplexers
- 9.3 Three-State Buffers
- 9.4 Decoders and Encoders
- 9.5 Read-Only Memories
- 9.6 Programmable Logic Devices
- 9.7 Complex Programmable Logic Devices
- 9.8 Field Programmable Gate Arrays
- Problems

Click the mouse to move to the next page.
Use the ESC key to exit this chapter.

 


Figure 9-1: 2-to-1 Multiplexer and Switch Analog

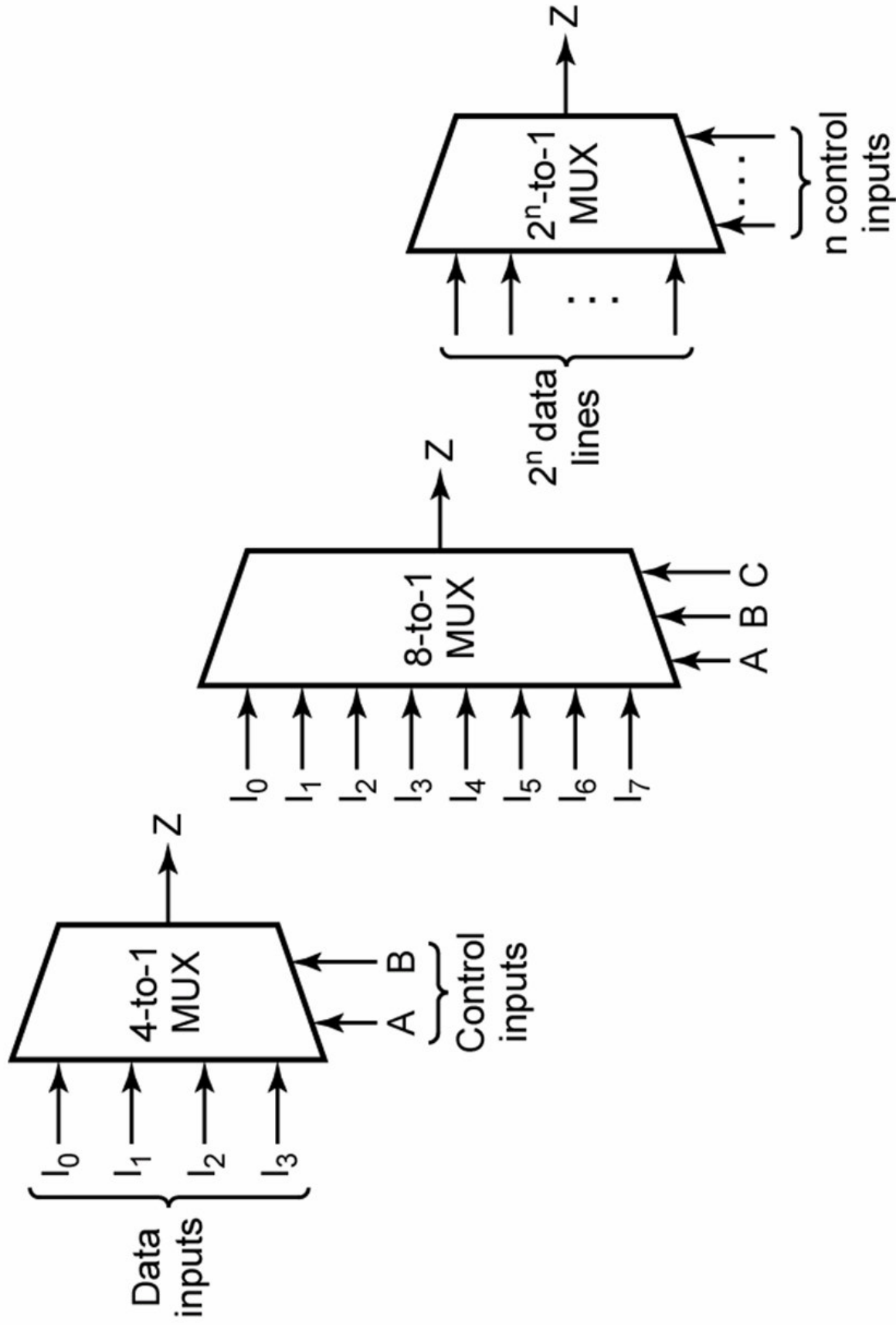


Figure 9-2: Multiplexers



 


Figure 9-3: Logic Diagram for 8-to-1 MUX

 


Figure 9-4: Quad Multiplexer Used to Select Data

 


Figure 9-5: Quad Multiplexer with Bus Inputs and Output

 


Figure 9-6: Gate Circuit with Added Buffer




 


Figure 9-7: Three-State Buffer

 

B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

(a)

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

(b)

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z

(c)

B	A	C
0	0	1
0	1	0
1	0	Z
1	1	Z

(d)

Figure 9-8: Four Kinds of Three-State Buffers




 


Figure 9-9: Data Selection Using Three-State Buffers

 

S1	S2	Z
X	0	X
X	1	X
0	X	0
1	X	1
Z	X	Z

Figure 9-10: Circuit with Two Three-State Buffers

 


Figure 9-11: 4-Bit Adder with Four Sources for One Operand



 


Figure 9-12: Integrated Circuit with Bi-Directional Input/Output Pin

 


Figure 9-13: 3-to-8 Line Decoder



a	b	c	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Figure 9-13: 3-to-8 Line Decoder

 


Figure 9-14a:
A 4-to-10 Line
Decoder
 (a) Logic diagram



 


Figure 9-14b:
A 4-to-10 Line Decoder (b) Block diagram



BCD Input				Decimal Output									
A	B	C	D	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	0	1	1	1	1	1	1	0	1	1	1
0	1	1	1	1	1	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0
1	0	1	0	1	1	1	1	1	1	1	1	1	1

Figure 9-14c:
A 4-to-10 Line Decoder (c) Truth Table




 


Figure 9-15: Realization of a Multiple-Output Circuit Using a Decoder

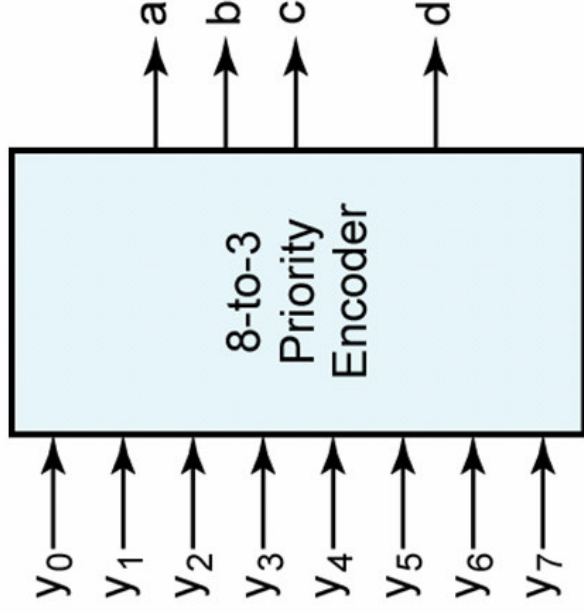




y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1

Figure 9-16: 8-to-3 Priority Coder



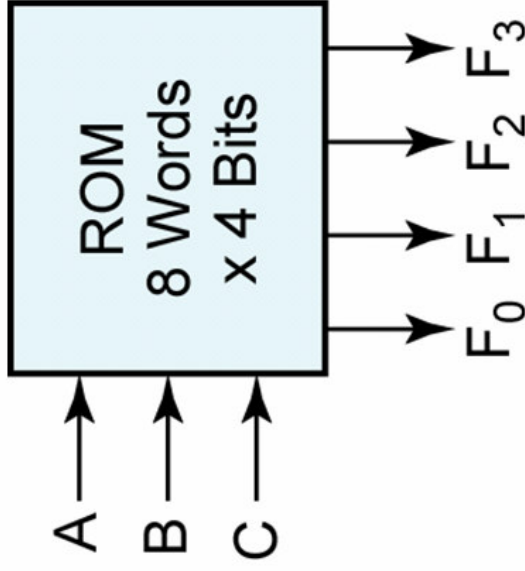


(a) Block diagram

A	B	C	F_0	F_1	F_2	F_3
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

typical data
stored in ROM
(2^3 words of
4 bits each)

(b) truth table for ROM

Figure 9-17: An 8-Word x 4-Bit ROM

 

n Input Variables	m Output Variables
00 ... 00	100 ... 110
00 ... 01	010 ... 111
00 ... 10	101 ... 101
00 ... 11	110 ... 010
⋮	⋮
11 ... 00	001 ... 011
11 ... 01	110 ... 110
11 ... 10	011 ... 000
11 ... 11	111 ... 101

Figure 9-18: Read-Only Memory with n Inputs and m Outputs

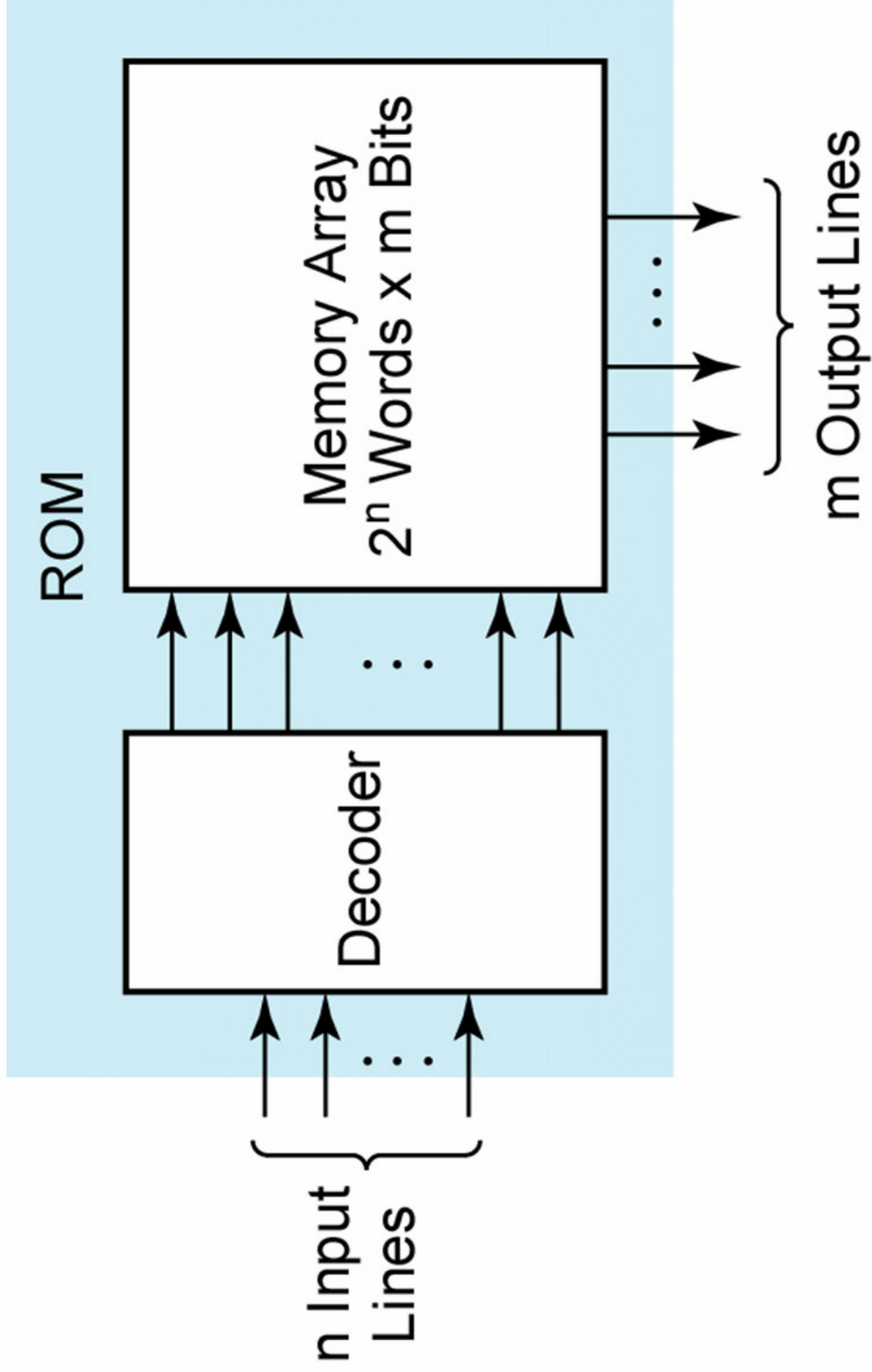


Figure 9-19: Basic ROM Structure



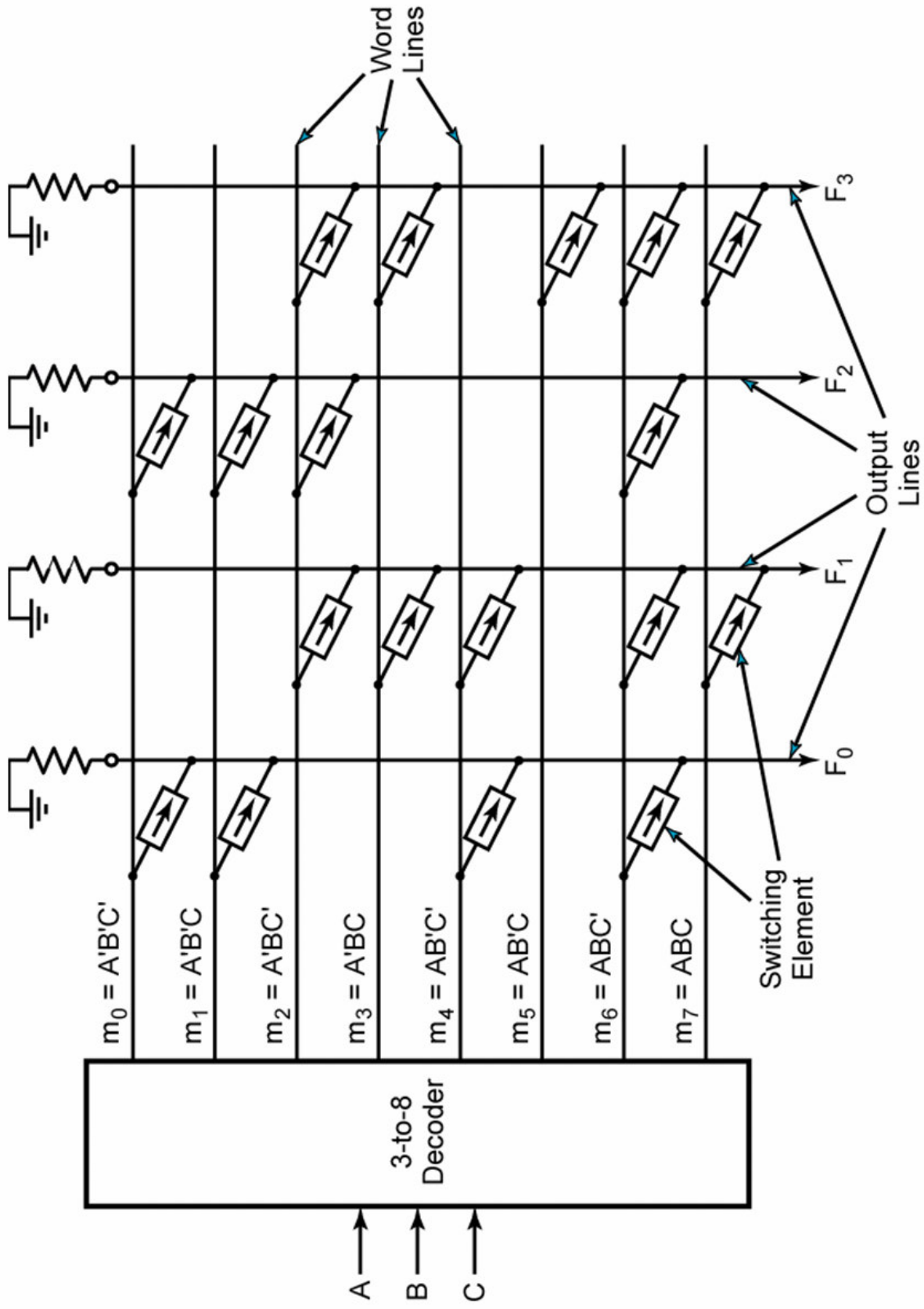


Figure 9-20: An 8-Word x 4-Bit ROM



 


Figure 9-21: Equivalent OR Gate for F_0

Input		Hex	ASCII Code for Hex Digit								
W	X	Y	Z	Digit	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0	0	1	1	0	0	0	0
0	0	0	1	1	0	1	1	0	0	0	1
0	0	1	0	2	0	1	1	0	0	1	0
0	0	1	1	3	0	1	1	0	0	1	1
0	1	0	0	4	0	1	1	0	1	0	0
0	1	0	1	5	0	1	1	0	1	0	1
0	1	1	0	6	0	1	1	0	1	1	0
0	1	1	1	7	0	1	1	0	1	1	1
1	0	0	0	8	0	1	1	1	0	0	0
1	0	0	1	9	0	1	1	1	0	0	1
1	0	1	0	A	1	0	0	0	0	0	1
1	0	1	1	B	1	0	0	0	0	1	0
1	1	0	0	C	1	0	0	0	0	1	1
1	1	0	1	D	1	0	0	0	1	0	0
1	1	1	0	E	1	0	0	0	1	0	1
1	1	1	1	F	1	0	0	0	1	1	0

Figure 9-22: Hexadecimal to ASCII Code Converter

©2004 Brooks/Cole



 


Figure 9-22: Hexadecimal to ASCII Code Converter



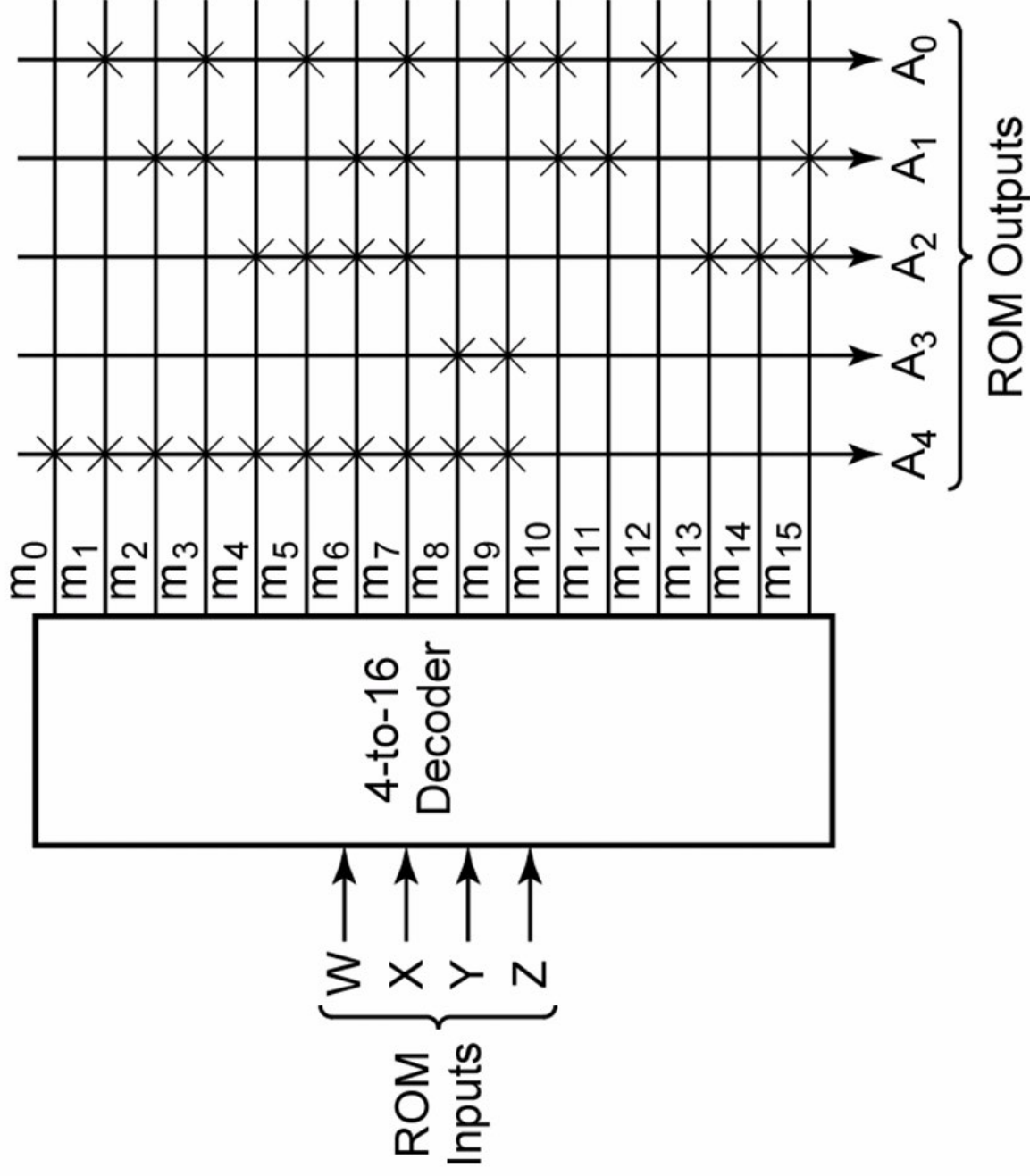


Figure 9-23: ROM Realization of Code Converter



 


Figure 9-24: Programmable Logic Array Structure

 


Figure 9-25: PLA with Three Inputs, Five Product Terms, and Four Outputs

 


Figure 9-26: AND-OR Array Equivalent to Figure 9-25



Table 9-1. PLA Table for Figure 9-25

Product Term	Inputs			Outputs			
	A	B	C	F_0	F_1	F_2	F_3
$A'B'$	0	0	-	1	0	1	0
AC'	1	-	0	1	1	0	0
B	-	1	-	0	1	0	1
BC'	-	1	0	0	0	1	0
AC	1	-	1	0	0	0	1

$$F_0 = A'B' + AC'$$

$$F_1 = AC' + B$$

$$F_2 = A'B' + BC'$$

$$F_3 = B + AC$$



(a) PLA table

	a	b	c	d	f_1	f_2	f_3
	0	1	-	1	1	1	0
	1	1	-	1	1	0	1
	1	0	0	-	1	0	1
	-	0	1	-	1	0	0
	-	-	1	-	0	1	0
	-	1	1	-	0	0	1


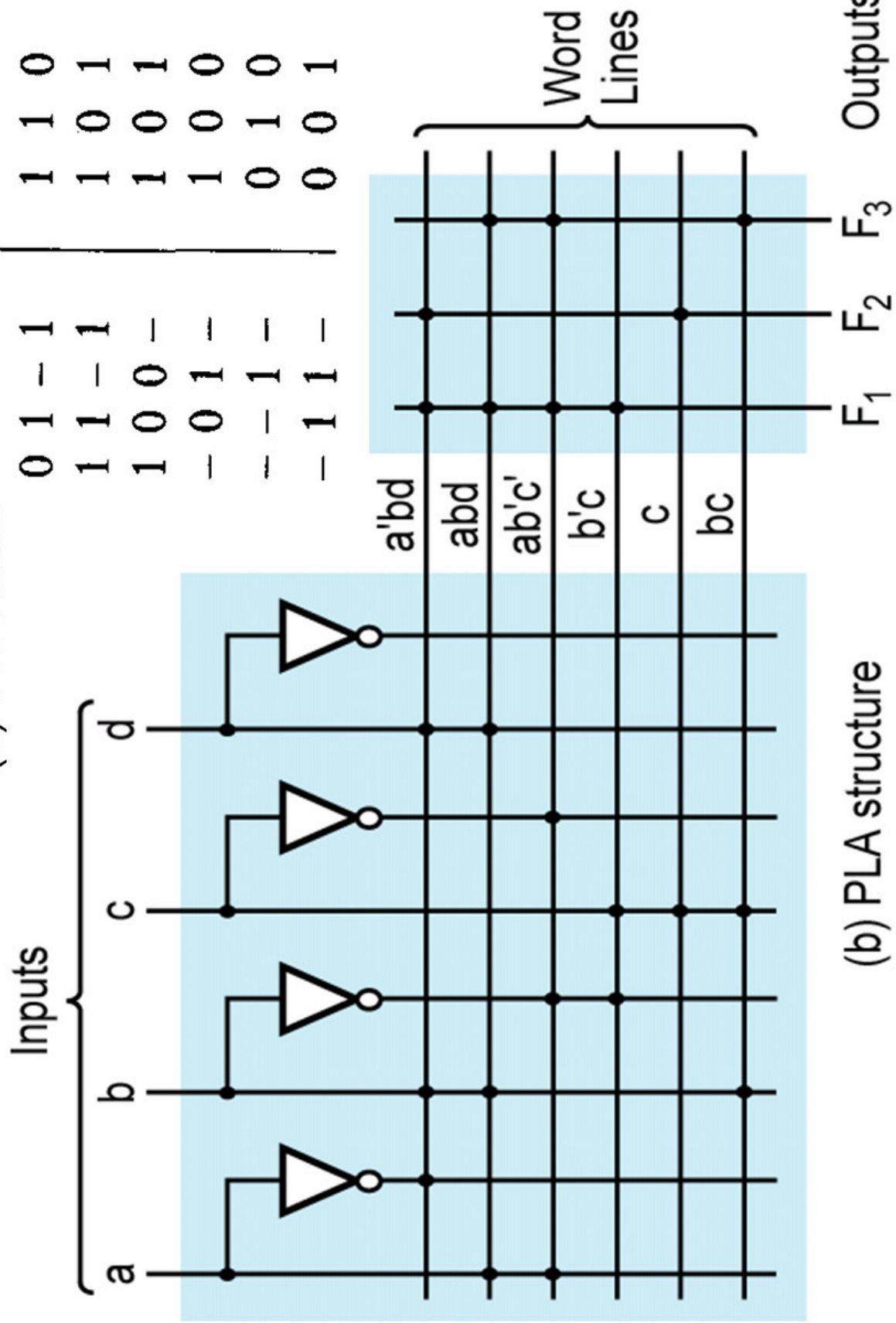


Figure 9-27b: PLA Realization of Equations

 



Buffer logically equivalent to



Section 9.6, p. 245



Section 9.6, p. 246




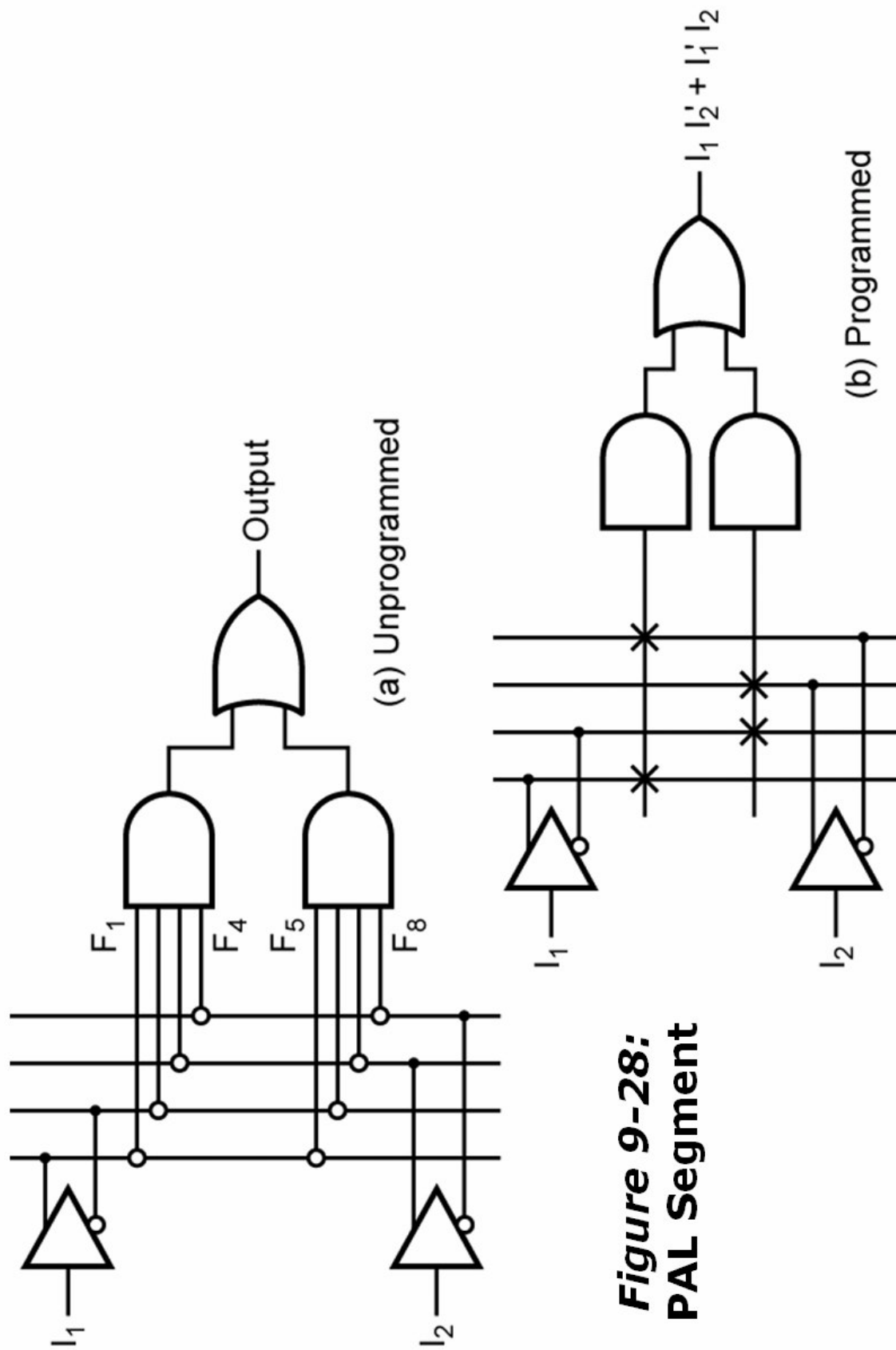


Figure 9-28:
PAL Segment

Figure 9-29:
Implementation
of a Full Adder
Using a PAL

 

 


Figure 9-30: Architecture of Xilinx XCR3064XL CPLD

(Figure based on figures and text owned by Xilinx, Inc., Courtesy of Xilinx, Inc. © Xilinx, Inc. 1999-2003. All rights reserved.)



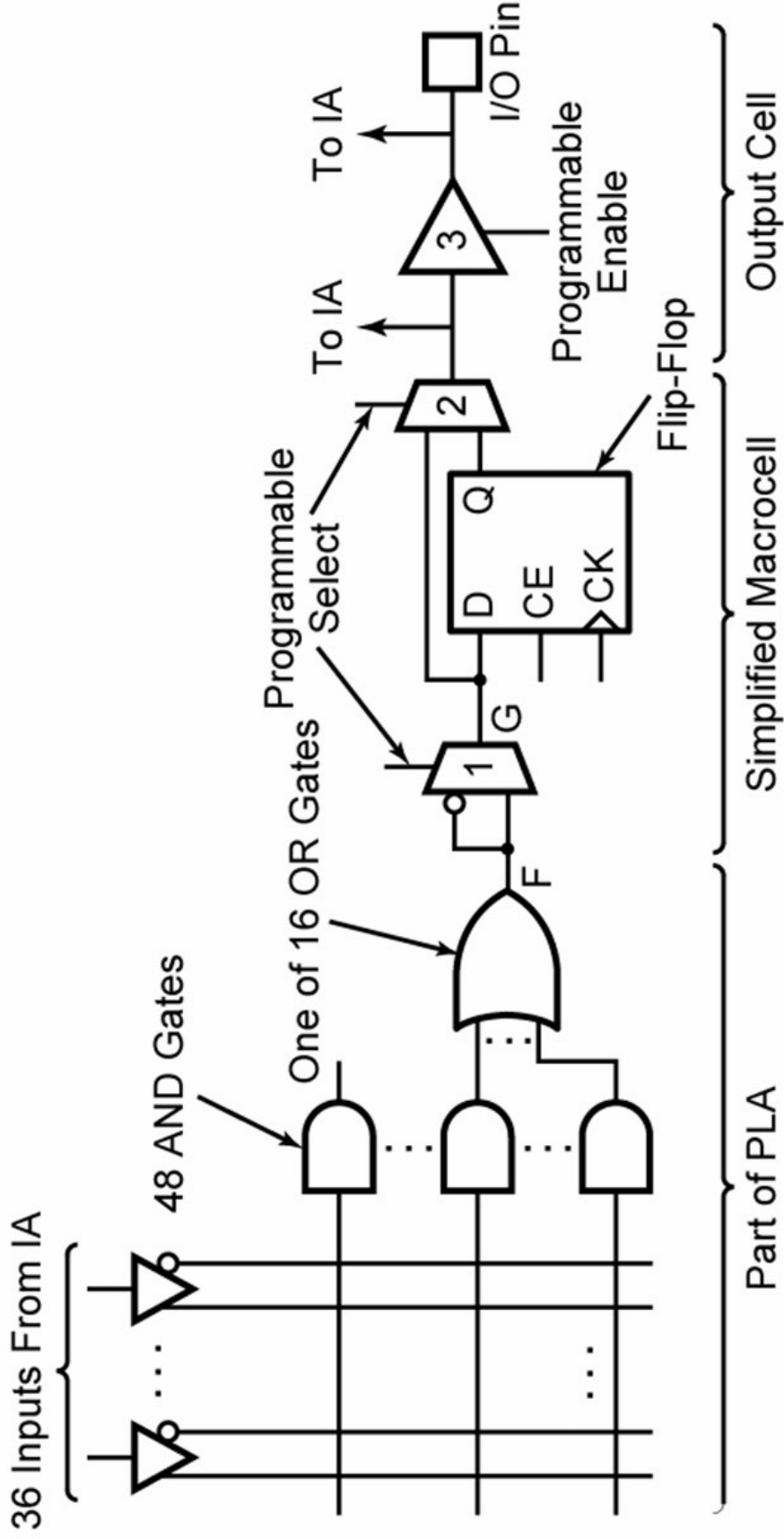


Figure 9-31: CPLD Function Block and Macrocell
 (A Simplified Version of XCR3064XL)




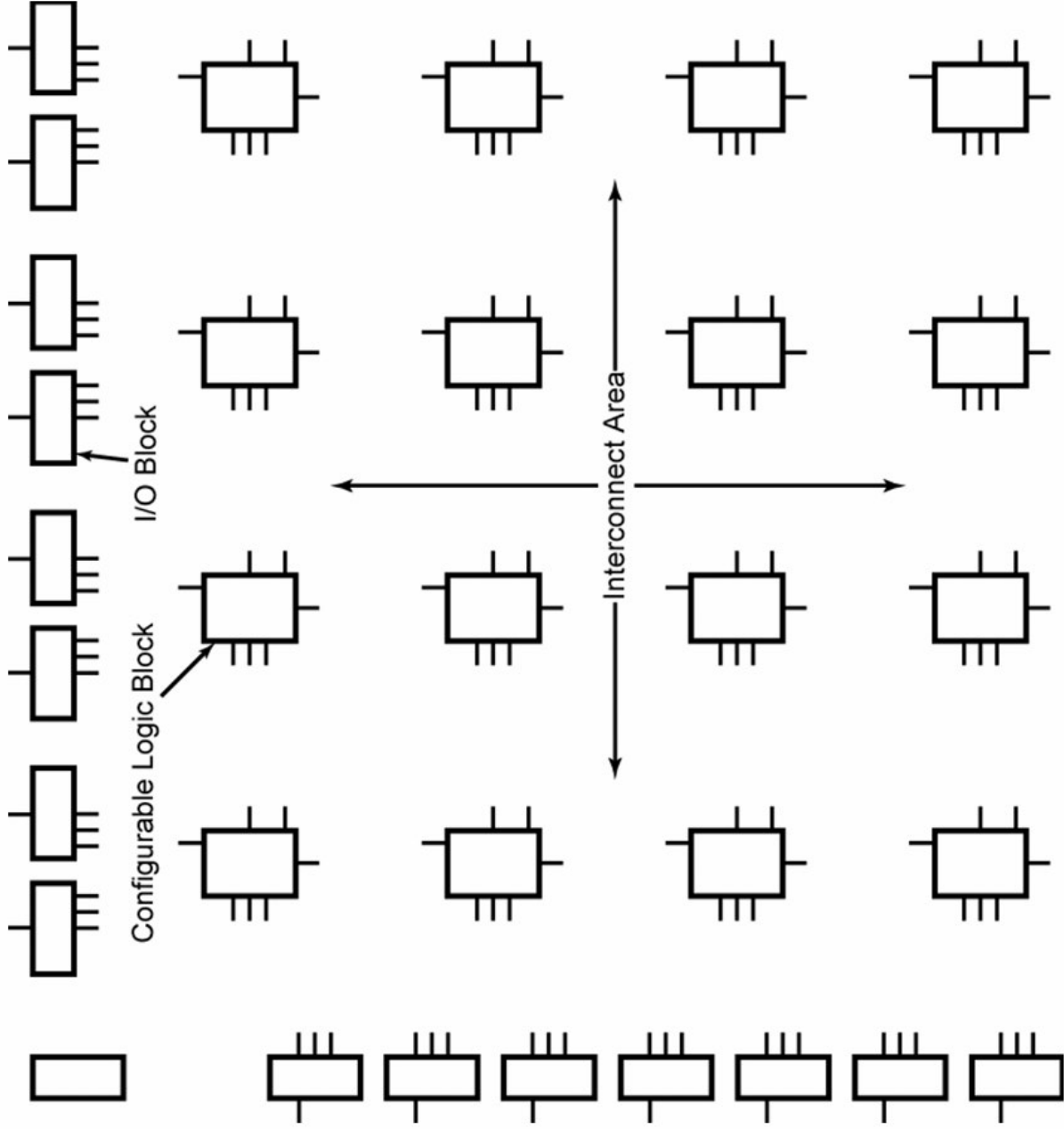


Figure 9-32: Layout of a Typical FPGA

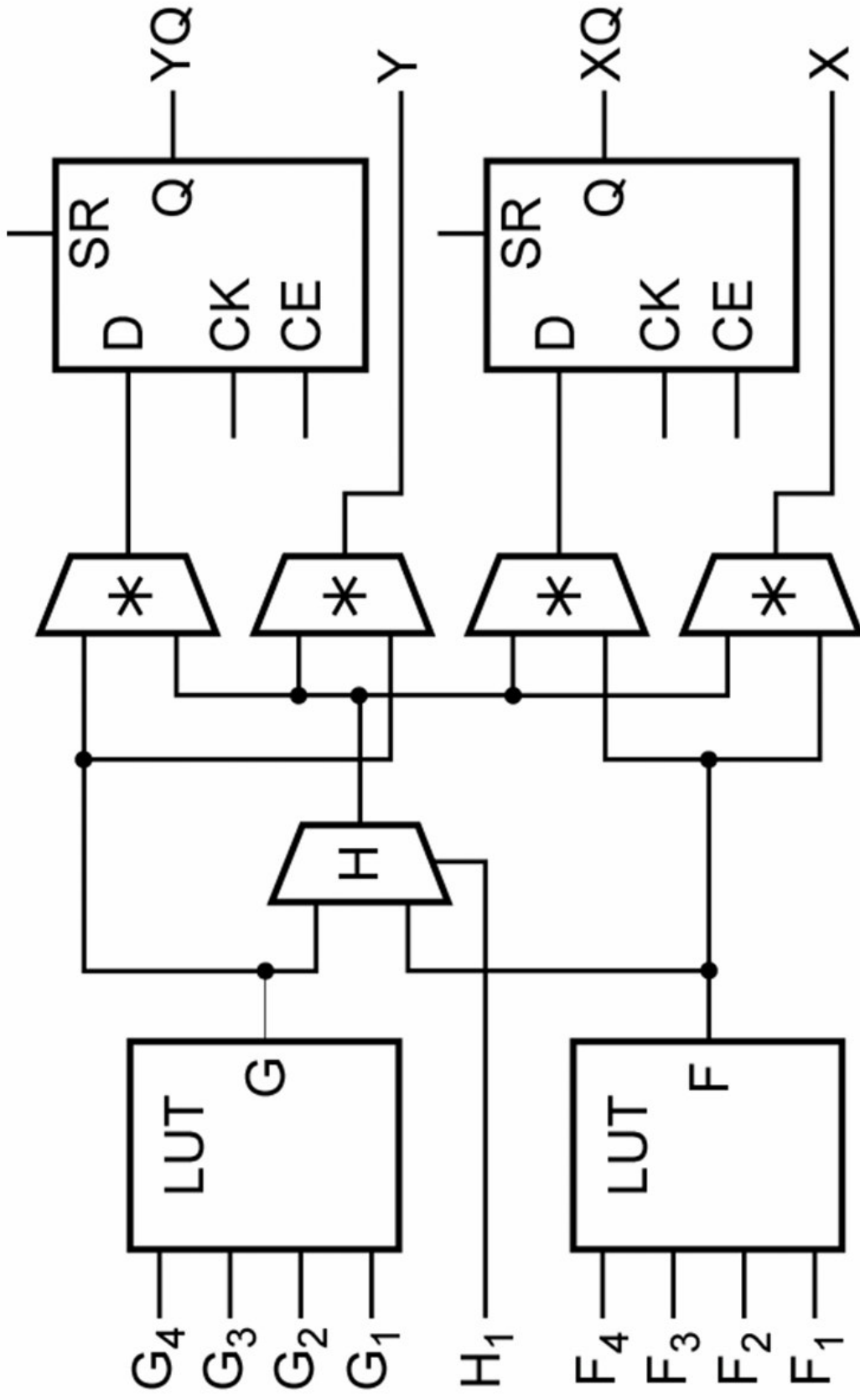



* = Programmable MUX

Figure 9-33: Simplified Configurable Logic Block (CLB)



abcd	F
0000	0
0001	1
.	.
.	.
.	.
1111	1

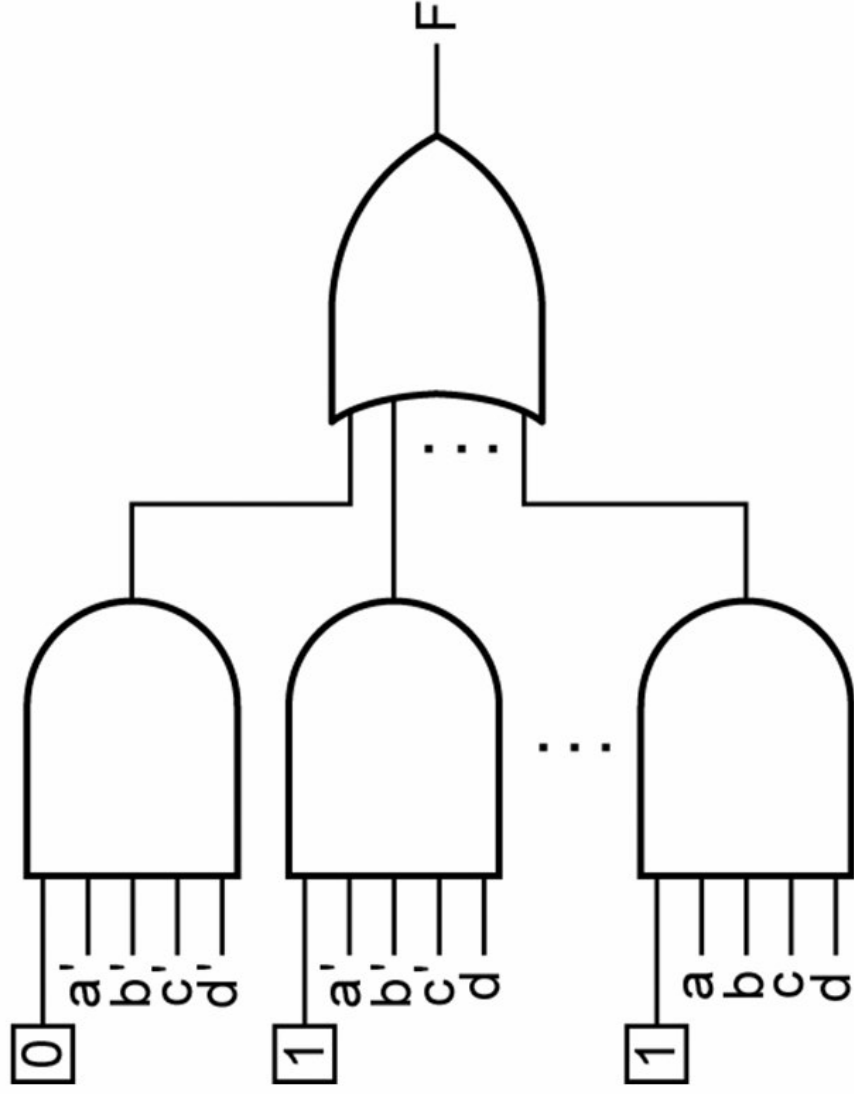


Figure 9-34:

Implementation of a Lookup Table (LUT)






 


Figure 9-35: Function Expansion Using a Karnaugh Map

 

 

(a) 5-variable function

 

(b) 6-variable function

Figure 9-36: Realization of Five- and Six-Variable Functions with Function Generators